

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year I Semester Regular & Supplementary Examinations December-2023

ANALOG ELECTRONIC CIRCUITS

(Electrical and Electronics Engineering)

Time: 3 Hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a List the characteristics of negative feedback amplifiers. **CO1 L1 6M**
 b A voltage series negative feedback amplifier has a voltage gain without feedback of $A=500$, input resistance $R_i=3\text{ k}\Omega$, output resistance $R_o=20\text{ k}\Omega$ and feedback ratio $\beta=0.01$. Calculate the voltage gain A_f , input resistance and output resistance of the amplifier with feedback. **CO3 L3 6M**

OR

- 2 a An amplifier has open loop gain 2000 and feedback ratio of 0.04, if the open loop gain changes by 10% due to temperature, find the percentage change in the gain of the amplifier feedback. **CO3 L3 6M**
 b Show that how a negative feedback reduces gain of an amplifier. **CO1 L1 6M**

UNIT-II

- 3 a Explain Barkhausen criterion for oscillations with suitable diagram. **CO1 L2 6M**
 b In the Hartley oscillator $L_2=0.4\text{mH}$ and $C=0.004\mu\text{F}$. If the frequency of the oscillator is 120kHz, find the value of L_1 . Neglect mutual inductance. Also calculate the frequency of oscillation if L_2 changes to 0.04 mH. **CO4 L3 6M**

OR

- 4 a In the Colpitts oscillator, $C_1=0.2\mu\text{F}$ and $C_2 = 0.02\mu\text{F}$. If the frequency of oscillator is 10kHz, find the value of inductor. Also calculate the frequency of oscillation if C_2 changes to $2\mu\text{F}$. **CO4 L3 6M**
 b Explain the concept of stability in oscillators in detail. **CO6 L2 6M**

UNIT-III

- 5 a What are the four different configuration of differential amplifier? **CO1 L1 6M**
 b For an Non-inverting amplifier, $R_1= 5\text{kohm}$, $R_f =10\text{ k}\Omega$ with input voltage $V_i = 0.5\text{V}$ and a load resistance of $R_L= 10\text{ k}\Omega$ is connected to the output terminal. Calculate i) V_o ii) A_{CL} iii) i_L and iv) load current i_o indicating proper direction of flow. **CO4 L3 6M**

OR

- 6 a What is voltage follower? What are its features and applications? **CO1 L1 6M**
 b Explain AC characteristics of op-amp. **CO5 L2 6M**

UNIT-IV

- 7 a The op-amp non-inverting summing circuit has the following parameters $V_{CC} = +15\text{ V}$, $V_{EE} = -15\text{V}$, $R = R_1= 1\text{ k}\Omega$, $R_f = 2\text{ k}\Omega$, $V_1 = +2\text{ V}$, $V_2 = -3\text{ V}$, $V_3 = +4\text{ V}$. Determine the output voltage V_o . **CO3 L3 6M**
 b Draw a neat circuit of astable multivibrator using op-amp and explain operation with waveforms. **CO2 L2 6M**

OR

- 8 a** Draw the input-output waveforms and frequency response of integrator. **CO1 L1 6M**
b Define the duty cycle .Identify the percentage of duty cycle if $T_{on} = 0.6$ msec , $T_{off} = 0.4$ msec. **CO4 L3 6M**

UNIT-V

- 9 a** Draw the frequency response of filters. **CO1 L3 6M**
b The basic step of a 9 bit DAC is 10.3 mV. If “000000000” represents 0 V. What output is produced if the input is “101101111”? **CO4 L3 6M**

OR

- 10 a** Explain the first order low pass butter worth filter with a neat circuit diagram. **CO2 L2 6M**
b Summarize the truth table for a flash type op-amp ADC using 8 by 3 priority encoder. **CO4 L2 6M**

***** END *****