

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year I Semester Regular & Supplementary Examinations December-2023

ELECTRONIC DEVICES AND CIRCUITS

(Electronics and Communication Engineering)

Time: 3 Hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- | | | | | | |
|---|---|---|-----|----|----|
| 1 | a | A PN junction germanium diode has a reverse saturation current of $10\mu\text{A}$ at the room temperature of 270C . It is observed to be $30\mu\text{A}$, when the room temperature is increased. Calculate the new room temperature. | CO2 | L3 | 6M |
| | b | Analyze the current components of a PN Junction Diode and derive the diode current equation. | CO2 | L4 | 6M |

OR

- | | | | | | |
|---|---|--|-----|----|----|
| 2 | a | Derive the expression for transition capacitance of a PN Junction Diode. | CO2 | L3 | 6M |
| | b | Explain Breakdown mechanisms in PN Junction Diode. | CO3 | L2 | 6M |

UNIT-II

- | | | | | | |
|---|---|--|-----|----|----|
| 3 | a | Draw the circuit symbol of Varactor diode, give its characteristics.and list its applications. | CO1 | L1 | 6M |
| | B | With neat circuit diagram and waveforms, explain the operation of Full Wave Rectifier with Capacitor filter and derive the expression for its ripple factor. | CO3 | L3 | 6M |

OR

- | | | | | | |
|---|---|--|-----|----|----|
| 4 | a | A Full Wave Rectifier circuit is fed from a transformer having a center-tapped secondary winding. The RMS voltage from either end of secondary to center tap is 30V . If the diode forward resistance is 2Ω and that of the half secondary is 8Ω , for a load of $1\text{K}\Omega$. Calculate DC power delivered to the load, efficiency of rectification and Transformer Utilization Factor (TUF) of secondary. | CO5 | L4 | 6M |
| | b | Give the classification of LCD based on construction and explain. List the advantages and applications of LCD. | CO1 | L2 | 6M |

UNIT-III

- | | | | | | |
|---|---|---|-----|----|----|
| 5 | a | Explain the characteristics of N-Channel enhancement type MOSFET. | CO1 | L2 | 6M |
| | b | Compare the performance of JFET with MOSFET. | CO1 | L1 | 6M |

OR

- | | | | | |
|------------|---|------------|-----------|-----------|
| 6 a | Evaluate the relation between α and β of a Transistor. | CO2 | L3 | 5M |
| b | With a neat diagram, explain how a transistor acts as an amplifier. | CO3 | L1 | 7M |

UNIT-IV

- | | | | | |
|------------|--|------------|-----------|-----------|
| 7 a | Define transistor biasing and explain the need for biasing. | CO2 | L1 | 3M |
| b | Derive the expression for Stability Factor, Sf. from Collector current equation. | CO3 | L4 | 4M |
| c | Explain the concept of DC and AC Load lines and discuss the criteria for fixing the Q-point. | CO3 | L2 | 5M |

OR

- | | | | | |
|------------|---|------------|-----------|-----------|
| 8 a | Estimate the condition for achieving Thermal Stability. | CO4 | L2 | 6M |
| b | If the various parameters of a CE amplifier which uses the self bias method are $V_{CC}=12v$, $R_1=10K\Omega$, $R_2=5K\Omega$, $R_c=1K\Omega$, $R_E=2K\Omega$ & $\beta=100$, find the operating point. Assume Si Transistor. | CO6 | L3 | 6M |

UNIT-V

- | | | | | |
|------------|--|------------|-----------|-----------|
| 9 a | Derive expressions for A_i , R_i , A_v and R_0 for a Common Collector Amplifier using simplified hybrid model. | CO5 | L3 | 6M |
| b | A voltage source of internal resistance, $R_s = 900\Omega$ drives a CC amplifier using load resistance $R_L=2000\Omega$. The CE h parameters are $h_{fe}=60$, $h_{ie}=1200\Omega$, $h_{oe} = 25\mu A/V$ and $h_{re} = 2 \times 10^{-4}$. Calculate A_i , R_i , A_v and R_0 using approximate analysis. | CO6 | L4 | 6M |

OR

- | | | | | |
|-------------|---|------------|-----------|-----------|
| 10 a | A CE amplifier is driven by a voltage source of internal resistance, $R_s = 1000\Omega$ and the load impedance of $R_C=2k\Omega$. The h-parameters are $h_{ie}=1.3k$, $h_{fe}=55$, $h_{oe} = 22\mu A/V$ and $h_{re} = 2 \times 10^{-4}$. Neglecting biasing resistors, Estimate the value of current gain, voltage gain, input impedance, output impedance for the value of Emitter Resistor $R_E = 200\Omega$ inserted in the emitter circuit. | CO4 | L4 | 6M |
| b | Draw the small signal model of FET. | CO2 | L1 | 6M |

***** END *****