

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR**  
(AUTONOMOUS)

**B.Tech II Year I Semester Regular & Supplementary Examinations December-2023**

**SWITCHING THEORY AND LOGIC DESIGN**

(Electronics and Communication Engineering)

**Time: 3 Hours**

**Max. Marks: 60**

(Answer all Five Units 5 x 12 = 60 Marks)

**UNIT-I**

- 1 a Express the following functions in Sum of Minterms and Product of Maxterms. CO1 L1 6M  
 i)  $F1(A,B,C,D) = B'D + A'D + BD$   
 ii)  $F2(x,y,z) = (xy + z)(xz+y)$   
 b Prove De Morgan's theorems using Perfect Induction Method. CO1 L3 6M

**OR**

- 2 a List the different Boolean expressions for Two binary Variables. CO1 L1 6M  
 b State Universal Gates and represent their truth tables with Graphic symbols. CO1 L1 6M

**UNIT-II**

- 3 Simplify the following Boolean function by using Tabulation method. CO2 L4 12M  
 $F = \Sigma (0, 1, 2, 8, 10, 11, 14, 15)$

**OR**

- 4 a Outline the disadvantage of K-Map method, of reducing a Boolean function and explain the ways to overcome it. CO1 L2 6M  
 b Demonstrate the steps involved in simplification of K-Map. CO1 L2 6M

**UNIT-III**

- 5 a Define Combinational Circuit and Explain the analysis procedure of a combinational logic circuit using suitable example. CO1 L2 6M  
 b Construct a BCD Adder-circuit using 4-bit binary adders. CO5 L3 6M

**OR**

- 6 a Recall Demultiplexer and Design an 1:8 demultiplexer using two 1:4 demultiplexer. CO4 L3 6M  
 b Define Multiplexer. Construct 4:1 multiplexer with logic gates and truth table. CO4 L3 6M

**UNIT-IV**

- 7 a Convert SR flip flop into JK Flip-Flop. Draw and explain its logic diagram. CO4 L2 6M  
 b Express Shift register and explain its types. CO1 L2 6M

**OR**

- 8 a Explain in brief about a 2-bit synchronous up-counter. CO6 L2 6M  
 b With the help of logic diagram, obtain the characteristic table of D & T Flip-Flops. Also draw their graphic symbols. CO3 L3 6M

**UNIT-V**

- 9 Elaborate in detail on Programmable Read Only Memory (PROM) with a suitable example. CO2 L2 12M

**OR**

- 10 a Classify various types of RAMs. CO1 L2 6M  
 b Compare ROM and RAM. CO1 L2 6M

\*\*\* END \*\*\*

