

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech. I Year I Semester Supplementary Examinations February-2024
BASIC ELECTRICAL & ELECTRONICS ENGINEERING

(Mechanical Engineering)

Time: 3 Hours

Max. Marks: 60

(Answer all Six Units 6 X 10 = 60 Marks)


PART-A

UNIT-I

- 1 a Write the derivation for equivalent resistance in series circuit. **CO1 L3 5M**
 b A 5ohm , 10 ohm ,20 ohm, resistors are connected in series across 120V DC supply calculates Total Resistance, Total current, Voltage drop across each resistor. **CO1 L4 5M**

OR

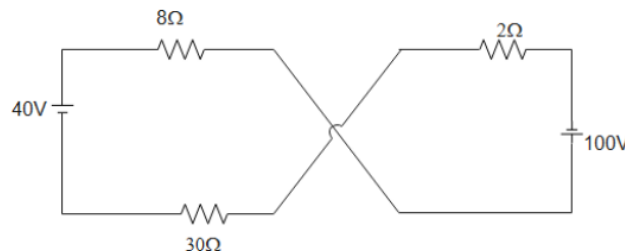
- 2 a Find the voltage across 30 ohm resistor and current across 30 ohm resistor in the given circuit as shown below. **CO1 L2 5M**



- b Write the derivation of RMS Value of Alternating voltage. **CO1 L3 5M**

UNIT-II

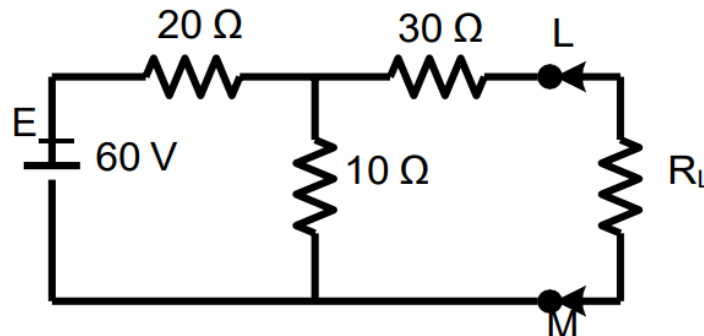- 3 Determine the maximum power delivered to the load resistance R_L . **CO2 L3 10M**



OR

- 4 a Explain Long Shunt Compound Generator and short shunt generator with neat diagram **CO2 L3 5M**
 b List the applications of different types of dc generators. **CO2 L5 5M**

UNIT-III

- 5 a Derive Torque equation of dc motor. **CO3 L3 5M**
 b The counter EMF of Shunt motor is 227 V. The field resistance is 160Ω and field current 1.5A. If the line current is 36.5A, find the armature resistance also find armature current when the motor is stationary. **CO3 L5 5M**

OR

- 6 a Explain the constructional details of transformer. **CO3 L2 6M**
 b A 20 kVA, 2000/200V, 50Hz transformer has 66 secondary turns. Calculate the number of primary turns and primary and secondary currents. Neglect losses. **CO3 L4 4M**

PART-B

UNIT-IV

- 7 a Explain the working of a PN junction diode under forward and reverse bias. **C05 L2 5M**
b Sketch the V-I Characteristics of a PN Junction Diode. **C05 L3 5M**

OR

- 8 a Explain the working principle of Bridge Rectifier with neat circuit diagram. Also draw its input and output waveforms. **C05 L2 5M**
b Explain the working principle of Full wave rectifier with a capacitor filter. **C05 L2 5M**

UNIT-V

- 9 a What is a Bipolar junction Transistor? Mention its types. **C05 L1 5M**
b Discuss the operation of NPN transistor with neat schematic diagram. **C05 L2 5M**

OR

- 10 a Derive the relationship between α , β and γ of a Transistor. **C05 L3 5M**
b A transistor operating in CB configuration has $I_C = 2.98\text{mA}$, $I_E = 3.00\text{mA}$ and $I_{CO} = 0.01\text{mA}$. Determine the current that will flow in the collector circuit when connected in CE configuration with a base current of $30\mu\text{A}$. **C06 L3 5M**

UNIT-VI

- 11 a With a neat diagram, explain the Transfer characteristics of N-channel JFET. **C05 L2 5M**
b Sketch the transfer characteristics of P-channel JFET. **C05 L3 5M**

OR

- 12 a List the differences between N-channel JFET and P-channel JFET. **C05 L2 5M**
b Compare between CS, CG, CD configuration of JFET. **C05 L4 5M**

***** END *****