

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)**

B.Tech I Year I Semester Regular Examinations February-2024

BASIC ELECTRICAL & ELECTRONICS ENGINEERING

(Common to EEE & CSIT)

Time: 3 Hours

Max. Marks: 70

PART-A (ELECTRICAL)

(Answer all the Questions 5 x 1 = 5 Marks)

- | | | | | |
|---|--|-----|----|----|
| 1 | a State Kirchoff's laws. | CO1 | L1 | 1M |
| | b Write any three applications of a DC Motor. | CO2 | L1 | 1M |
| | c What are the Conventional Energy sources? | CO3 | L1 | 1M |
| | d What is the power rating of Air Conditioner and Fan? | CO3 | L1 | 1M |
| | e Define unit of Electrical Energy. | CO3 | L1 | 1M |


(Answer all Three Units 3 x 10 = 30 Marks) (ELECTRICAL)

UNIT-I

- | | | | | |
|---|--|-----|----|----|
| 2 | a Determine the Equivalent Capacitance when the Capacitors are connected in Series & Parallel. | CO2 | L3 | 5M |
| | b Explain about the Energy Sources. | CO4 | L2 | 5M |

OR

- | | | | | |
|---|---|-----|----|----|
| 3 | a State the Super position theorem and explain with an example in detail. | CO2 | L3 | 4M |
| | b Determine the current in a branch A-B by using Superposition theorem. | CO2 | L3 | 6M |

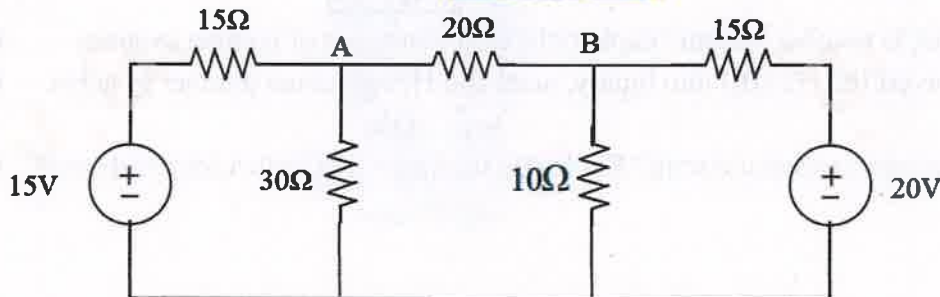

UNIT-II

- | | | | | |
|---|--|-----|----|-----|
| 4 | Draw and explain the construction features of a dc machine. | CO2 | L4 | 10M |
| | | | | OR |
| 5 | Explain construction and operating principle of Permanent Magnet Moving Coil (PMMC) instruments. | CO2 | L2 | 10M |

UNIT-III

- | | | | | |
|---|---|-----|----|-----|
| 6 | Explain Layout and operation of Wind power generating station. | CO3 | L2 | 10M |
| | | | | OR |
| 7 | a What are the working principles of fuse and MCB? | CO1 | L1 | 4M |
| | b What is an electric shock? How to prevent electric shock at home? | CO4 | L1 | 6M |

PART-B (ELECTRONICS)

(Answer all the Questions 5 x 1 = 5 Marks)

- | | | | | | |
|---|---|---|-----|----|----|
| 1 | f | What is meant by semiconductor? | CO1 | L1 | 1M |
| | g | How PN diode is formed? | CO1 | L1 | 1M |
| | h | Define amplifier. | CO2 | L4 | 1M |
| | i | What is the function of a transducer? | CO2 | L1 | 1M |
| | j | Write the names of basic logical operators. | CO4 | L3 | 1M |

(Answer all Three Units 3 x 10 = 30 Marks) (ELECTRONICS)

UNIT-IV

- 8 With a neat sketch Explain the input and output and current gain characteristics of a transistor in common base (CB) configuration. CO2 L1 10M

OR

- 9 Explain the operation of pn junction diode under forward bias and reverse bias conditions with the help of V-I characteristics curve. CO1 L5 10M

UNIT-V

- 10 Explain the working of a full wave bridge rectifier with a neat diagram with wave forms. CO2 L1 10M

OR

- 11 What is a Voltage Regulator? How the Zener Diode works as a Voltage Regulator? CO2 L1 10M

UNIT-VI

- 12 a What is number system? explain the different types of number systems CO3 L2 5M
b Convert the (555)₁₀ into binary, octal and Hexadecimal number systems. CO3 L1 5M

OR

- 13 Define combinational circuit? Explain Half Adder and Full Adder with truth table. CO3 L2 10M

*** END ***