

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech. I Year I Semester Supplementary Examinations February-2024

PRINCIPLES OF ELECTRICAL ENGINEERING

(Common to CSE, CSIT, CSM, CIC, CAD, CCC & CAI)


Time: 3 Hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)


UNIT-I

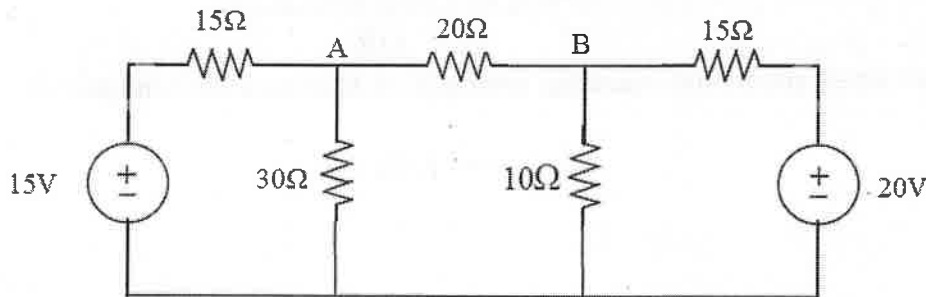- 1 a State and Explain about the ohm's law. CO1 L1 6M
 b Determine the current in branch A-B by using KVL. CO1 L2 6M



OR

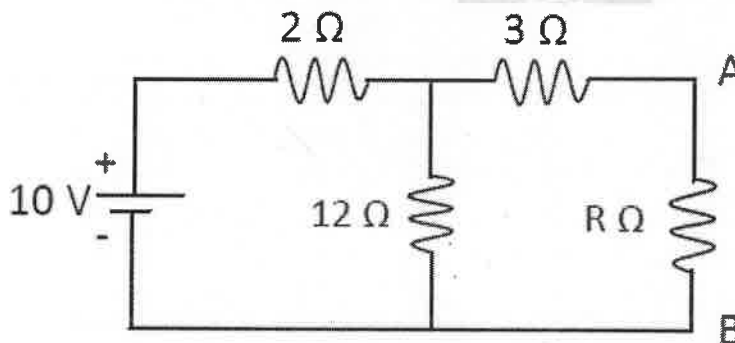- 2 a State and Prove Maximum Power Transfer Theorem. CO1 L2 6M
 b Draw the Norton's equivalent circuit for the circuit shown in figure. CO1 L2 6M



UNIT-II

- 3 a Define active power, apparent power, and reactive power. CO3 L2 6M
 b The impedances of series circuit are $Z_1 = (6+j8)$ ohms and $Z_2 = (8-j6)$ ohms. If the applied voltage is 120V, find total impedance, current and power factor. Draw the phasor diagram. CO3 L3 6M

OR

- 4 a Derive an expression for the current and impedance for a series RL circuit excited by a Sinusoidally alternating voltage. Draw the phasor diagrams. CO3 L2 6M
 b A series circuit consisting of a 10Ω resistor, a $100\mu\text{F}$ capacitor and a 10 mH inductor is driven by a 50 Hz a.c. voltage source of maximum value 100 volts. Calculate the equivalent impedance, Current in the circuit and the phase angle. CO3 L3 6M

UNIT-III

5 Explain the Constructional details of DC machine with neat sketch. CO4 L2 12M

OR

6 What are the different types of DC. motors. Explain in detail. CO4 L2 12M

UNIT-IV

7 Explain the Working principle of single phase transformer. CO5 L2 12M

OR

8 Define voltage regulation of an alternator. Explain procedure to determine voltage regulation by Synchronous Impedance Method. CO5 L3 12M

UNIT-V

9 Explain operating principle of Moving Iron (MI) instruments. CO6 L2 12M

OR

10 Explain construction and operating principle of Moving Coil Ammeter in detail. CO6 L2 12M

***** END *****

