

Reg. No: 

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR**

(AUTONOMOUS)

**B.Tech II Year I Semester Supplementary Examinations Feb-2021****DIGITAL LOGIC DESIGN**

(Common to CSE &amp; CSIT)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

**UNIT-I**

1 Explain about complements with examples? 12M

OR

2 Convert the following 12M

i)  $(1AD)_{16} = ( )_{10}$

ii)  $(453)_8 = ( )_{10}$

iii)  $(10110011)_2 = ( )_{10}$

iv)  $(5436)_{10} = ( )_{16}$

**UNIT-II**

3 Simplify the Boolean expression using K-MAP 12M

$$F(A,B,C,D,E) = \sum m(0,2,4,6,9,11,13,15,17,21,25,27,29,31)$$

OR

4 a Design the circuit by Using NAND gates  $F = ABC' + DE + AB'D'$  6Mb Design the circuit by Using NOR gates  $F = (X+Y) \cdot (X'+Y'+Z')$  6M**UNIT-III**

5 a Implement the following Boolean function using 8:1 multiplexer 6M

$$F(A,B,C,D) = \sum m(0,1,2,5,7,8,9,14,15)$$

b Explain about Decimal Adder? 6M

OR

6 a What is combinational circuits and explain analysis and design procedure of combinational circuits? 6M

b Explain about Priority encoder? 6M

**UNIT-IV**

7 a Explain the Logic diagram of JK flip-flop? 6M

b Write difference between Combinational &amp; Sequential circuits? 6M

OR

8 a Explain about Ring counter? 6M

b Explain about ripple counter? 6M

**UNIT-V**

9 a Write a short notes on Programmable array Logic? 6M

b Explain about Error correction &amp; Detection Codes? 6M

OR

10 Implement the following function using PLA 12M

$$A(x,y,z) = \sum m(1,2,4,6), B(x,y,z) = \sum m(0,1,6,7) \text{ and } C(x,y,z) = \sum m(2,6)$$

\*\*\* END \*\*\*