

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech III Year I Semester Supplementary Examinations Feb-2021

LINEAR IC APPLICATIONS

(Common to ECE & EEE)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a Draw and explain the various functional blocks of an operational amplifier IC. 6M
b Discuss the DC characteristics of an OP-AMP in detail. 6M

OR

- 2 a Compare different configurations of differential amplifier. 6M
b Explain the dual input balanced output differential amplifier with a neat circuit diagram. 6M

UNIT-II

- 3 a Explain voltage shunt feedback amplifier with Voltage gain and input resistance. 8M
b In Non-inverting inverting feedback op-amp $R_1 = 10K\Omega$, $R_f = 100K\Omega$ and $V_{in} = 1V$ then the load of $25K\Omega$ is connected to the output terminal, calculate I_1 , V_o , I_L and I_o . 4M

OR

- 4 a Draw and Explain the high frequency equivalent model of the op-amp. 7M
b Explain about the unity gain bandwidth product that how influences the frequency response. 5M

UNIT-III

- 5 Explain & Derive the expression for 3 input non-inverting summing amplifier with circuit diagram. 12M

OR

- 6 a Derive the output voltage V_o of practical differentiator circuit. 6M
b Draw a neat circuit of an integrator circuit. Explain the functioning with the input-output Waveforms. 6M

UNIT-IV

- 7 a What is the purpose of low pass filter in a phase Locked Loop? Describe different types of low pass filters used in a PLL. 6M
b Explain the performance parameters of multiplier & its characteristics. 6M

OR

- 8 a Draw and explain the operation of Wein bridge oscillator and derive its frequency expression. 6M
b Generate a triangular wave from the square wave with a neat expressions. 6M

UNIT-V

- 9 a Explain about the sample and hold circuits. 6M
b Explain about flash type ADC. 6M

OR

- 10 a Explain the operation of Weighted Resistor DAC with the help of circuit Diagram. 6M
b The basic step of a 9 bit DAC is $10.3mV$. If "000000000" represents 0 V. What output is produced if the input is "101101111". 6M

*** END ***