

**Reg. No:**

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR**

(AUTONOMOUS)

**B Tech II Year I Semester Supplementary Examinations Feb-2021**

**NETWORK THEORY**

(Electronics and Communication Engineering)

Time: 3 hours

Max. Marks: 60

**PART-A**

(Answer all the Questions 5 x 2 = 10 Marks)


- 1 a Define Duality & Dual networks. 2M
- b Draw the block diagram of band-pass and band-elimination filters. 2M
- c What are the initial conditions? Explain briefly. 2M
- d Define Two-port network. 2M
- e Write the expression for exponential form of Fourier series. 2M

**PART-B**

(Answer all Five Units 5 x 10 = 50 Marks)

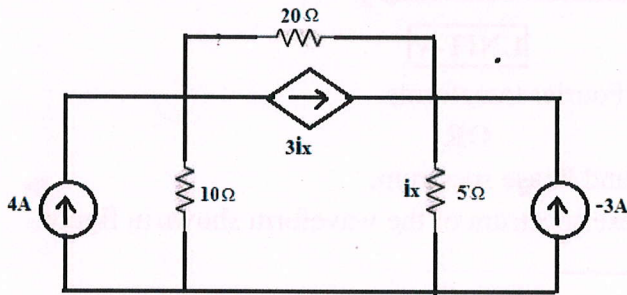**UNIT-I**


- 2 a Determine  $i_x$  for the following network. 5M



- b Explain about source transformation briefly. 5M

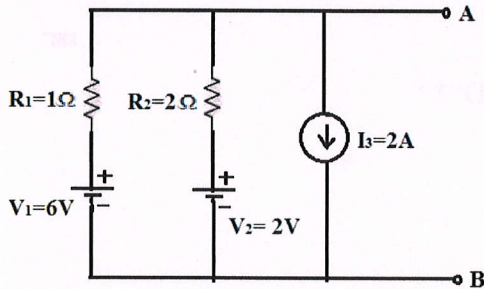**OR**

- 3 a State and prove Tellegen's theorem. 5M
- b Determine the equivalent current source between the terminals A and B. 5M



**UNIT-II**

- 4 a A series RLC circuit has  $R=10\Omega$ ,  $L=0.1H$  and  $C=50\mu F$ . The applied voltage is 100V. Find Resonant frequency & Quality factor of a coil. 5M
- b Explain about Propagation constant and Characteristic impedance in T-network filters. 5M

**OR**

- 5 a Explain about Parallel resonance with phasor diagrams. 5M
- b Explain about classification of filters. 5M

## UNIT-III

- 6 a Derive the Transient Response of Series RC circuits with Pulse excitation 5M  
 b A series RL circuit with  $R=30\Omega$  and  $L=15H$  has a constant voltage  $V=60v$  applied at  $t=0$ . Determine the current "I", voltage across resistor and voltage across inductor. 5M

OR


- 7 Derive the Transient Response of Series RLC circuit with Sinusoidal excitation. 10M

## UNIT-IV

- 8 a The given ABCD parameters are,  $A=2$ ,  $B=0.9$ ,  $C=1.2$ ,  $D=0.5$ . Find Y-parameters. 5M  
 b Derive the expressions for Chain parameters in terms of Z-parameters. 5M

OR

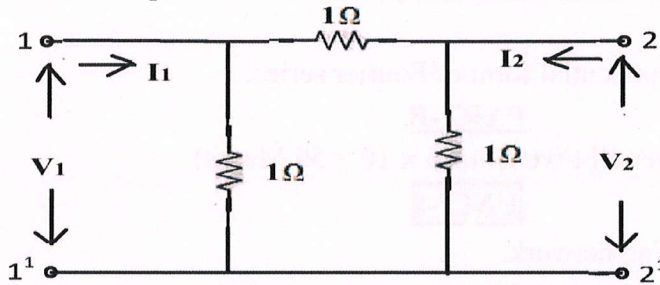- 9 a Explain about h-parameters in terms of y-parameters. 5M  
 b Find the Z-parameters of the network shown in below figure. 5M




## UNIT-V

- 10 Write and prove the properties of Fourier transforms. 10M

OR

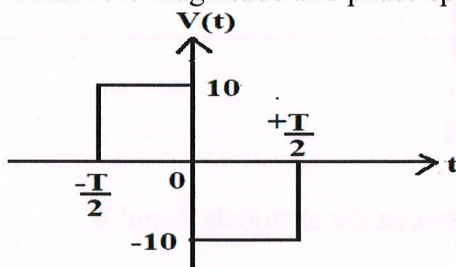- 11 a Explain about Line spectrum and Phase spectrum. 5M  
 b Obtain the magnitude and phase spectrum of the waveform shown in figure. 5M



\*\*\*END\*\*\*