

Reg. No:

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY: PUTTUR**  
(AUTONOMOUS)

**B. TECH II Year I Semester Regular Examinations Feb-2021**  
**BASIC ELECTRICAL & ELECTRONICS ENGINEERING**  
(Mechanical Engineering)

Time: 3 hours

Max. Marks: 60


(Answer all Six Units 6 X 10 = 60 Marks)

**PART- A****UNIT-I**


- Q.1** Three resistances of values 20, 30 and 50 are connected in series across 20 V DC supply. **10M**  
Calculate, i) Equivalent resistance of the circuit. ii) Total current from the supply. iii) Voltage drop across each resistor. iv) Power dissipated in each resistor.

OR

- Q.2** Find the current delivered by the source for the circuit shown in figure. **10M**

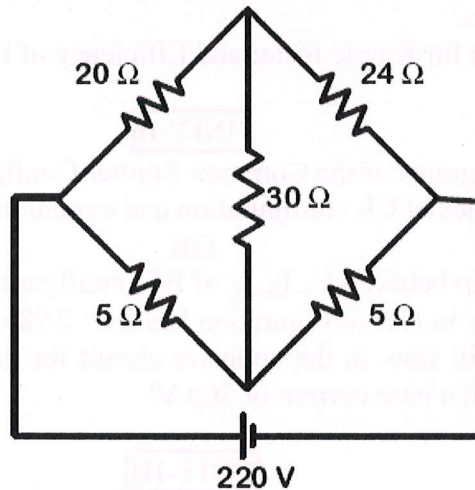**UNIT-II**

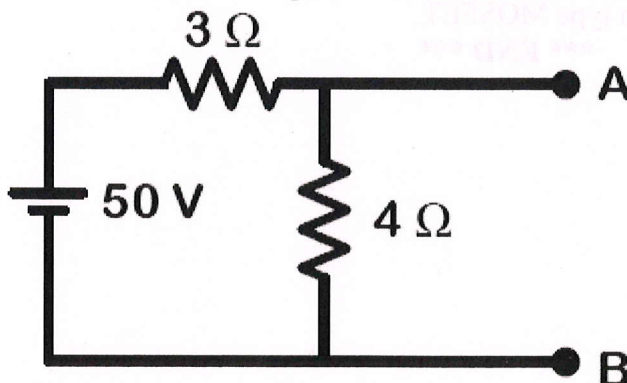- Q.3** a State Thevenin's theorem. **2M**  
b Find the Thevenin's equivalent circuit across AB for the circuit shown. **8M**



OR

- Q.4** a The given ABCD parameters are  $A=2$ ,  $B=0.9$ ,  $C=1.2$ ,  $D=0.5$ . Find Y-parameters. **5M**  
b The given Y-parameters are  $Y_{11}=0.5$ ,  $Y_{12}=Y_{21}=0.6$ ,  $Y_{22}=0.9$ . Find the impedance parameters. **5M**

**UNIT-III**

- Q.5** a Derive Torque equation of dc motor. 5M  
 b The counter emf of Shunt motor is 227 V. The field resistance is  $160\Omega$  and field current 1.5A. If the line current is 36.5A, find the armature resistance also find armature current when the motor is stationary. 5M

**OR**

- Q.6** a Explain constructional details of transformer. 5M  
 b A 20 kVA, 2000/200 V, 50 Hz transformer has 66 secondary turns. Calculate the number of primary turns and primary and secondary currents. Neglect losses. 5M

**PART - B****UNIT-I**

- Q.7** Describe the working of a PN junction diode when it is connected in forward bias and reverse bias. Draw VI Characteristics of PN Junction Diode. 10M

**OR**

- Q.8** a With neat diagram, explain the working principle of Half Wave Rectifier. Draw its input and output waveforms. 5M  
 b Derive the expression for Ripple factor and Efficiency of Half Wave Rectifier. 5M

**UNIT-II**

- Q.9** a Discuss with neat diagrams of the Common Emitter Configuration. 5M  
 b Draw the characteristics of CE configuration and explain it. 5M

**OR**

- Q.10** a Derive the relationship between  $I_C$ ,  $I_B$ ,  $I_E$  of BJT configuration. 5M  
 b A transistor operating in CB configuration has  $I_C = 2.98\text{mA}$ ,  $I_E = 3.00\text{mA}$  and  $I_{CO} = 0.01\text{mA}$ . What current will flow in the collector circuit for this transistor when connected in CE configuration with a base current of  $30\mu\text{A}$ ? 5M

**UNIT-III**

- Q.11** a Explain the Drain characteristics of JFET. 5M  
 b Explain the transfer characteristics of JFET. 5M

**OR**

- Q.12** a Draw the construction of Enhancement type MOSFET and explain its operation. 5M  
 b Explain the operation of Depletion type MOSFET 5M

**\*\*\* END \*\*\***