

Reg. No: 

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR  
(AUTONOMOUS)**

**B.Tech I Year II Semester Supplementary Examinations Dec 2019**

**ELECTRIC CIRCUITS-I  
(EEE)**

Time: 3 hours

Max. Marks: 60

**PART-A**

(Answer all the Questions 5 x 2 = 10 Marks)


- |   |   |    |
|---|---|----|
| 1 | a State Kirchoff's laws.                | 2M |
|   | b Define form factor.                   | 2M |
|   | c State Norton's theorem.               | 2M |
|   | d Define resonant frequency.            | 2M |
|   | e What are passive and active elements? | 2M |

**PART-B**

(Answer all Five Units 5 x 10 = 50 Marks)

**UNIT-I**


- |   |  |    |
|---|--|----|
| 2 | a Find the equivalent resistance across the terminals A and B of the network shown in figure using Star delta transformation | 5M |
|---|--|----|

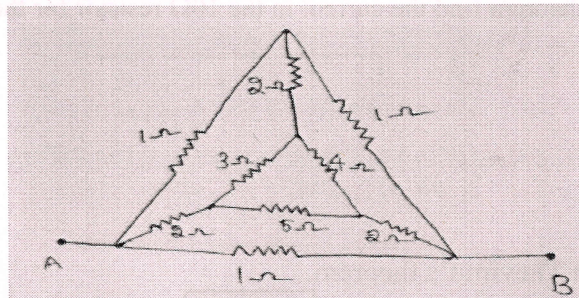

- |   |   |    |
|---|---|----|
| b | Derive the expression for Delta connected resistances in terms of star connected resistances. | 5M |
|---|---|----|

**OR**


- |   |  |    |
|---|--|----|
| 3 | a Find the current passing through each resistor for the circuit shown in figure | 5M |
|---|--|----|

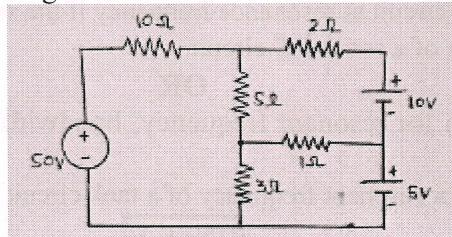

- |   |  |    |
|---|--|----|
| b | What are the types of sources? Explain them with suitable diagrams and characteristics | 5M |
|---|--|----|

**UNIT-II**

- |   |  |    |
|---|--|----|
| 4 | a The full wave rectified sine wave shown in figure has a delay angle of 60°. Calculate the average value and RMS value. | 5M |
|---|--|----|

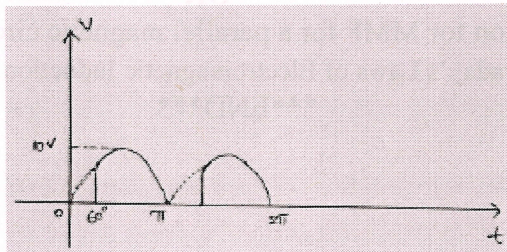


- |   |   |    |
|---|---|----|
| b | A 1KΩ resistor is connected in series with an inductance of 50mH across a 230V, 50Hz AC supply. Find (a) Inductive reactance (b) Impedance (c) Current (d) Phase angle (e) Voltage drop resistance (f) Voltage drop across Inductance | 5M |
|---|---|----|




OR

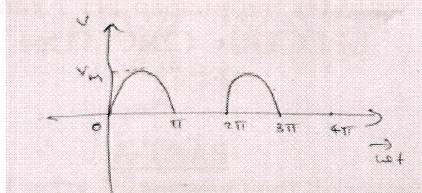- 5 a A  $50\Omega$  resistor is connected in series with a  $25\mu\text{F}$  Capacitor across a  $230\text{V}$ ,  $50\text{Hz}$  AC supply. Find capacitive reactance, impedance, Current, Phase angle, voltage drop across Capacitance and power factor. 5M
- b Find the form factor of the half wave rectified sine wave shown in figure 5M



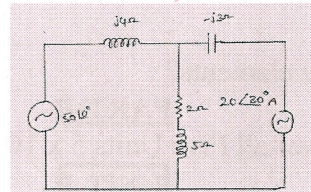**UNIT-III**


- 6 a Determine the voltage across  $(2+j5)\Omega$  impedance as shown in figure by using Superposition theorem. 5M



- b State and explain Reciprocity Theorem. 5M

OR

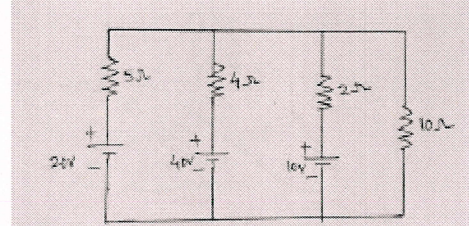- 7 a Using Millman's theorem find the current in the  $10\Omega$  resistor for the circuit shown in figure. 5M



- b State and explain Thevenin's theorem. 5M

**UNIT-IV**

- 8 a Two coils one of  $R_1=0.51\Omega$ ,  $L_1=32\text{mH}$  and other coil of  $R_2=1.3\Omega$ ,  $L_2=15\text{mH}$  are in series and are connected in series with a capacitor of  $C_1=25\mu\text{F}$ ,  $C_2=62\mu\text{F}$  and a resistor of  $R_3=0.24\Omega$ . Determine Resonant Frequency, Quality factor of the circuit, Bandwidth, and Power dissipated in the circuit at resonance frequency if the supply is  $230\text{V}$  AC supply. 6M
- b Draw the locus diagram of a series RC circuit. 4M

OR

- 9 a Obtain the expression for resonant frequency, bandwidth and Q-factor for series R-L-C circuit. 5M
- b Derive the expression for resonant frequency of a tank circuit. 5M

**UNIT-V**

- 10 Two coupled coils with  $L_1=0.02\text{H}$ ,  $L_2=0.01\text{H}$  and  $K=0.5$  are connected in four ways series aiding, series opposing, parallel aiding and parallel opposing. Determine the equivalent inductances in all the four cases. 10M

OR

- 11 a Derive the expression for MMF for a parallel magnetic circuit. 5M
- b State and explain Faraday's Laws of Electromagnetic Induction. 5M

\*\*\*END\*\*\*