

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY: PUTTUR
(AUTONOMOUS)

B. TECH I Year II Semester Supplementary Examinations Dec 2019
BASIC ELECTRICAL AND ELECTRONICS ENGINEERING
(CE, AGE)

Time: 3 hours

Max. Marks: 60

(Answer all Six Units 6 X 10 = 60 Marks)

PART- A**UNIT-I**

- 1 a State and explain Ohm's law and its limitations. 5M
b State and prove Kirchhoff law's with an example. 5M

OR

- 2 Derive an expression for RMS and Average value of sine waveform. 10M

UNIT-II

- 3 a State and Explain Thevenin's Theorem. 4M
b Find Thevenin's equivalent circuit across AB for the circuit shown in below. 6M

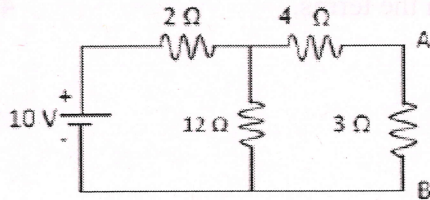
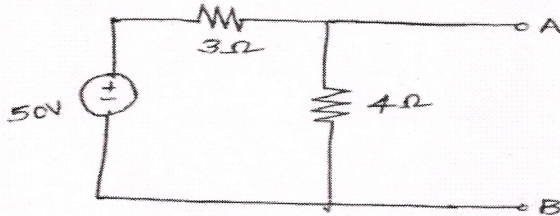


Fig. (1)

OR

- 4 a State and Explain Norton's theorem. 4M
b Find Norton's equivalent circuit across AB for the circuit shown in below. 6M

**UNIT-III**

- 5 a Explain the working principle of DC Motor in detail. 5M
b Derive Torque equation of dc motor. 5M

OR

- 6 a Explain the working principle of a transformer. 4M
b Explain OC and SC test of a single phase transformer. 6M

PART - B**UNIT-I**

- 7 a Describe the working of a PN junction diode with neat diagram. 5M
b With a neat sketch explain the V-I characteristics of the diode. 5M

OR

- 8 a With a neat sketch explain the operation of Half-wave rectifier. 5M
b Derive an expression for ripple factor of a Half-wave rectifier with and without load. 5M

UNIT-II

- 9 a What is a Transistor? 2M
b With a neat sketch explain how current flows in a transistor. 8M

OR

- 10 a Explain the working of the CB configuration of a BJT. 5M
b Derive an expression between I_b , I_c and I_e of a BJT. 5M

UNIT-III

- 11 Draw and Explain the construction of n-channel Depletion mode MOSFET. Explain how current flows through the MOSFET. 10M

OR

- 12 a With a neat sketch explain the working principle of JFET. 6M
b Write the expression for drain current of JFET and explain the terms. 4M

***** END *****