

Reg. No:

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR  
(AUTONOMOUS)  
B.TECH I Year II Semester (R16) Supplementary Examinations Dec 2017  
ELECTRICAL CIRCUITS  
(ELECTRICAL & ELECTRONICS ENGINEERING)**

Time: 3 hours

Max. Marks:60

(Answer all Five Units 5 X 12 = 60 Marks)

**UNIT-I**

- 1 a Explain circuit (or) Network elements 6M  
 b Find the current in the 5Ω resistor in the network shown in figure (1)

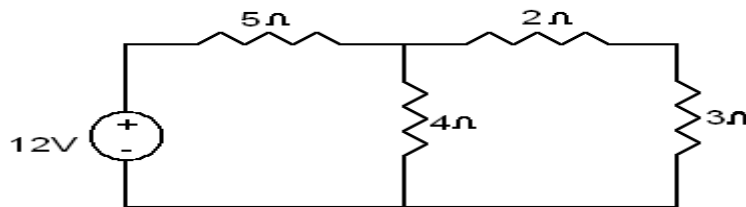


fig-1

6M

**OR**

- 2 a Derive the expression for Delta connected resistances in terms of Star connected 6M  
 b Determine the current in the 5Ω resistor in the network given in figure (2)

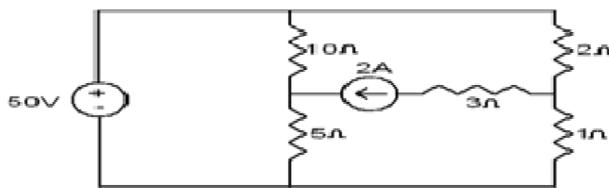


fig-2

6M

**UNIT-II**

- 3 a Find the form factor of the half wave rectified sine wave shown in fig(3)

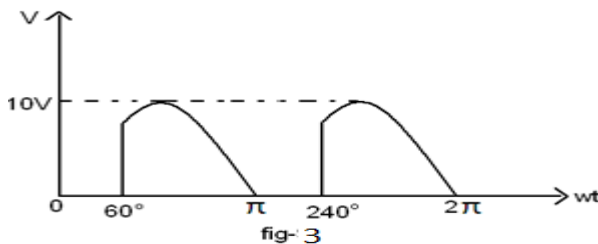


fig-3

6M

- b A Capacitor of 1μF is connected across an AC Voltage of  $V=170 \sin (400t)$ .  
 Determine (i) Capacitive Reactance 6M  
 (ii) Sinusoidal expression for current (iii) Maximum current.

**OR**

- 4 a An AC Circuit consists of a pure resistance of 20Ω and it is connected across an AC supply of 230V, 50HZ. Find (a) Current (b) Power Consumed (c) Sinusoidal equations for Voltage and Current. 6M  
 b Find the form factor for the following waveform shown in fig(4):

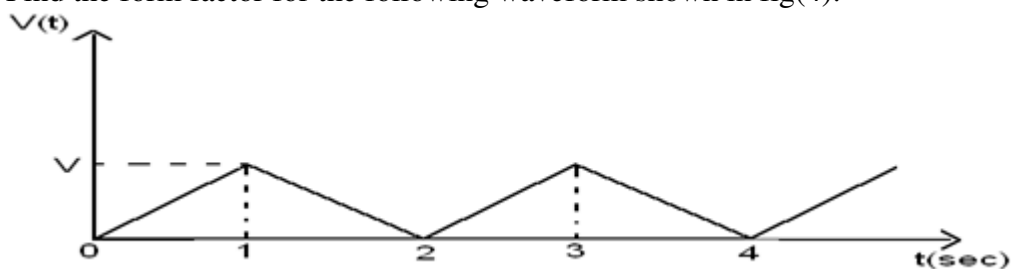


fig-4


6M

UNIT-III

- 5 a Derive the expression for the centre and radius of series RC circuit using Locus diag 6M
- b Draw the Locus diagram of a Series RC Circuit? 6M

OR

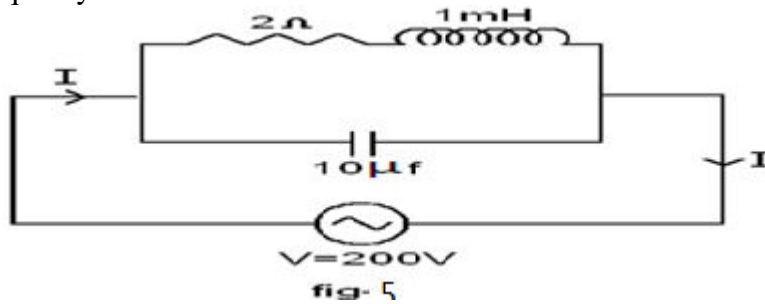- 6 a Obtain the expression for resonant frequency and Q-factor for Series R-L-C circuit 6M
- b In a parallel resonant circuit shown in figure (5) find the resonance frequency and quality factor



6M

UNIT-IV


- 7 a State and explain Faraday's Laws of Electro Magnetic Induction? 6M
- b Explain Self Inductance, Mutual Inductance and Co-efficient of coupling in detail? 6M
- Give the relation between L1, L2, K & M?

OR

- 8 a Derive the expression for equivalent inductance when the coupled inductors are connected in Parallel aiding and parallel opposition? 6M
- b explain the difference between Electrical circuits and magnetic 6M

UNIT-V

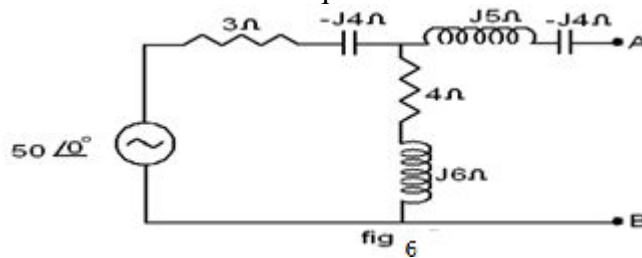
- 9 a State and explain tellegance,s theorem 6M
- b Determine the Norton's equivalent circuit for the circuit shown in figure(6)



6M

OR

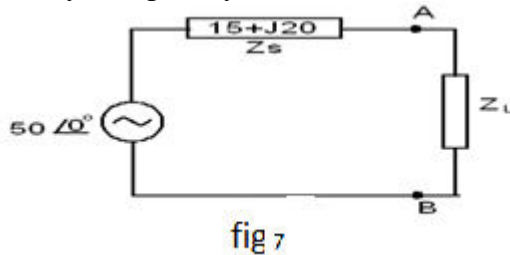- 10 a State and explain super position theorem 6M
- b Verify Reciprocity Theorem for the network shown in figure (7)



6M

\*\*\* END \*\*\*