

Reg. No.

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY::PUTTUR
(AUTONOMOUS)****M.Tech I year II Semester Regular Examinations June 2019****SWITCHED MODE AND RESONANT CONVERTERS**

(Power Electronics)

Time: 3 hours**Max. Marks:60****(Answer all Five Units 5×12=60 Marks)****UNIT I**

- 1 a Write short notes on the buck switching regulator **4M**
 b Explain the modes of operation in boost switching regulator? **8M**

OR

- 2 a Explain the basic operation of push-pull converter with necessary waveforms? **8M**
 b Write short notes on forward converter flux imbalance? **4M**

UNIT II

- 3 a Explain the half-bridge converter topology? **6M**
 b Discuss about the full-bridge magnetics? **6M**

OR

- 4 a Explain the flux-imbalance problem in bridge transformer? **6M**
 b Write short notes on current-mode control in SMPS? **6M**

UNIT III

- 5 a What is a resonant converter and Explain? **6M**
 b Explain zero voltage switching clamped voltage topologies? **6M**

OR

- 6 a Discuss about Fly back converter discontinuous mode of operation? **6M**
 b Compare the properties of voltage-fed and current-fed topologies? **6M**

UNIT IV

- 7 a Explain in detail about the basic voltage PWM controller? **6M**
 b What are the deficiencies and limitations of current mode control? **6M**

OR

- 8 a Explain Slope Compensation to Correct Problems in Current Mode control method? **6M**
 b Describe typical Current Mode PWM Control? **6M**

UNIT V

- 9 a Explain about Voltage Mode SMPS Transfer Function? **6M**
 b Explain about Radiated Emission Mechanisms in SMPS? **6M**

OR

- 10 a Discuss about Power Circuit Layout for minimum EMI in SMPS? **6M**
 b Write a brief note on Effect of EMI Filter on SMPS Control? **6M**

*****END*****