

Reg. No:

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

M.Tech I Year I Semester Regular Examinations January 2020

ADVANCED POWER ELECTRONIC CIRCUITS

(Power Electronics)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

1 Draw and explain the operation of 1- ϕ capacitor commutated CSI with R-load. 12M

OR

2 Draw and explain the operation of three-phase series-inverter. 12M

UNIT-II

3 Explain the operation of three phase boost type APFC switched mode rectifier. 12M

OR

4 Explain about DC-clamped switched mode rectifier. 12M

UNIT-III

5 Explain the principle and operation of the Buck-Boost converter. 12M

OR

6 Classify the converters based on various aspects. 12M

UNIT-IV

7 a Explain the circuit diagram of a double ended forward converter. 6M

b Compare fly back converter and forward converter. 6M

OR

8 Explain the modes of operation of full-bridge converter. 12M

UNIT-V

9 a Explain the L-type ZCS resonant converter with various modes of operations and wave forms. 6M

b Compare ZCS and ZVS resonant converters. 6M

OR

10 Explain the operation of ZVS resonant converter with the help of circuit diagram. 12M

*** END ***