

Reg. No:

--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

M.Tech I Year I Semester (R16) Regular Examinations January 2017
DIGITAL IC DESIGN

(VLSI)

(For Students admitted in 2016 only)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units **5 X 12 =60** Marks)

UNIT-I

- Q.1** a Give the advantages of dynamic logic over static CMOS logic? 7M
 b With a neat sketch explain the circuit topology and operation of CMOS domino logic 5M

OR

- Q.2** a How does the domino logic solves the dynamic logic problem? 4M
 b How is dynamic CMOS circuits faster than static CMOS circuits? 8M

UNIT-II

- Q.3** a Draw the schematic diagram of a SRAM memory cell along with sense amplifier and data write circuitry and explain. 6M
 b Explain the logical effort of two – input NAND and NOR gates with neat circuit diagram 6M

OR

- Q.4** a What are the design considerations of a 4 bit RAM with the help of CMOS logic diagram. 5M
 b Draw one cell dynamic RAM circuit and explain its working. 7M

UNIT-III

- Q.5** a Elaborate on delay and power consumption in BiCMOS logic circuits. 6M
 b What are the advantages and disadvantages of BiCMOS 6M

OR

- Q.6** a Explain in detail about bipolar gate design with neat sketches. 7M
 b Give the schematic diagram of different Bi-CMOS inverters. Explain its operation 5M

UNIT-IV

- Q.7** a Explain: (i) Area capacitance. 6M
 b What is the need of wired capacitance? Where it is used? Explain. 6M

OR

- Q.8** a Explain two input NAND gate with relevant Layout example. 7M
 b How do you determine the capacitance of a MOS capacitor 5M

UNIT-V

- Q.9** a Analyze the timing of the array multiplier and explain. 7M
 b With a neat sketch explain the working of array multiplier 5M

OR

- Q.10** a What are the design approach of 4 bit shifter 5M
 b Draw and explain the booth decode cell used for booth multiplier 7M

*** END ***