

Reg. No:

|  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR  
(AUTONOMOUS)

B.Tech II Year I Semester Regular Examinations November 2019

DIGITAL LOGIC DESIGN

(CSE)

Time: 3 hours

Max. Marks: 60

**PART-A**

(Answer all the Questions 5 x 2 = 10 Marks)

- 1 a State the associative property of Boolean algebra. 2M
- b What are the 2 forms of Boolean expression? 2M
- c Differentiate between encoder and decoder. 2M
- d What is state diagram? 2M
- e What are BIT, BYTE and WORD? 2M

**PART-B**

(Answer all Five Units 5 x 10 = 50 Marks)

**UNIT-I**

- 2 a Represent the decimal number 3452 in i)BCD ii)Excess-3. 5M
- b Perform (-50)-(-10) in binary using the signed-2's complement. 5M

OR

- 3 a Explain binary to Gray & Gray to binary conversion with example. 5M
- b State and Explain the DeMorgan's Theorem and Consensus Theorem. 5M

**UNIT-II**

- 4 Simplify the Boolean expressions to minimum number of literals 10M
  - i)  $(A + B)(A + C')(B' + C')$
  - ii)  $AB + (AC)' + AB'C (AB + C)$
  - iii)  $(A+B)' (A'+B)'$

OR

- 5 Determine the minimal sum of product form of 10M
  - i)  $f(w,x,y,z)=\sum m(4,5,7,12,14,15) +d(3,8,10)$ .
  - ii)  $F(A,B,C,D)=\pi M(0,3,5,6,8,12,15)$ .

**UNIT-III**

- 6 a Implement the following Boolean function using 8:1 multiplexer 5M
 
$$F(A,B,C,D) = \sum m(0,1,2,5,7,8,9,14,15)$$
- b Explain about Decimal Adder. 5M

OR

- 7 Explain The Half adder and implement the full adder using two half adders. 10M

**UNIT-IV**

- 8 Explain the design of a 4-bit binary counter with parallel load in detail. 10M

OR

- 9 a Explain synchronous and ripple counters compare their merits and demerits. 5M
- b Design a 4-bit binary synchronous counter with D-flip flop. 5M

**UNIT-V**

- 10 Encode the 11-bit code 10111011101 into 15-bit information code. 10M

OR

- 11 Design PAL for a combinational circuit that squares a 3-bit number. 10M

\*\*\*END\*\*\*