

Reg. No:

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)**

B.Tech II Year I Semester Regular Examinations Nov/Dec 2019

NETWORK THEORY

(Electronics & Communication Engineering)

Time: 3 hours

Max. Marks: 60

PART-A

(Answer all the Questions **5 x 2 = 10** Marks)


- | | | |
|----------|--|-----------|
| 1 | a Define Super node and Super mesh. | 2M |
| | b Define Quality-factor and Selectivity. | 2M |
| | c What is the behavior of Capacitor in Initial and Steady state conditions? | 2M |
| | d What is the condition for Reciprocity in Z and Y parameters? | 2M |
| | e Write the expression for trigonometric form of Fourier series. | 2M |

PART-B

(Answer all Five Units **5 x 10 = 50** Marks)


UNIT-I

- | | | |
|----------|--|-----------|
| 2 | a State and prove Maximum power transfer theorem. | 5M |
| | b Calculate the current 'I' shown in below figure by using Millman's theorem. | |

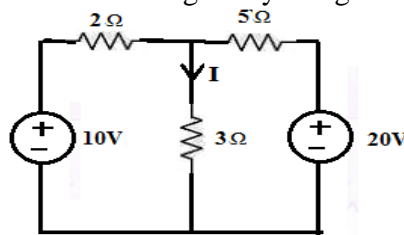

OR

- | | | |
|----------|--|-----------|
| 3 | a Explain about Nodal analysis and write the steps for applying nodal analysis. | 5M |
| | b Determine the mesh currents for the following network. | |

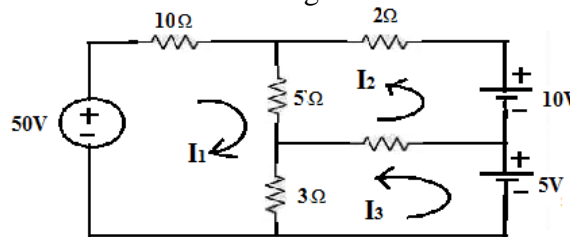


UNIT-II

- | | | |
|-----------|--|-----------|
| 4 | a A series RLC circuit has $R=10\Omega$, $L=0.1H$ and $C=50\mu F$. The applied voltage is 100V. Find Resonant frequency & Quality factor of a coil. | 5M |
| | b Explain about Series resonance with phasor diagrams. | 5M |
| OR | | |
| 5 | a Explain about Propagation constant and Characteristic impedance in Π -network filters. | 5M |
| | b Design Low Pass Filter in both T & Π section having a cut off frequency of 2KHz to operate with a terminated load resistance of 500 Ω . | 5M |

UNIT-III

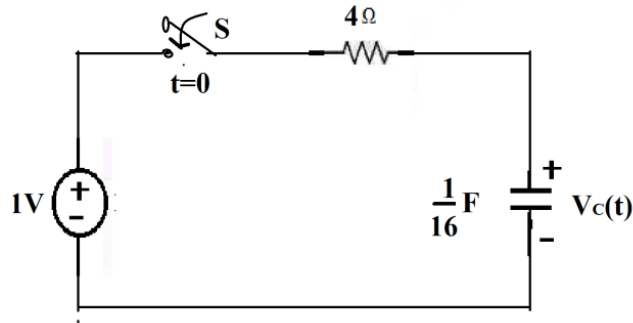- 6 a Derive the Transient Response of series RL-circuit with D.C excitation. 5M
 b Using classical method of solution of differential equations, find the value of $V_c(t)$ for $t > 0$ in the circuit shown in figure. Assume $V_c(0^-) = 9v$.




5M

OR

- 7 Derive the Transient Response of Series RL circuit with Sinusoidal excitation. 10M

UNIT-IV

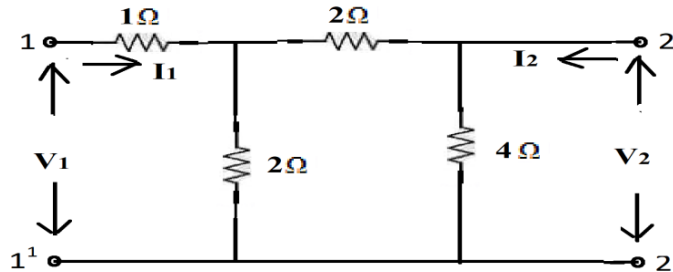- 8 a Explain about short-circuit parameters. 6M
 b Find the h-parameters of the network shown in figure





4M

OR

- 9 a Derive the expressions for Chain parameters in terms of Z-parameters. 5M
 b The Z-parameters of a two-port network are $Z_{11} = 10\Omega$, $Z_{22} = 15\Omega$, $Z_{12} = 5\Omega$ and $Z_{21} = 5\Omega$. Find the equivalent T-network and ABCD parameters. 5M

UNIT-V

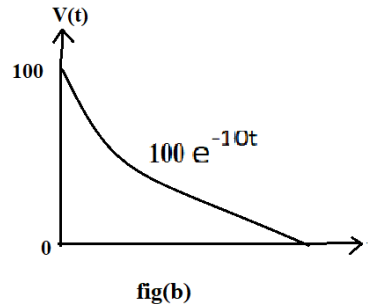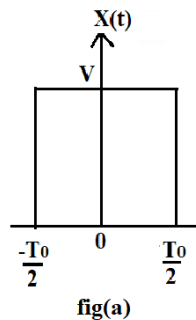- 10 Write and prove the properties of Fourier transforms. 10M
 OR
 11 Determine the Fourier transforms of the following waveforms shown in Figure (a) and Figure (b).



10M

END