

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR

(AUTONOMOUS)

B.Tech II Year I Semester Supplementary Examinations Nov/Dec 2019**SWITCHING THEORY AND LOGIC DESIGN****(Electronics & Communication Engineering)**

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a Reduce the following Boolean expressions using Boolean algebra. **6M**
 i) $(X'Y'+Z)+Z+XY+WZ$
 ii) $A'B(D'+C'D)+B(A+A'CD)$
 iii) $(A'+C)(A'+C')(A+B+C'D)$
 b Convert the given decimal number 351 to binary, octal, hexadecimal and BCD equivalent. **6M**

OR

- 2 a State Duality theorem. List the Boolean laws and their Duals. **6M**
 b Solve for x **6M**
 i) $(257)_8 = (x)_2$
 ii) $(BC2)_{16} = (x)_8$
 iii) $(33)_{10} = (201)_x$

UNIT-II

- 3 a Simplify the Boolean function $F(A,B,C,D)=\sum(1, 3, 7, 11, 15)+d(0, 2, 5)$ using map method. **6M**
 b Implement the given Boolean function $Y= (AB'+A'B)(C+D')$ using NOR gates only. **6M**

OR

- 4 Simplify the following Boolean function using Tabulation method. **12M**
 $Y(A,B,C,D) = \Sigma(1,3,5,8,9,11,15)$

UNIT-III

- 5 a Explain Carry Look Ahead Adder circuit with the help of logic diagram **8M**
 b Realize a 2-bit comparator using logic gates. **4M**

OR

- 6 a What is encoder? Design octal to binary encoder. **6M**
 b Design a 16 line to 1 line multiplexer using 4 line to 1 line multiplexer. **6M**

UNIT-IV

- 7 a Design D Flip Flop by using SR Flip Flop and draw the timing diagram **6M**
 b Write the differences between combinational and sequential circuits. **6M**

OR

- 8 a With a neat sketch explain MOD 6 Johnson counter using D Flip-flop. **6M**
 b What is race around problem in JK Flip-Flop? Explain how it is eliminated in master slave JK Flop-Flop. **6M**

UNIT-V

- 9 a** Implement the following Boolean function using PLA. **8M**
(i) $F(w,x,y,z) = \Sigma m(0,1,3,5,9,13)$
(ii) $F(w,x,y,z) = \Sigma m(0,2,4,5,7,9,11,15)$
- b** Explain about memory decoding. **4M**
- OR**
- 10 a** Given the 4-bit data word 1101, generate the composite word for the hamming code that corrects and detects single errors. **6M**
- b** Differentiate among ROM, PROM, DROM , EPROM, EEPROM, RAM. **6M**

*** END ***