

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)
B.TECH II Year II Semester (R16) Supplementary Examinations December 2018
ELECTRONIC CIRCUIT ANALYSIS
(ECE)


Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 X 12 = 60 Marks)

UNIT-I

- 1 a A voltage source of internal resistance $R_s = 900\Omega$ drives a CC amplifier using load resistance $R_L = 2000\Omega$. The CE h parameter are $h_{fe} = 60$, $h_{ie} = 1.2k$, $h_{oe} = 25\mu A/V$ and $h_{re} = 2 \times 10^{-4}$. Compute A_i , R_i , A_v and R_o using approximate analysis 8M
 b Compare the transistor amplifier parameters for CE, CB and CC configurations. 4M
- OR**
- 2 a Derive input impedance, output impedance and voltage gain of JFET Common Source amplifier with voltage divider bias for bypassed R_s . 6M
 b For the circuit shown in Fig. determine input impedance, voltage gain, output impedance Z_o and Z_o' . Assume for FET $g_m = 2mA/V$, $r_d = 10k\Omega$. 6M

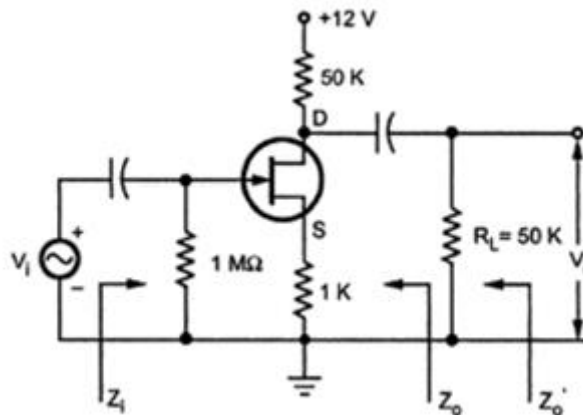

UNIT-II

- 3 Derive the expression for CE Short circuit current gain with the help of necessary circuit diagrams and approximations. 12M
- OR**
- 4 Derive the expression for Current gain with R_L and explain the variation of frequency response with R_L . 12M

UNIT-III

- 5 Describe different methods used for coupling multistage amplifiers with their frequency response. 12M
- OR**
- 6 a Draw the block diagram of n-stage cascaded amplifier and analyze its various parameters. 10M
 b List the classification of amplifiers. 2M

UNIT-IV

- 7 a A voltage series negative feedback amplifier has a voltage gain without feedback of $A = 500$, input resistance $R_i = 3k\Omega$, output resistance $R_o = 20k\Omega$ and feedback ratio $\beta = 0.01$. Calculate the voltage gain A_f , input resistance R_{if} , and output resistance R_{of} of the amplifier with feedback. 8M
 b Classify the different types of oscillators. 4M

OR

- 8 a Determine the input and output resistances of Current Series feedback amplifier. 6M
b Explain Feedback topologies. 6M

UNIT-V

- 9 a Discuss Double Tuned Amplifier with neat diagram and derive the expression for its bandwidth. 6M
b With neat diagram explain Series fed, Directly coupled Class A Power Amplifier and derive its maximum efficiency. 6M

OR

- 10 A class B push pull amplifier supplies power to a resistive load of 12Ω . The output transformer has a turns ratio of 3:1 and efficiency of 78.5%. Obtain
(i) Maximum power output,
(ii) Maximum power dissipation in each transistor and
(iii) Maximum base and collector current
For each transistor. Assume $h_{fe} = 25$ and $V_{CC} = 20V$. 12M

***** END *****