

**Reg. No:**

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR**  
(AUTONOMOUS)

**BTECH II Year I Semester Supplementary Examinations June 2019**

**SWITCHING THEORY AND LOGIC DESIGN**

(Electronics & Communication Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units **5 x 12 = 60** Marks)

**UNIT-I**

- 1 a** Perform the following using BCD arithmetic 6M  
 (i)  $(79)_{10} + (177)_{10}$  (ii)  $(481)_{10} + (178)_{10}$   
**b** Subtraction by using 2's complement for the given 6M  
 i) 111001-1010 ii) 10011-10001 iii) 1001-101000
- OR**
- 2 a** State Duality theorem. List Boolean laws and their Duals. 6M  
**b** Give the truth table of logic gates. 6M

**UNIT-II**

- 3** Minimize the given Boolean function  $F(A, B, C, D) = \sum m(0, 1, 2, 3, 6, 7, 13, 15)$  using tabulation method and implement using basic gates. 12M
- OR**
- 4** Simplify the following Boolean function for minimal SOP & POS form using K-map 12M  
 i)  $F(A, B, C, D) = \sum (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$   
 ii)  $F(A, B, C, D) = \pi(1, 3, 6, 9, 11, 12, 14)$

**UNIT-III**

- 5 a** Design & implement BCD to Excess-3 code converter. 6M  
**b** Design & implement 4-bit Binary Adder-subtractor. 6M
- OR**
- 6 a** What is Decoder? Design three to eight-line Decoder. 6M  
**b** Design & implement BCD To seven segment decoder. 6M

**UNIT-IV**

- 7 a** a) Draw the logic symbol, characteristics table and derive characteristics equation of JK flip flop. 6M  
**b** b) Design T Flip Flop by using JK Flip Flop and draw the timing diagram. 6M
- OR**
- 8 a** Implement 6-bit ring counter using suitable shift register. Briefly describe its operation. 10M  
**b** Write the difference between Latch and Flip flop 2M

**UNIT-V**

- 9** Implement the following Boolean function using PLA 12M  
 (i)  $F1 = \sum m(0, 1, 2, 3, 8, 10, 12, 14)$  (ii)  $F2 = \sum m(0, 1, 2, 3, 4, 6, 8, 10, 12, 14)$
- OR**
- 10** Give the logic implementation of a 32x4 bit ROM using a decoder with necessary diagram. 12M

\*\*\* END \*\*\*