

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)**

**B.Tech II Year II Semester (R16) Regular & Supplementary Examinations May 2019
ELECTRONIC CIRCUIT ANALYSIS**

Time: 3 hours

Max. Marks:60

(Answer all Five Units $5 \times 12 = 60$ Marks)

UNIT-I

- 1 Using low frequency h-parameter model, derive the expressions for voltage gain, current gain, input impedance and output admittance for a BJT Amplifier in CE configuration. 12M

OR

- 2 a Compare the transistor amplifier parameters for CE, CB and CC configurations. 5M
 b Determine Voltage Gain, Current Gain, Input resistance and Output resistance for a CE amplifier using NPN transistor with $h_{ie} = 1200\Omega$, $h_{re} = 0$, $h_{fe} = 36$ and $h_{oe} = 2 \times 10^{-6}$ mhos, $R_L = 2.5k\Omega$ and $R_S = 500\Omega$ (neglect the effect of biasing circuit). 7M

UNIT-II

- 3 a Draw the Hybrid-pi model and explain the significance of each and every component in it. 6M
 b Derive the expression for Hybrid- π capacitance of CE transistor at high frequency. 6M

OR

- 4 With the help of necessary circuit diagrams and approximations obtain the expression for CE Short circuit current gain and derive the relation between f_B and f_T . 12M

UNIT-III

- 5 a Describe different methods used for coupling multistage amplifiers with their frequency response. 10M
 b List the classification of amplifiers. 2M

OR

- 6 a What is Darlington Connection? Mention the advantages of Darlington Pair Amplifier. 4M
 b With diagram, derive the expression for current gain and input resistance of Darlington amplifier. 8M

UNIT-IV

- 7 Explain the characteristics of negative feedback amplifiers. 12M

OR

- 8 a Derive the expression for frequency of oscillations for RC phase shift Oscillator. 6M
 b Discuss the working principle of Wein bridge oscillator and derive the expression for frequency of oscillations. 6M

UNIT-V

- 9 a Discuss with diagram, Transformer coupled Class A Power Amplifier and derive its Maximum efficiency. 6M
 b Explain second harmonic distortion by three point method. 6M

OR

- 10 a Compare Single Tuned and Double Tuned Amplifier. 2M
 b Describe the operation of a single tuned capacitive coupled amplifier with diagram and derive the expression for its centre frequency, Quality factor, Voltage gain and bandwidth. 10M

*** END ***