

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech III Year I Semester Regular & Supplementary Examinations Nov/Dec 2019
ELECTRONIC MEASUREMENTS AND INSTRUMENTATION
(Electronics & Communication Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a** Explain the construction of multi-range voltmeter & Range extension DC voltmeter. **7M**
b A D'Arsonval movement with a full scale deflection current of 50 μ A and internal resistance of 500 Ω is to be converted into a multirange voltmeter. Define the value of multiplier required for 0-20v, 0-50v, 0-100v. **5M**

OR

- 2 a** Define following characteristics i) Accuracy ii) Resolution iii) sensitivity **6M**
b Discuss about basic DC Ammeters. **6M**

UNIT-II

- 3 a** Explain the major parts of CRT with a block diagram. **6M**
b Compare dual trace oscilloscopes and dual beam CRO. **6M**

OR

- 4 a** Describe in details the construction and working of an analog type storage oscilloscope. **6M**
b Explain with the block diagram how the digital frequency can be measured using counter/meter instrument. **6M**

UNIT-III

- 5 a** With help of a neat sketch, explain the working of a frequency selective wave analyzer. **6M**
b With a neat sketch explain the operation of Spectrum analyzer. **6M**

OR

- 6 a** List the application of wave analyzers. **4M**
b Draw the block diagram of a function generator and explain its operation. **8M**

UNIT-IV

- 7 a** Explain any Two ac bridges to measure unknown inductance. **8M**
b Distinguish between AC Bridges and DC bridges. **4M**

OR

- 8 a** Explain Anderson's bridge. **6M**
b What is interference & explain noise reduction techniques. **6M**

UNIT-V

- 9 a** Explain the operation of LVDT. **6M**
b Describe the operation of capacitive transducers. **6M**

OR

- 10 a** Write short notes on i) Inductive transducers. ii) Thermocouple. **6M**
b Discuss the signal conditioning circuits. **6M**

*** END ***