

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR

(AUTONOMOUS)

B.Tech III Year II Semester Supplementary Examinations Dec 2019

ELECTRICAL AND ELECTRONIC MEASUREMENTS

(Electrical & Electronics Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a With neat sketch explain the working of PMMC instrument. Derive the torque equation of PMMC instrument. 6M
- b A MC instrument gives a full scale deflection of 10 mA when the potential difference across its terminals is 100 mV. Calculate the shunt resistance for a full scale deflection corresponding to 100 A and the series resistance for full scale reading with 1000 V. Calculate the power dissipation in each case. 6M

OR

- 2 a Discuss about various types of errors and compensations of measuring instruments. 6M
- b A 10 A electro-dynamometer is controlled by a spring having a torsion constant of 0.1×10^{-6} N-m/degree. The full scale deflection is 110° . Determine the inductance of the instrument when measuring a current of 10 A. The mutual inductance at 0° deflection is $2 \mu\text{H}$. 6M

UNIT-II

- 3 a The value of high resistance is measured by loss of charge method. A capacitor having a capacitance of $2.5 \mu\text{F}$ is charged to a potential of 500 V DC and is discharged through the high resistance. An electrostatic voltmeter kept across the high resistance, reads the voltage as 300 V at the end of 60 sec. Calculate high value of resistance. 6M
- b Classify the different types of DC bridges based on resistance value and explain the Wheatstone bridge for the unknown value of resistance with neat sketch. 6M

OR

- 4 a Explain the working of Maxwell's inductance and capacitance bridge for measurement of inductance with a circuit diagram. Derive the equations under balanced conditions and draw its phasor diagram. 6M
- b With the help of circuit diagram determine the unknown capacitance using Schering bridge under balanced condition and draw its phasor diagram. 6M

UNIT-III

- 5 a Discuss the errors and their compensations in the dynamometer type wattmeter. 6M
- b A wattmeter has a current coil of 0.03Ω resistance and a pressure coil of 6000Ω resistance. Calculate the percentage error
- (i) if the wattmeter current coil is connected on the load side;
- (ii) if the wattmeter pressure coil is connected on the load side.
- (a) If the load takes 20 A at a voltage of 220 V and 0.6 p.f in each case;
- (b) At which load current will give equal errors with the two connections? 6M

OR

- 6 a With neat sketch explain construction and working of a single phase induction type energy meter. 6M
- b Discuss the errors and compensations in Energy meters. 6M

UNIT-IV

- 7 a Describe with the help of suitable diagrams how a DC potentiometer is used for the measurement of unknown resistance and unknown current? 6M
- b A Crompton's potentiometer consists of a resistance dial having 15 steps of $10\ \Omega$ each and a series connected slide wire of $10\ \Omega$ which is divided into 100 divisions. If the working current of the potentiometer is $10\ \text{mA}$ and each division of slide wire can be read accurately up to $1/5$ of its span. Calculate the resolution of the potentiometer in volts. 6M
- OR**
- 8 a Derive the expression for ratio error and phase angle error of CT. 6M
- b Explain the construction, operation & characteristics of potential transformer 6M

UNIT-V

- 9 a Derive equation of motion of Ballistic galvanometer. 6M
- b A ballistic galvanometer has a free period of 10 seconds and gives a steady deflection of 200 divisions with a steady current of $0.1\ \text{mA}$ and a charge of $121\ \mu\text{C}$ is instantaneously discharged through the galvanometer giving rise to a first maximum deflection of 100 divisions. Calculate the decrement of the resulting oscillations. 6M
- OR**
- 10 a With the help of neat sketch explain the working of each block in CRO. 6M
- b Explain the working of digital meters with neat sketch. 6M

*** END ***