

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

M.Tech II Year I Semester Regular Examinations January 2021

HVDC TRANSMISSION SYSTEMS

(Power Electronics)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a Give the comparison between AC and DC Transmission and explain the factors in detail. **6M**
b What are the applications of DC Transmission and also mention the modern trends in HVDC technology? **6M**

OR

- 2 a Explain the line commutated converter based systems. **6M**
b Explain the basic conversion principles with neat circuit diagrams. **6M**

UNIT-II

- 3 a Explain the rectifier and inverter operation of a power converter and also write the equivalent circuit of converter. **6M**
b Derive the expressions for average dc voltage, AC current and reactive power absorbed by the converter. **6M**

OR

- 4 a Explain the Effect of Commutation Failure, Misfire and Current Extinction in LCC links. **6M**
b Explain the Sinusoidal Pulse Width Modulation. **6M**

UNIT-III

- 5 a Explain the Principles of Link Control in a LCC HVDC system. **6M**
b Give detailed explanation of about two firing angle controls. **6M**

OR

- 6 a Explain Higher level Controllers Power control, Frequency Control. **6M**
b Explain the Stability Controllers, Reactive Power Control. **6M**

UNIT-IV

- 7 a What is meant by DC Power modulation? Explain it in detail? **6M**
b Briefly explain what are the different harmonic instability problems? **6M**

OR

- 8 a Explain the DC power modulation scheme used in interconnected operations of AC and DC Systems. **6M**
b Explain the interaction between HVAC & DC systems. **6M**

UNIT-V

- 9 a List out different types of multi-terminal DC links with suitable diagrams. **6M**
b Explain parallel connected multi terminal DC link with suitable diagram. **6M**

OR

- 10 a Explain series parallel connected multi terminal DC link with suitable diagram. **6M**
b Explain series connected multi terminal DC link with suitable diagram. **6M**

*** END ***