

Reg. No: 

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR****(AUTONOMOUS)****B.Tech III Year II Semester Supplementary Examinations March-2021****DIGITAL IC APPLICATIONS****(Electronics and Communication Engineering)**

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

**UNIT-I**

- 1 a Draw the circuit diagram of basic CMOS gate and explain its operation. 6M  
 b Compare CMOS, TTL and ECL logic families. 6M

**OR**

- 2 a Design a 4-input CMOS AND-OR-INVERTER gate. Draw the logic diagram and functional table. 6M  
 b Explain the following terms with reference to TTL gate  
 i) D.C noise margin ii) Logic levels 6M

**UNIT-II**

- 3 a Explain the various data types supported by VHDL. Give the necessary examples. 6M  
 b Explain about VHDL program structure. 6M

**OR**

- 4 a Write about structural design elements with an example. 6M  
 b Write a VHDL entity and Architecture for the following function.  $F(x) = (a + b)(c + d)$   
 Also draw the relevant logic diagram. 6M

**UNIT-III**

- 5 a Design a 4 to 16 decoder with 74x138 IC's. 6M  
 b Write a VHDL program for the above design. 6M

**OR**

- 6 a Design a priority encoder that can handle 32 requests. Use 74x148 and required discrete gates. Provide the truth table and explain the operation. 8M  
 b Draw the logic symbol of 74 x 85, 4-bit comparator. 4M

**UNIT-IV**

- 7 a Design an 8 bit parallel in and serial out shift register and explain its operation with the timing waveforms. 8M  
 b Draw the logic diagram of IC 74194. 4M

**OR**

- 8 a Design a bit LFSR counter using 74x194. List out the sequence assuming that the initial state is 111. 6M  
 b Write a VHDL code for the LFSR counter using 74x194. 6M

**UNIT-V**

- 9 a Design a 8-bit barrel shifter using three control inputs. 6M  
 b Write a VHDL program for the same in data flow style. 6M

**OR**

- 10 a Distinguish between latch and flip flop. Show the logic diagram for both. 6M  
 b Explain the operation with the help of function table for latch and flip flop. 6M

\*\*\* END \*\*\*