

Reg. No: 

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING &amp; TECHNOLOGY:: PUTTUR

(AUTONOMOUS)

B Tech I Year II Semester Supplementary Examinations October-2020

NETWORK ANALYSIS

(Electronics and communication Engineering)


Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

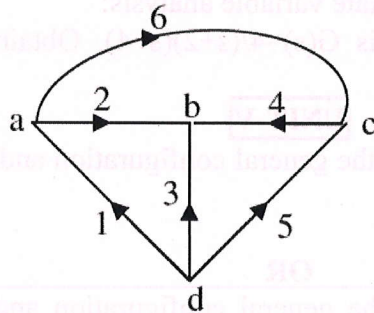
**UNIT-I**

- 1 a 1. Define the following terms 4M  
 (i) Branch (ii) Sub graph (iii) Node (iii) Tree & co-tree
- b For the graph shown below find incidence and cut set matrices. 8M



OR

- 2 a What is the condition for maximum power transfer to the load? 4M  
 b Find Thevenin's equivalent for the following circuit. 8M

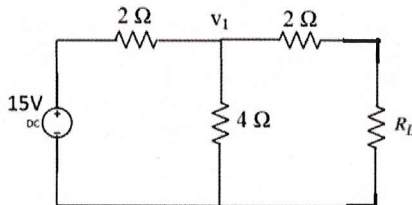**UNIT-II**

- 3 a Define i) admittance, ii) impedance, iii) phase difference, iv) power factor 4M  
 b A parallel RLC circuit is supplied with a voltage source of 230 V, 50Hz. Determine circuit current and power factor if  $R=40\Omega$ ,  $L=0.2H$  and  $C=50\mu F$ . 8M

OR

- 4 a What is time constant? What are the time constants of series RL and RC circuits? 4M  
 b Deduce the transient response source free series RC circuit. 8M

**UNIT-III**


- 5 a Obtain the expression for resonant frequency, bandwidth and Q-factor for parallel R-L-C circuit. 5M  
 b In a parallel resonance circuit (Tank circuit)  $R=2\Omega$ ,  $L=1mH$  and  $C=10\mu F$ , Find the Resonant frequency, Dynamic impedance and Bandwidth. 7M

OR

- 6 a Explain about dot convention in mutually coupled circuits: 5M  
 b Show that the resonant frequency circuit  $f_r^2 = f_1 f_2$  where  $f_1$  and  $f_2$  are the half power frequencies and  $f_r$  is the resonant frequency. 7M
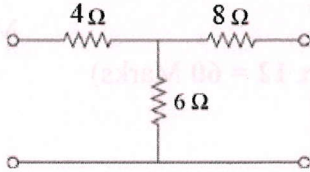
## UNIT-IV

- 7 a Mention the condition for symmetry and reciprocity for z-parameters: 6M  
 b Find the h- parameters for the following circuit. 6M



OR

- 8 a What are the merits and demerits of state variable analysis: 4M  
 b The transfer function of a system is  $G(s) = 4/(s+2)(s+4)$ . Obtain a state variable representation for the system. 8M

## UNIT-V

- 9 a What is an m-derived filter? Explain the general configuration and parameters of m-derived low pass filter. 10M  
 b Define filter: 2M

OR

- 10 a What is high pass filter? Explain the general configuration and parameters of a constant-K-high pass filter. 10M  
 b Mention the properties of band pass filters: 2M

\*\*\* END \*\*\*