

Reg. No:

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)**

**B.Tech I Year II Semester Supplementary Examinations March-2021
BASIC ELECTRICAL AND ELECTRONICS ENGINEERING
(Common to CE & AGE)**

Time: 3 hours

Max. Marks: 60

(Answer all Six Units 6 X 10 = 60 Marks)

PART-A**UNIT-I**


- 1 a Define RMS value, average value, form factor and peak factor. 5M
 b Show the form factor of the sine current is 1.11./ Find form factor of the sine Current. 5M

OR


- 2 a Explain about basic circuit components in detail. 5M
 b Explain about KVL. 5M

UNIT-II

- 3 Determine the maximum power delivered to the load in the circuit shown in fig 10M

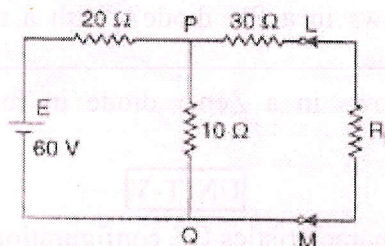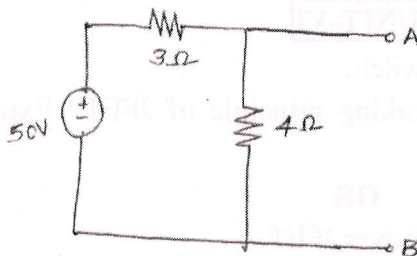**OR**

- 4 a Find Thevenin's equivalent circuit across AB for the circuit shown in below 5M



- b The given Y-parameters are $Y_{11}=0.5$, $Y_{12}=Y_{21}=0.6$, $Y_{22}=0.9$. Find impedance. 5M

UNIT-III

- 5 a Calculate the value of Torque established by the armature of a 4-pole motor having 774 conductors, 2 paths in parallel, 24 mwb flux per pole when the total armature current is 50A. 5M
- b Derive Torque equation of dc motor. 5M

OR

- 6 a Explain principle of operation of transformer. 5M
- b An ideal transformer has 1000 turns on its primary and 500 turns on its secondary the driving voltage of primary side is 100V and the load resistance is $5\ \Omega$, calculate V_2 , I_1 and I_2 ? 5M

PART-B**UNIT-IV**

- 7 a Explain the importance of filters in voltage regulators with necessary expressions? 5M
- b Explain the following with an example 5M
- i) Atom ii) Ion iii) Ohms law

OR

- 8 a Explain how current flows in a PN diode? With a neat sketch explain the VI characteristics of the diode. 5M
- b Explain how current flows in a Zener diode in reverse bias with necessary diagrams. 5M

UNIT-V

- 9 a Draw input and output characteristics CE configuration. Explain the Operation of CE transistor with necessary expressions. 5M
- b Explain the following terms 5M
- i) Biasing ii) Early effect iii) Q-point iv) Transportation factor

OR

- 10 a With a neat sketch? Explain the construction and working principle of NPN transistor. 5M
- b Explain Emitter follower with necessary expression. 5M

UNIT-VI

- 11 a Discuss how a MOSFET acts as a Switch. 5M
- b With a neat sketch explain the working principle of JFET? Explain how the current flows in a JFET. 5M

OR

- 12 a Discuss the Advantages of MOSFET over JFET. 5M
- b Write the expression for drain current of a MOSFET and explain the terms. 5M

***** END *****