

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech III Year I Semester Supplementary Examinations November-2020

SWITCHING THEORY AND LOGIC DESIGN

(Electrical & Electronics Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a** Convert the following numbers. **6M**
- i) $(6153.7406)_8$ to binary.
- ii) Convert $(A3C2.D)_{16}$ to binary and then to Octal.
- iii) $(1032.2)_6$ to decimal.
- b** i) Convert gray code 1010011011 into its binary equivalent. **6M**
- ii) Use 2's complement to perform $M - N$ with the given number $M=101010100$
 $N=100000100$.

OR

- 2 a** Express the function $Y=A+B'C$ in canonical SOP form. **4M**
- b** Prove the following using Boolean algebra **8M**
- i) $y'z' + w'x'z' + w'xyz' + wyz' = z'$
- ii) $ABC + A'B'C + A'BC + ABC' + A'B'C' = A'B' + B(A + C)$

UNIT-II

- 3 a** Simplify the Boolean function using K-map **8M**
- i) $F(W,X,Y,Z) = \sum_m(4, 5, 7, 12, 13, 14) + \sum_d(1, 9, 11, 15)$
- ii) $F(W, X, Y, Z) = W'X'Y'Z' + WXY'Z' + W'X'YZ + WXYZ$
- b** Explain about EX-OR gate functions. **4M**

OR

- 4 a** Simplify the Boolean function by using tabulation method **8M**
- $F(A,B,C,D) = \sum_m(0,1,2,5,6,7,8,9,10,14)$
- b** Implement the AND and OR gates by using NAND gates only. **4M**

UNIT-III

- 5 a** Design and Implement Half adder and Full Adder with truth tables. **6M**
- b** Draw and explain the operation of 2×2 binary multiplier. **6M**

OR

- 6 a** Implement the following Boolean function using 4:1 Multiplexer **6M**
- $F(A,B,C,D) = \sum_m(0,1,2,4,6,9,12,14)$.
- b** Design and Implement 3 to 8 Decoder with its truth table. **6M**

UNIT-IV

- 7 a** Convert SR Flip-Flop to JK Flip-Flop. **6M**
- b** Implement 4-bit ring counter using suitable shift register. Briefly describe its operation. **6M**

OR

- 8 a** Explain and design asynchronous MOD10 counter using T-Flip-flops. **6M**
b What is a shift register? Explain about the following modes of operation in a four bit shift register. (i) Shift right (ii) Shift left and (iii) bidirectional. **6M**

UNIT-V

- 9 a** Implement the following Boolean function using PLA. **6M**
 $F1(w,x,y,z) = \Sigma m(0,1,3,5,9,13)$
 $F2(w,x,y,z) = \Sigma m(0,2,4,5,7,9,11,15)$
b Explain the following related to sequential circuits. **6M**
i) State diagram
ii) State table
iii) State assignment

OR

- 10 a** Implement the following Boolean function using PAL. **8M**
 $A(w,x,y,z) = \Sigma m(0,2,6,7,8,9,12,13)$
 $B(w,x,y,z) = \Sigma m(0,2,6,7,8,9,12,13,14)$
 $C(w,x,y,z) = \Sigma m(1,3,4,6,10,12,13)$
 $D(w,x,y,z) = \Sigma m(1,3,4,6,9,12,14)$
b What is ROM. Explain about Different types of ROMs briefly? **4M**

*** END ***