

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)**B.Tech II Year II Semester Regular Examinations October-2020****ANALOG CIRCUITS****(Electronics & Communication Engineering)**

Time: 3 hours

Max. Marks: 60

PART-A

(Answer all the Questions 5 x 2 = 10 Marks)

- 1 a What is the need of Darlington pair circuit? 2M
 b What will happen to the oscillation if the magnitude of the loop gain is greater than unity? 2M
 c Compare class A and class B amplifier. 2M
 d Define common mode rejection ratio. 2M
 e List the specifications of D/A and A/D converters. 2M

UNIT-I

- 2 a Draw the appropriate hybrid model for CE amplifier. Obtain expression for current gain. 5M
 b Define f_B and f_T and show that $f_T \approx h_{fe} f_B$. 5M

OR

- 3 a Describe the different methods used for coupling of multistage amplifiers 5M
 b What is the effect of cascading on Bandwidth? Explain 5M

UNIT-II

- 4 a An amplifier has a midband gain of 125 and a bandwidth of 250KHz. If 4% negative feedback is introduced, find the new bandwidth and gain.. 5M
 b Draw the circuit diagram of a wein bridge oscillator and explain its operation. 5M

OR

- 5 a Explain the characteristics of negative feedback amplifiers 5M
 b Draw and explain the operation of Colpitt's oscillator. 5M

UNIT-III

- 6 a Explain the operation of Class-A series fed power amplifier and derive the expression of output power P_0 . 6M
 b Discuss the Stability considerations of tuned amplifiers. 4M

OR

- 7 a Write short note on Crossover Distortion 4M
 b Draw the circuit of double tuned transformer coupled amplifier and explain its operation. 6M

UNIT-IV

- 8 a Design a 3 input amplifier using op-amp with minimum number of resistors such that the output voltage will be $V_0 = 3V_1 - 2V_2 + V_3$ where V_1, V_2, V_3 are three input voltages. 6M
 b Explain the operation of Schmitt Trigger circuit with neat schematic. 4M

OR

- 9 a Explain the inverting mode of operation of op-amp and derive the expression for input resistance R_{if} and output resistance R_{of} . 6M
 b Design a practical differentiator circuit using op-amp. 4M

UNIT-V

- 10 a** Design a HPF at a cut – off frequency of 1 kHz and a pass band gain of 2. **5M**
b Discuss the operation of Inverted R – 2R DAC with neat diagram **5M**

OR

- 11 a** Design a wide band reject filter having $f_h = 400$ Hz and $f_l = 2$ kHz having pass band gain as 2. **5M**
b Explain the operation of 4 – bit successive approximation ADC with an example **5M**

END