

Reg. No:

--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)**B.Tech II Year I Semester Supplementary Examinations November 2020****ANALOG ELECTRONIC CIRCUITS**

(Common to EEE, CSE & CSIT)

Time: 3 hours

Max. Marks: 60

PART-A

(Answer all the Questions 5 x 2 = 10 Marks)

- | | | |
|----------|--|---|
| 1 | a What are the applications of diode clamping circuits?
b Mention the applications of Transistor.
c What is meant by pinchoff voltage.
d Define Slew rate of Op-amp.
e Draw the circuit of an practical integrator. | 2M
2M
2M
2M
2M |
|----------|--|---|

PART-B

(Answer all Five Units 5 x 10 = 50 Marks)

UNIT-I

- | | | |
|----------|---|------------------------|
| 2 | a Derive the expressions for Ripple Factor and Efficiency of Full Wave Rectifier.
b A Half wave rectifier has a load of 3.5k Ω . If the diode resistance and the secondary coil Resistance together have resistance of 800 Ω and the input voltage of 240V, Calculate
(i) Peak, Average and RMS value of the current flowing (ii) DC power output
(iii) AC Power input and (iv) Efficiency of the rectifier. | 5M
5M |
|----------|---|------------------------|

OR

- | | | |
|----------|---|------------------------|
| 3 | a Draw and discuss the VI characteristics of a Zener Diode.
b Discuss the working of inductor filter with circuit diagram. | 5M
5M |
|----------|---|------------------------|

UNIT-II

- | | | |
|----------|--|------------------------|
| 4 | a Describe the Input and Output characteristics of a BJT in CC Configuration. Indicate the regions of operations in the output characteristics.
b Why hybrid model is used for the analysis of BJT amplifier at low frequencies? Draw hybrid model for CE transistor and derive the parameters. | 5M
5M |
|----------|--|------------------------|

OR

- | | | |
|----------|--|------------------------|
| 5 | a Compare CB, CE and CC configurations of BJT.
b If the base current in a transistor is 20 μ A when the emitter current is 6.4mA, what are the values of α and β ? Also calculate the collector current. | 5M
5M |
|----------|--|------------------------|

UNIT-III

- | | | |
|----------|---|------------------------|
| 6 | a Discuss the Drain and Transfer Characteristics of Common Source configuration of n channel JFET.
b Derive input impedance and voltage gain of JFET Common Drain amplifier with neat diagram. | 5M
5M |
|----------|---|------------------------|

OR

- | | | |
|----------|---|------------------------|
| 7 | a Compare CG, CS and CD configurations of JFET.
b With diagram, explain Common Gate Amplifier of JFET. | 6M
4M |
|----------|---|------------------------|

UNIT-IV

- | | | |
|----------|--|------------------------|
| 8 | a Explain briefly i) virtual ground concept ii) current mirror
b Compare and contrast ideal and practical op-amp. | 6M
4M |
|----------|--|------------------------|

OR

- | | | |
|----------|--|------------------------|
| 9 | a Define the terms cmrr, common mode gain, differential mode gain, slew rate.
b Explain the term slew rate and write the importance in op-amp circuits? | 5M
5M |
|----------|--|------------------------|

UNIT-V

- 10 a** Draw the circuit diagram of Dual Slope ADC and explain its working with neat sketches. **6M**
- b** An 8-bit Analog to Digital converter has a supply voltage of +12 volts. Calculate: (i) The voltage step size for LSB. **4M**
(ii) The value of analog input voltage for a digital output of 01001011.
- OR**
- 11 a** Draw and explain successive approximation type ADC. **5M**
- b** The basic step of a 9 bit DAC is 10.3 mV. If “000000000” represents 0 V. What output is produced if the input is “101101111”? **5M**

*****END*****