

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)**B.Tech II Year II Semester Regular Examinations October-2020****DIGITAL ELECTRONICS**

(Electrical & Electronics Engineering)

Time: 3 hours

Max. Marks: 60

PART-A(Answer all the Questions **5 x 2 = 10 Marks**)

- 1 a Convert decimal $(48)_{10}$ to equivalent binary form. **2M**
 b What is multiplexer? Draw 4x2 multiplexer. **2M**
 c How the shift register works? **2M**
 d Design NAND gate using NOR gates. **2M**
 e Define cache memory. **2M**

PART-B(Answer all Five Units **5 x 10 = 50 Marks**)**UNIT-I**

- 2 a What is Switching Functions? Explain switching functions. **5M**
 b Simplify the following Boolean functions to minimum number of literals: **5M**
 $F = ABC + ABC' + A'B$

OR

- 3 Explain about canonical SOP and POS forms. **10M**

UNIT-II

- 4 Minimize the given Boolean function $F(A,B,C,D) = \sum m(0,1,2,3,6,7,13,15)$ using tabulation method and implement using basic gates? **10M**

OR

- 5 a Implement the following Boolean function with 8:1 multiplexer. **5M**
 $F(A,B,C,D) = \pi M(0,3,5,6,8,9,10,12,14)$
 b Implement the following Boolean function with 8:1 multiplexer. **5M**
 $F(A,B,C,D) = \sum m(0,2,6,10,12,13) + d(3,8,14)$

UNIT-III

- 6 Draw the circuit of JK flip-flop using NAND gates and explain its operation. **10M**

OR

- 7 What is Register Explain **10M**
 i) Parallel in Parallel out Register
 ii) Series in Parallel out Register.

UNIT-IV

- 8 What does ECL mean? Draw the circuit of Tristate ECL logic and explain the functions? **10M**

OR

- 9 Explain about Logic gates with symbols and truth tables. **10M**

UNIT-V

- 10 What is ROM organization? Explain about Different types of ROM. **10M**

OR

- 11 Implement PLA circuit for the following functions $F1(A,B,C) = \sum m(3,5,6,7)$, **10M**
 $F2(A,B,C) = \sum m(0,2,4,7)$.

END