

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year I Semester Supplementary Examinations November-2020

ELECTRICAL CIRCUITS-II

(Electrical & Electronics Engineering)

Time: 3 hours

Max. Marks: 60

PART-A

(Answer all the Questions 5 x 2 = 10 Marks)

- | | | | |
|---|---|---|----|
| 1 | a | Differentiate balanced and unbalanced circuits. | 2M |
| | b | Draw the DC response of R-L circuit and the response curve. | 2M |
| | c | Define tree. | 2M |
| | d | State reciprocity theorem. | 2M |
| | e | Summarize some of the properties of Laplace Transform. | 2M |

PART-B

(Answer all Five Units 5 x 10 = 50 Marks)

UNIT-I

- 2 An unbalanced 4 wire star connected load has a balanced voltage of 400V. The load are $Z_1 = (4+j8) \Omega$, $Z_2 = (5+j4)\Omega$, $Z_3 = (15+j20)\Omega$. Calculate line currents, current in neutral wire, total power. **10M**

OR

- 3 A 400V, 3 Φ supply feeds an unbalanced 3 wire star connected 3 wire, star connected load. The branch impedances of the load are $Z_R = (4+j8) \Omega$, $Z_Y = (3+j4) \Omega$, $Z_B = (5+j20) \Omega$. Find the line currents and voltages across phase impedance. Assume RYB phase sequence. **10M**

UNIT-II


- 4 Derive the transient response of an RLC circuit with AC excitation. **10M**

OR

- 5 Derive the transient response of an RC circuit with DC excitation. **10M**


UNIT-III

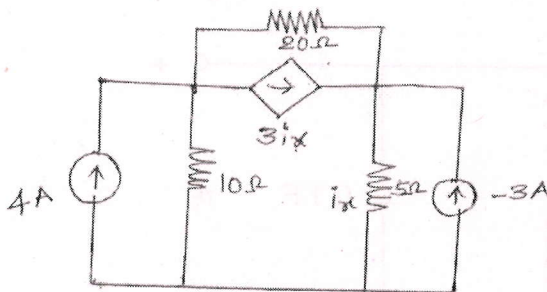- 6 Determine i_x for the following network using network topology. **10M**




OR

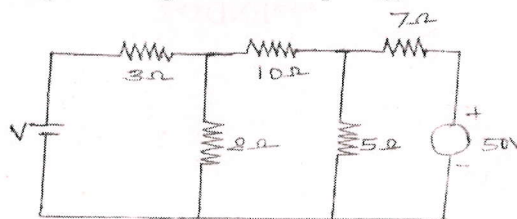- 7 Find voltage V for the circuit shown below which makes the current in the 10 Ω resistor is zero by using nodal analysis using network topology. **10M**




UNIT-IV

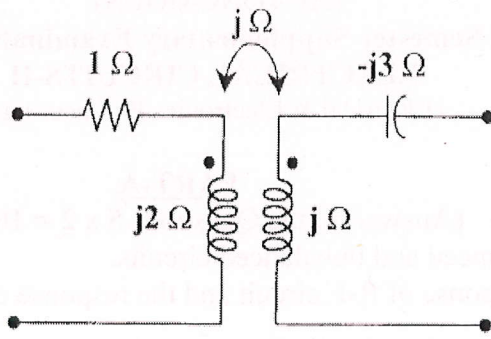8 Obtain the T parameters of the following two-port network. 10M



OR

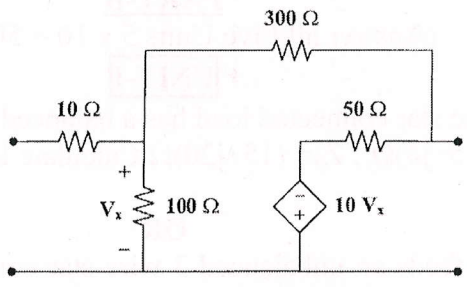9 Obtain h and g parameters of following two port network. 10M



UNIT-V


10 The unit impulse response of a circuit is 10M

$$v_o(t) = 10,000e^{-70t} \cos(240t + \theta)u(t)V \text{ Where } \tan\theta = \frac{7}{24}$$

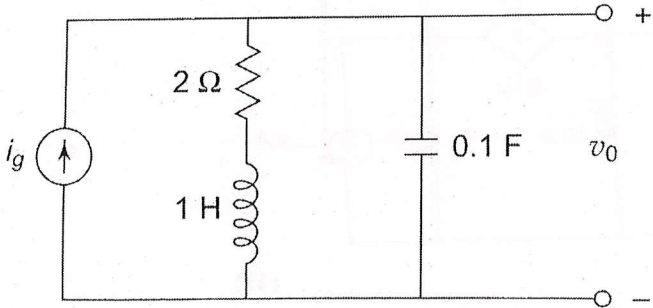- (i) Find the transfer function of the circuit.
- (ii) Find the unit step response of the circuit.

OR

11 Derive the numerical expression for the transfer function v_o/I_g for the circuit shown below. 10M



END