

Reg. No: 

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR**  
(AUTONOMOUS)**B.Tech II Year II Semester Regular Examinations October-2020**  
**POWER ELECTRONICS**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 60

**PART-A**

(Answer all the Questions 5 x 2 = 10 Marks)

- |          |                                                                          |           |
|----------|--------------------------------------------------------------------------|-----------|
| <b>1</b> | <b>a</b> Define forward break overvoltage.                               | <b>2M</b> |
|          | <b>b</b> List the different applications of phase-controlled converters. | <b>2M</b> |
|          | <b>c</b> What are the applications of dc chopper?                        | <b>2M</b> |
|          | <b>d</b> What is meant by PWM control?                                   | <b>2M</b> |
|          | <b>e</b> Write the advantages of VSI.                                    | <b>2M</b> |

**PART-B**

(Answer all Five Units 5 x 10 = 50 Marks)

**UNIT-I**

- |          |                                                                                                   |            |
|----------|---------------------------------------------------------------------------------------------------|------------|
| <b>2</b> | Briefly explain about insulated gate bipolar transistor (IGBT) and its switching characteristics. | <b>10M</b> |
|----------|---------------------------------------------------------------------------------------------------|------------|

**OR**

- |          |                                                                    |            |
|----------|--------------------------------------------------------------------|------------|
| <b>3</b> | Explain briefly voltage commutation and Draw the output waveforms. | <b>10M</b> |
|----------|--------------------------------------------------------------------|------------|

**UNIT-II**

- |          |                                                                                                                                                                                                                                                                                                             |            |
|----------|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|------------|
| <b>4</b> | A single-phase half wave converter operated from a 230V, 50Hz supply. If the load is resistive of value $10\ \Omega$ and firing angle is $60^\circ$ . Determine i) the rectification efficiency ii) Form factor iii) ripple factor iv) Transformer utilization factor v) Peak inverse voltage of thyristor. | <b>10M</b> |
|----------|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|------------|

**OR**

- |          |                                                                                                                          |            |
|----------|--------------------------------------------------------------------------------------------------------------------------|------------|
| <b>5</b> | Explain the operation of three-phase fully controlled rectifier with R load and derive the average and RMS load voltage. | <b>10M</b> |
|----------|--------------------------------------------------------------------------------------------------------------------------|------------|

**UNIT-III**

- |          |                                                                                          |            |
|----------|------------------------------------------------------------------------------------------|------------|
| <b>6</b> | Explain the buck converter operation with help of diagram and draw the output waveforms. | <b>10M</b> |
|----------|------------------------------------------------------------------------------------------|------------|

**OR**

- |          |                                                                                           |            |
|----------|-------------------------------------------------------------------------------------------|------------|
| <b>7</b> | Explain the boost converter operation with help of diagram and draw the output waveforms. | <b>10M</b> |
|----------|-------------------------------------------------------------------------------------------|------------|

**UNIT-IV**

- |          |                                                                   |            |
|----------|-------------------------------------------------------------------|------------|
| <b>8</b> | Explain briefly bipolar sinusoidal modulation with neat diagrams. | <b>10M</b> |
|----------|-------------------------------------------------------------------|------------|

**OR**

- |          |                                                                                                                                                                                                                                                                                                                                                                                    |            |
|----------|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|------------|
| <b>9</b> | A 1- $\phi$ half bridge inverter has a resistive load of $R=3\ \Omega$ , and the D.C. source voltage $V_s/2=115V$ . (a) Sketch the waveforms for $V_0$ , load current $i_{01}$ , currents through thyristor 1 and diode 1 and voltage across thyristor T1.<br>(b) Find the power delivered to load due to fundamental current<br>(c) Check whether forced commutation is required. | <b>10M</b> |
|----------|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|------------|

**UNIT-V**

- |           |                                                                                                                                  |            |
|-----------|----------------------------------------------------------------------------------------------------------------------------------|------------|
| <b>10</b> | Explain the three-phase Voltage Source Inverter with $180^\circ$ conduction mode Also derive the output voltage, output current. | <b>10M</b> |
|-----------|----------------------------------------------------------------------------------------------------------------------------------|------------|

**OR**

- |           |                                                                                   |            |
|-----------|-----------------------------------------------------------------------------------|------------|
| <b>11</b> | Explain briefly three-phase sinusoidal pulse width modulation with neat diagrams. | <b>10M</b> |
|-----------|-----------------------------------------------------------------------------------|------------|

\*\*\*END\*\*\*