

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B Tech I Year II Semester Supplementary Examinations October-2020

BASIC ELECTRICAL ENGINEERING

(Common to ECE, CSE & CSIT)

Time: 3 hours

Max. Marks: 60

PART-A

(Answer all the Questions 5 x 2 = 10 Marks)


- | | | |
|----------|--|-----------|
| 1 | a What is Circuit and Network? | 2M |
| | b Draw Star and Delta Connections of Three Phase circuit. | 2M |
| | c Write Transformation ratio. | 2M |
| | d Define Torque and slip. | 2M |
| | e Define Fuse and Circuit Breaker. | 2M |

PART-B

(Answer all Five Units 5 x 10 = 50 Marks)

UNIT-I


- | | | |
|----------|---|-----------|
| 2 | a Determine the mesh currents for the circuit shown below. | 5M |
|----------|---|-----------|

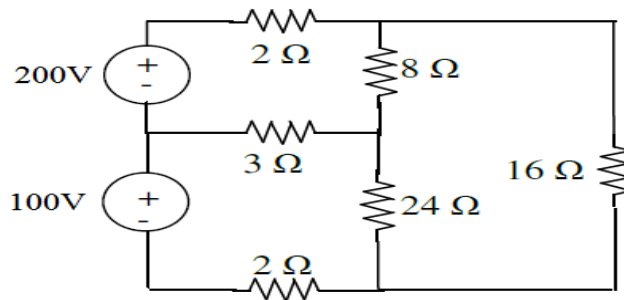

- | | | |
|----------|---|-----------|
| b | Derive the time response of RC circuit. | 5M |
|----------|---|-----------|

OR


- | | | |
|----------|--|-----------|
| 3 | a State and Explain the Super position theorem. And By using superposition theorem find the current flowing through the 3 ohm resistor. | 5M |
|----------|--|-----------|

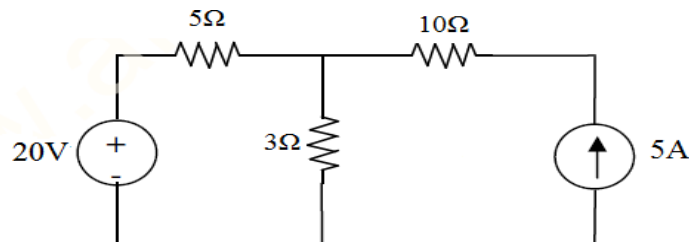

5M

b Find the equivalent resistance between AB for the circuit shown below.
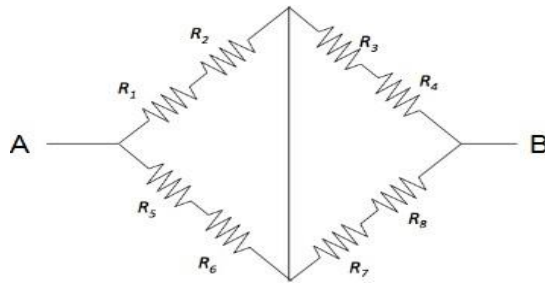
$$R_1=4\Omega, R_2=2\Omega, R_3=8\Omega, R_4=1\Omega, R_5=12\Omega, R_6=3\Omega, R_7=10\Omega \text{ \& } R_8=5\Omega$$



UNIT-II

- 4 a Explain the phasor relation for R, L & C elements. 5M
 b A series RLC circuit of $R=50$ ohms, $L=j25$ ohms. Determine the value of capacitive reactance and impedance at resonance. 5M

OR

- 5 a Derive an expression for the voltage and impedance for a series RLC circuit excited by a sinusoidally alternating voltage. 5M
 b A 120V AC circuit contain 10Ω resistance and 30Ω inductive reactance in series. What is average power of this circuit? 5M

UNIT-III

- 6 a Explain BH characteristics. 5M
 b Explain about magnetic materials. 5M

OR

- 7 a What are three phase transformer connections and explain it? 6M
 b Explain the various losses in a transformer. 4M

UNIT-IV

- 8 a What is rotating magnetic field? Explain in brief. 6M
 b Explain the construction of DC motor. 4M

OR

- 9 a Explain the working principle of single-phase induction motor. 5M
 b Sketch and explain the torque speed characteristics of DC motor. 5M

UNIT-V

- 10 a Explain different types of wiring system. 5M
 b Explain the characteristics of batteries. 5M

OR

- 11 a Explain briefly about earthing and how it plays an important role in installation. 5M
 b What is energy consumption and Explain how it is calculated by an example? 5M

END