

Reg. No:

--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)**B.Tech I Year II Semester Regular Examinations October-2020****DIGITAL LOGIC DESIGN**

(Common to CSE & CSIT)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units **5 x 12 = 60** Marks)**UNIT-I**

- 1 a Convert the following 6M
 i) $(1AD)_{16} = ()_{10}$ ii) $(453)_8 = ()_{10}$ iii) $(10110011)_2 = ()_{10}$ iv) $(5436)_{10} = ()_{16}$
 b Express the Boolean function $F = A + BC$ as a sum of min-terms. 6M

OR

- 2 a Prove the following identities 6M
 $A' B' C' + A' B C' + A B' C' + A B C' = C'$.
 b $A B + A B C + A' B + A B' C = B + A C$. 6M

UNIT-II

- 3 Simplify the Boolean expression using K-map and implement using NAND gates. 12M
 $F(A,B,C,D) = \sum m(0,2,3,8,10,11,12,14)$

OR

- 4 Simplify the Boolean expression using K-MAP. 12M
 $F(A,B,C,D) = \pi M(3,5,6,7,11,13,14,15) \cdot d(9,10,12)$

UNIT-III

- 5 a Explain about Binary Half Adder. 6M
 b Design and draw a full adder circuit. 6M

OR

- 6 Implement BCD to 7-segment decoder for common anode using 4:16 decoder. 12M

UNIT-IV

- 7 a Explain the Logic diagram of JK flip-flop. 6M
 b Explain about Shift Registers. 6M

OR

- 8 Explain the design of a 4 bit binary counter with parallel load in detail. 12M

UNIT-V

- 9 What is memory decoding? Explain about the construction of 4 X 4 RAM? 12M

OR

- 10 a Write difference between PROM, PLA & PAL. 6M
 b Implement the following Boolean expressions using ROM. 6M
 $F1(A,B,C) = \sum m(0,2,4,7)$
 $F2(A,B,C) = \sum m(1,3,5,7)$

*** END ***