

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech I Year II Semester Regular Examinations October-2020

BASIC ELECTRICAL ENGINEERING
(Electronics & Communication Engineering)


Time: 3 hours

Max. Marks: 60

(Answer all Five Units **5 x 12 = 60** Marks)

UNIT-I

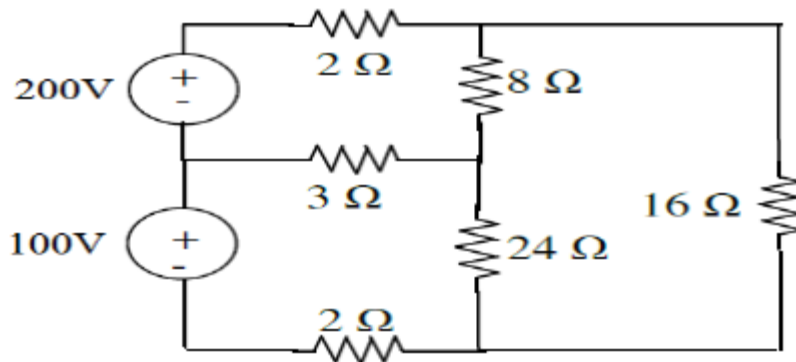
- 1 a** Determine the mesh currents for the circuit shown below. **6M**



- b** State and explain Thevinin's theorem. **6M**

OR

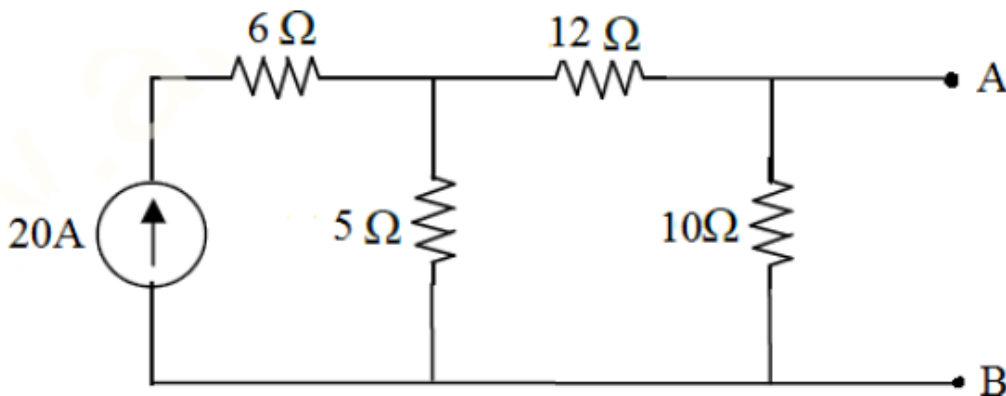- 2 a** Determine the equivalent Capacitance when the resistors are connected in series & parallel. **6M**
- b** Find the Norton's equivalent for the circuit shown below. **6M**



UNIT-II

- 3 Derive an expression for the current and impedance for a series RL and RC circuit excited by a sinusoidally alternating voltage. Draw the phasor diagrams. **12M**

OR

- 4 a Explain resonance for series RLC circuit and derive the equation for resonant frequency. **7M**
- b A series RLC circuit of $R=40\Omega$, $L=50.07\text{mH}$ and a capacitor is connected across a 400V, 50Hz, A.C. supply. This RLC combination draws a current of 10A. Calculate: **5M**
- a) power factor of the circuit
- b) Capacitor value.

UNIT-III

- 5 List the various types of D.C Generators and Explain in detail. **12M**

OR

- 6 a What is the necessity of speed control? **5M**
- b How to control the speed of D.C. Shunt motor. Explain it with anyone example. **7M**

UNIT-IV

- 7 a Write the short notes on Voltage Regulation & Efficiency. **6M**
- b Derive an EMF equation of a single-phase transformer. **6M**

OR

- 8 Explain working principle of induction motor in detail. **12M**

UNIT-V

- 9 With neat diagrams, explain various types of fuses used in electrical wiring systems. **12M**

OR

- 10 Define the following: **12M**
- i) What is the difference between wire and cable?
- ii) Fusing Current
- iii) Fusing Factor
- iv) Rated Current
- v) Fuse element

***** END *****