

O.P.Code: 20CS0503b

R20

H.T.No.

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech I Year II Semester Regular & Supplementary Examinations August-2023

DIGITAL LOGIC DESIGN

(Common to CSE, CSM, CCC, CIC, CAI)

Time: 3 Hours

(Answer all Five Units 5 x 12 = 60 Marks)

Max. Marks: 60

UNIT-I

- 1 a Convert the following numbers:
i) $(AB)_{16} = ()_2$ ii) $(1234)_8 = ()_{16}$ CO1 L5 4M
b Convert $(AB33)_{16}$ to binary and then to gray code. CO1 L5 4M
c Using BCD arithmetic, perform addition of $(7129)_{10} + (7711)_{10}$ CO1 L5 4M

OR

- 2 a Express the Boolean function, $F = A + B'C$ in sum of min terms form. CO1 L1 6M
b Convert $Y = A(A+B+C)$ to standard POS form. CO1 L6 6M

UNIT-II

- 3 Simplify the Boolean function using K-MAP and draw the logic diagram.
 $F(A, B, C, D) = \sum m(1, 2, 3, 8, 9, 10, 11, 14) + d(7, 15)$ CO5 L6 12M

OR

- 4 a Design the circuit using NAND gates for the given function.
 $F = ABC' + DE + AB'D'$ CO5 L6 6M
b For the given function, design the circuit using NOR gates.
 $F = (X+Y).(X'+Y'+Z')$ CO5 L6 6M

UNIT-III

- 5 a Explain the working of a Carry- Look ahead adder. CO2 L2 6M
b Sketch BCD adder block diagram and explain its working. CO2 L3 6M

OR

- 6 a Design and implement the following Boolean function by 8:1 Multiplexer. $(A, B, C, D) = \sum m(0, 1, 2, 5, 7, 8, 9, 14, 15)$. CO5 L3 6M
b Explain in detail about Priority Encoder. CO4 L2 6M

UNIT-IV

- 7 a List the advantages and disadvantages of Flipflops. CO6 L1 6M
b What is the difference between Characteristic table and Excitation table? Give the excitation tables of SR, JK, T and D Flipflops. CO3 L2 6M

OR

- 8 a What are the steps involved in design of a Synchronous Sequential circuit? CO1 L2 6M
b Define a Register. Explain in detail about various Shift Registers. CO4 L2 6M

UNIT-V

- 9 a Define and distinguish between PROM, PLA & PAL. CO4 L4 6M
b Design and implement the following Boolean expressions using PROM.
 $F1(A, B, C) = \sum m(0, 2, 4, 7)$, $F2(A, B, C) = \sum m(1, 3, 5, 7)$. CO6 L5 6M

OR

- 10 a What is PAL? List its applications. CO1 L1 4M
b Design and implement the following functions using PAL
i) $A(w, x, y, z) = \sum m(0, 2, 6, 7, 8, 9, 12, 13)$ CO6 L6 8M
ii) $B(w, x, y, z) = \sum m(0, 2, 6, 7, 8, 9, 12, 13, 14)$

*** END ***

