

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech I Year II Semester Regular & Supplementary Examinations August-2023

FUNDAMENTALS OF ELECTRICAL CIRCUITS
(Electrical and Electronics Engineering)


Time: 3 Hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

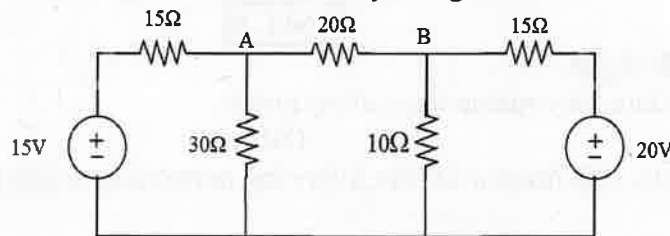- 1 a Determine the Equivalent Capacitance when two capacitor are connected in Series & Parallel. CO1 L3 6M
b Determine the current in branch A-B by using KVL CO1 L3 6M




OR

- 2 a State and explain Ohm's law. CO1 L2 6M
b Derive an expression for RMS values of sine wave form. CO1 L3 6M

UNIT-II

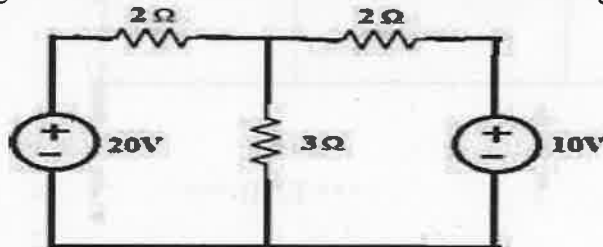
- 3 a Verify Tellegen's theorem for the circuit shown in below figure. CO2 L3 6M



- b State and prove Tellegen's theorem. CO2 L2 6M

OR

- 4 a State & explain Norton's theorem. CO2 L2 6M
b By using superposition theorem find the current flowing through the 3-ohm resistor CO2 L3 6M

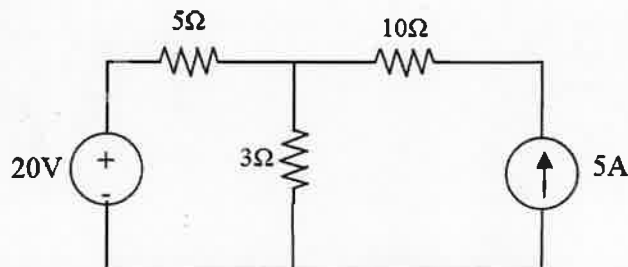**UNIT-III**

- 5 a Explain about Series resonance with phasor diagrams. CO3 L3 6M
b Determine the quality factor of coil for the series circuit consisting of R=10Ω, L=0.1H and C=10μF. CO3 L3 6M

OR

- 6 a Explain about Quality factor of parallel resonance. CO3 L3 6M
b Explain the importance of resonance and find the condition for series resonance? CO3 L3 6M

UNIT-IV

- 7 a Derive the expressions for mutual inductance with expressions. CO4 L2 6M
b A 15mH coil is connected in series with another coil. The total inductance is 70mH. When one of the coils is reversed, the total inductance is 30mH. Find the self-inductance of second coil, mutual inductance and coefficient of coupling. CO4 L3 6M

OR


- 8 a Write the expression for equivalent inductance of two coupled coils connected in series and parallel. CO4 L2 6M
b Two coils connected in series have a self-inductance of 20mH and 60mH respectively. The total inductance of the combination was found to be 100mH. Determine the amount of mutual inductance that exists between the two coils (i) aiding each other (ii) opposing each other. CO4 L3 6M

UNIT-V

- 9 a Define cut-set & tie-set. CO5 L2 6M
b Write the procedure for constructing cut-set matrix. CO5 L3 6M

OR

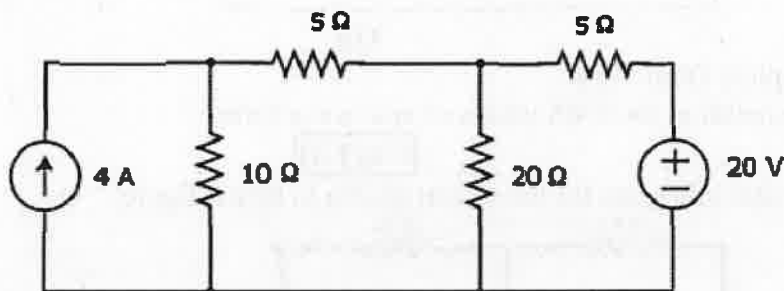- 10 Determine current in 10Ω resistor for the following network by using nodal analysis. CO5 L4 12M



*** END ***