

Reg. No: 

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR**  
(AUTONOMOUS)

**B.Tech I Year I Semester Regular & Supplementary Examinations March-2023**

**PRINCIPLES OF ELECTRICAL ENGINEERING**

(Common to CSE,CSIT, CSM, CIC, CAD, CCC & CAI)


Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

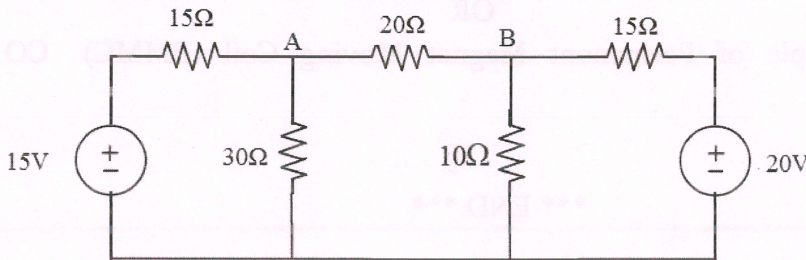
**UNIT-I**

- 1 a State and Explain about the ohm's law. CO 1 L1 6M  
 b Determine the current in branch A-B by using KVL. CO 1 L4 6M




OR

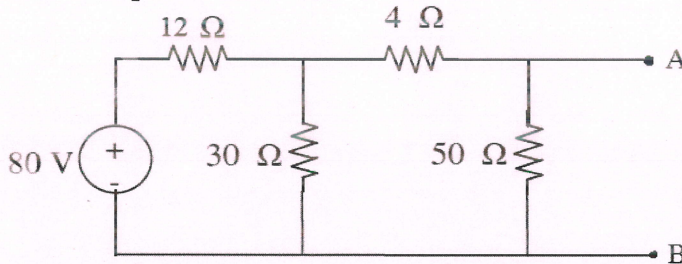- 2 a State and explain Thevenin's theorem. CO 1 L1 6M  
 b Find the Thevenin's equivalent for the circuit shown below CO 2 L4 6M



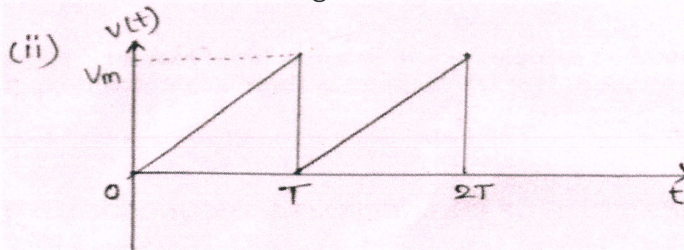**UNIT-II**

- 3 a Derive an expression for RMS value of sine wave form. CO 3 L2 6M  
 b Find the RMS value for the following waveform CO 3 L3 6M



OR

- 4 a Derive an expression for the current and impedance for a series RL circuit excited by a Sinusoidal alternating voltage. Draw the phasor diagrams. CO 3 L3 6M  
 b A series circuit consisting of a 10Ω resistor, a 100μF capacitor and a 10 mH inductor is driven by a 50 Hz a.c. voltage source of maximum value 100 volts. Calculate the equivalent impedance, Current in the circuit and the phase angle. CO 3 L2 6M

**UNIT-III**

- |   |  |      |    |     |
|---|--|------|----|-----|
| 5 | Explain the Constructional details of DC machine with neat sketch. | CO 4 | L1 | 12M |
|   | OR   |      |    |     |
| 6 | What are the different types of DC Motors? Explain in detail.      | CO 4 | L1 | 12M |

**UNIT-IV**

- |   |  |      |    |     |
|---|--|------|----|-----|
| 7 | Explain the Working principle of single phase transformer.   | CO 5 | L2 | 12M |
|   | OR   |      |    |     |
| 8 | Define voltage regulation of an alternator. Explain procedure to determine voltage regulation by Synchronous Impedance Method. | CO 5 | L4 | 12M |

**UNIT-V**

- |    |   |      |    |     |
|----|---|------|----|-----|
| 9  | a Classify different types of measuring instruments.                            | CO 6 | L1 | 6M  |
|    | b Explain operating principles of Moving Iron and PMMC instruments              | CO 6 | L2 | 6M  |
|    | OR  |      |    |     |
| 10 | Explain operating principle of Permanent Magnet Moving Coil (PMMC) instruments. | CO 6 | L2 | 12M |

\*\*\* END \*\*\*