

Reg. No:

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)**

B.Tech I Year I Semester Regular & Supplementary Examinations March-2023

PRINCIPLES OF ELECTRICAL CIRCUITS

(Electronics and Communication Engineering)

Time: 3 hours

Max. Marks: 60


(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-II


- | | | | | |
|---|---|-----|----|----|
| 1 | a Determine the Equivalent inductance when the two inductor are connected in series and parallel. | CO1 | L3 | 3M |
| | b State and prove Kirchoff's current law with suitable examples. | CO1 | L3 | 3M |
| | c Explain in detail about delta to star transformation of a resistive network. | CO1 | L3 | 6M |

OR

- | | | | | |
|---|---|-----|----|----|
| 2 | a Determine the current in 10Ω resistor for the following network by using KCL. | CO1 | L3 | 6M |
|---|---|-----|----|----|

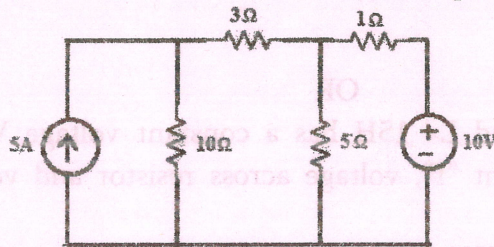


- | | | | | |
|---|--|-----|----|----|
| b | Write the Mesh Current equations in the Circuit shown in figure below, and determine the currents. | CO2 | L3 | 6M |
|---|--|-----|----|----|

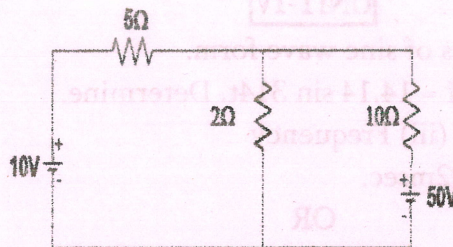


UNIT-III

- | | | | | |
|---|---|-----|----|-----|
| 3 | Verify Superposition Theorem for 4Ω resistor for the following circuit. | CO3 | L3 | 12M |
|---|---|-----|----|-----|

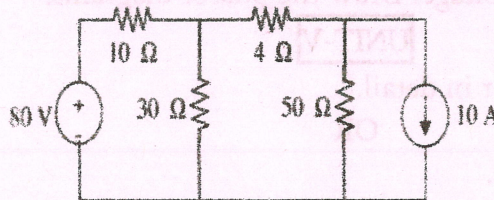


OR

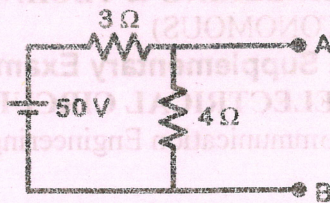- 4 a State Norton's theorem. CO3 L1 2M
 b Find Norton's equivalent circuit across AB for the circuit shown. CO3 L3 5M



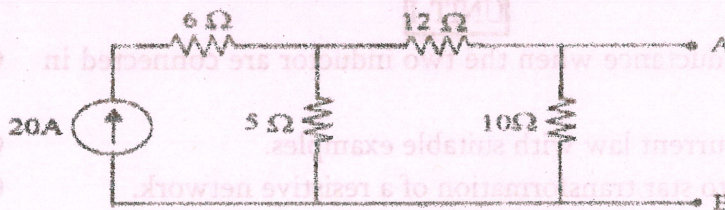- c Find the Norton's equivalent for the circuit shown below. CO3 L3 5M



UNIT-III

- 5 a Define Time constant of RL circuit. CO4 L4 6M
 b Define Time constant of RC circuit. CO4 L4 6M

OR

- 6 a A series RL circuit with $R=30\Omega$ and $L=15H$ has a constant voltage $V=60v$ applied at $t=0$. Determine the current "I", voltage across resistor and voltage across inductor. CO4 L4 6M
 b A Series RL circuit with $R=50\Omega$ and $L=10H$ has constant voltage $V=100volts$ applied at $t=0$ by the closing the switch find the complete current. CO4 L4 6M

UNIT-IV

- 7 a Derive an expression for average values of sine wave form. CO5 L4 6M
 b An alternating current is expressed as $I = 14.14 \sin 314t$. Determine.
 (i) Maximum current (ii) RMS current (iii) Frequency
 (iv) Instantaneous current when $t = 0.02msec$. CO5 L2 6M

OR


- 8 a Define Admittance and impedance. CO5 L2 4M
 b Derive an expression for the current and impedance for a series RC circuit excited by a Sinusoidally alternating voltage. Draw the phasor diagrams. CO5 L4 8M

UNIT-V

- 9 Explain about Constant-K High-pass filter in detail. CO6 L2 12M

OR

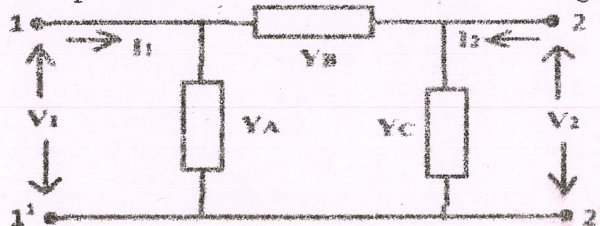- 10 a Explain about short-circuit parameters. CO6 L2 6M
 b Find the Short-circuit parameters for the circuit shown in figure. CO6 L2 6M



*** END ***