

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year I Semester Regular & Supplementary Examinations March-2023

SWITCHING THEORY AND LOGIC DESIGN

(Electronics and Communication Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a Define Boolean Algebra and list the postulates used in it. CO1 L1 6M
b State and prove any four Boolean theorems of Boolean algebra. CO1 L3 6M

OR

- 2 a Simplify the given Boolean function, F to minimum number of literals using Boolean algebra $F=XY'Z + X'Y'Z + W'XY + WX'Y + WXY$. CO1 L4 6M
b Draw the logic diagram for the simplified expression of the above using AOI logic. CO2 L1 6M

UNIT-II

- 3 a Simplify the Boolean function using Five Variable K-Map. CO2 L4 6M
 $F=\sum m(0, 1, 2, 4, 7, 8, 12, 14, 15, 16, 17, 18, 20, 24, 28, 30, 31)$
b Apply the K-Map technique to simplify the given Boolean expression in POS form using K-Map $F(A,B,C,D) = \sum(1,2,4,5,9,12,13,14)$ CO2 L4 6M

OR

- 4 Simplify the following Boolean function using Tabulation method, and realize its logic circuit with NAND gates and NOR gates. CO2 L4 12M
 $Y(A, B, C, D) = \sum(1, 3, 5, 8, 9, 11, 15)$

UNIT-III

- 5 a Explain the procedure of designing a combinational logic circuit with an example. CO1 L2 6M
b Design a Full Subtractor using truth table. CO5 L3 6M

OR

- 6 a Define Multiplexer. Construct 4:1 multiplexer with logic gates and truth table. CO4 L3 6M
b Represent the following Boolean function with an 8:1 multiplexer. CO4 L2 6M
 $F(A,B,C,D) = A'BD' + ACD + B'CD + A'C'D$

UNIT-IV

- 7 a Define Latch and list different types of Latches. CO1 L1 4M
b Define Flip-Flop. What are the different types of Flip-Flops? CO1 L1 4M
c Explain the working principle of RS Flip-Flop with the help of logic diagram and give its Characteristic Table and Graphic symbol. CO3 L2 4M

OR

- 8 What is a synchronous counter? Design a 3-bit synchronous up/down counter. CO6 L4 12M

UNIT-V

- 9 Explain the following related to sequential circuits with suitable examples: CO1 L2 12M
i) State diagram ii) State table iii) State assignment

OR

- 10 Illustrate the PAL for the following Boolean functions. CO5 L3 12M
(i) $A(w,x,y,z) = \sum m(0, 2, 6, 7, 8, 9, 12, 13)$ (ii) $B(w,x,y,z) = \sum m(0, 2, 6, 7, 8, 9, 12, 13, 14)$

*** END ***

Reg. No. _____

INDIAN INSTITUTE OF ENGINEERING & TECHNOLOGY - PUTTUR
(AUTONOMOUS)

II Tech II Year I Semester Regular & Supplementary Examinations March-2023
SWITCHING THEORY AND LOGIC DESIGN

(Electronics and Communication Engineering)

Max. Marks: 70

Time: 3 hours

Answer all Five Units 2 x 12 = 60 Marks

UNIT-I

288

- 1 a) Define Boolean Algebra and list the postulates used in it. (6M)
 - b) State and prove any two Boolean theorems of Boolean algebra. (6M)
- OR
- 2 a) Simplify the given Boolean function F to minimum number of literals using Boolean algebra $F = XYZ + X'YZ + W'XY + WXY + W'XY + WXY$. (6M)
 - b) Draw the logic diagram for the simplified expression of the above using AOI logic. (6M)

UNIT-II

- 3 a) Simplify the Boolean function using Five Variables K-Map. (6M)
 - $F = \sum m(12, 13, 14, 15, 16, 17, 18, 20, 24, 28, 30, 31)$
 - b) Apply the K-map technique to simplify the given Boolean expression in POS form using K-Map (A, B, C, D) = $\sum (1, 2, 4, 5, 9, 12, 14)$. (6M)
- OR

- 4 Simplify the following Boolean function using Tabulation method and realize logic circuit with NAND gates and NOR gates. (12M)
- $F(A, B, C, D) = \sum (2, 3, 5, 8, 11, 13)$

UNIT-III

- 5 a) Explain the procedure of designing a combinational logic circuit with an example. (6M)
 - b) Design a Full Subtractor using truth table. (6M)
- OR
- 6 a) Define Multiplexer. Construct 4:1 multiplexer with logic gates and truth table. (6M)
 - b) Represent the following Boolean function with an 8:1 multiplexer. (6M)
 - $F(A, B, C, D) = A'BD + ACD + B'CD + A'CD$

UNIT-IV

- 7 a) Define latch and list different types of latches. (4M)
 - b) Define flip-flop. What are the different types of flip-flops? (4M)
 - c) Explain the working principle of RS flip-flop with the help of logic diagram and give its Characteristic Table and Excitation table. (4M)
- OR

- 8 What is a synchronous counter? Design a 3-bit synchronous up/down counter. (12M)

UNIT-V

- 9 Explain the following related to sequential circuits with suitable examples. (12M)
 - (i) State diagram (ii) State table (iii) State assignment
- OR

- 10 Illustrate the KAT for the following Boolean functions. (12M)
- (i) $F(W, X, Y) = \sum m(2, 5, 6, 7, 10, 11, 12, 13)$ (ii) $G(X, Y, Z) = \sum m(0, 1, 2, 3, 7, 11, 12, 14)$

END