

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year II Semester Regular & Supplementary Examinations August-2023

ELECTRONIC CIRCUIT ANALYSIS
(Electronics & Communications Engineering)

Time: 3 Hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a With the help of necessary circuit diagrams and approximations, deduce the expression for CE short circuit current gain and derive the relation between f_{β} and f_T . CO4 L4 6M
b Construct the block diagram of n-stage cascade amplifier and analyze its various parameters. CO5 L3 6M

OR

- 2 a With diagram, calculate the expressions for Voltage gain, current gain, Input and output resistances of a Cascade amplifier. CO4 L4 6M
b Explain the effect of cascading on bandwidth in multistage amplifiers. CO3 L3 6M

UNIT-II

- 3 a Explain in detail about the basic Amplifiers used in Feedback amplifiers. CO3 L2 6M
b Analyze Emitter follower circuit with necessary diagram for input and output resistances with feedback. CO6 L4 6M

OR

- 4 a Compare various types of feedback amplifiers CO2 L4 6M
b Explain Feedback amplifier topologies with necessary diagrams. CO3 L2 6M

UNIT-III

- 5 a A Colpitts oscillator is designed with $C_1 = 100$ pF and $C_2 = 7500$ pF. The inductance is variable. Determine the range of inductance values, if the frequency of oscillations is to vary between 950 KHz to 2050 KHz. CO6 L3 6M
b Appraise the concept of stability in Oscillators. CO1 L4 6M

OR

- 6 a With circuit diagram, describe the stagger tuning operation. Sketch necessary waveforms. CO4 L4 6M
b Explain the working of a Crystal oscillator and sketch its characteristics. CO4 L3 6M

UNIT-IV

- 7 a Inspect about Transformer coupled Class A Power Amplifier with diagram and determine its Maximum efficiency. CO3 L4 6M
b Examine the stability considerations of a tuned amplifier. CO2 L3 6M

OR

- 8 a A Class B push pull amplifier drives a load of 16Ω , connected to the secondary of ideal transformer. The V_{CC} is 25V. If number of turns on primary is 200 and secondary is 50. Determine maximum power output, DC power input and efficiency. CO5 L3 6M
b With circuit diagram, describe the stagger tuning operation. Sketch necessary waveforms. CO3 L3 6M

UNIT-V

- 9 a Examine the operation of Emitter Coupled Monostable multivibrator. CO3 L4 6M
b Derive the expression for pulse width, T of collector coupled Monostable multivibrator. CO4 L4 6M

OR

- 10 a Summarize the effect of cascading single tuned amplifiers on bandwidth. CO4 L4 6M
b Demonstrate the operation of Bistable multivibrator with neat circuit diagram. CO3 L2 6M

*** END ***

