

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR**  
(AUTONOMOUS)

**B.Tech II Year II Semester Regular & Supplementary Examinations August-2023**  
**POWER ELECTRONICS**

(Electrical & Electronics Engineering)

**Time: 3 Hours**

**Max. Marks: 60**

(Answer all Five Units 5 x 12 = 60 Marks)

**UNIT-I**

- 1 Describe about Insulated Gate Bipolar Transistor (IGBT) and it's switching characteristics. **CO1 L2 12M**

**OR**

- 2 Illustrate the voltage commutation and draw the output wave forms. **CO1 L4 12M**

**UNIT-II**

- 3 A single Phase fully controlled converter supplies an inductive load. Assuming load current is constant=10A. Determine the following quantities if supply voltage is 230V, 50 Hz and  $\alpha=40$ . Calculate the i) Average Output Voltage of converter, ii) Supply RMS Current, iii) Supply Fundamental RMS Current, iv) Fundamental Power factor, v) Supply Power Factor, vi) Supply harmonic factor **CO2 L3 12M**

**OR**

- 4 Describe the operation of single-phase half wave converter with R-Load at  $\alpha=60$  with necessary wave forms. Also derive the output voltage, output current and RMS output voltages. **CO2 L2 12M**

**UNIT-III**

- 5 a For step down chopper dc source voltage is 230v, load resistance is 10 ohm. The chopper when it is in ON is 2V. For a duty cycle of 0.4. Calculate i) average and rms values of output voltage ii) chopper efficiency. **CO3 L3 8M**  
b List some applications of dc chopper. **CO3 L2 4M**

**OR**

- 6 A DC Chopper (Step-Down) has a resistive load  $R=10\Omega$  and the input voltage=200v. When the chopper remains on, its voltage drop is 2V. The chopper frequency is 1Khz. If the duty cycle is 50% Determine i) Average Output Voltage, ii) RMS Output Voltage, iii) Chopper Efficiency & iv) Effective input resistance of chopper **CO3 L3 12M**

**UNIT-IV**

- 7 Illustrate the principle of operation of single phase to single phase step-down Bridge type cycloconverter with Resistive Inductive Load for Discontinuous Load Current. **CO4 L4 12M**

**OR**

- 8 The Input Voltage to the Bridge type Cycloconverter is 230v, 50 Hz Single-Phase. The Load resistance is  $10\Omega$  and the load inductance is 60mH. The frequency of the output is 25Hz. If the Converters are operated as semi converters such that  $0 < \alpha < \pi$  and the delay angle  $\alpha=2\pi/3$ , Determine i) The RMS Value of Output voltage, ii) The RMS Current of each thyristor and iii) The input Power Factor (PF). **CO4 L4 12M**

**UNIT-V**

- 9 a Explain the operation of single phase full wave ac voltage controller with R-L load. **CO5 L2 6M**
- b Describe the operation of TRIAC in different modes. **CO5 L2 6M**

**OR**

- 10 a The single phase full wave AC voltage controller has a resistive load of  $R=5\Omega$  & the input voltage  $V_S=120V(RMS), 50HZ$ . The delay angles of thyristors T1 & T2 are equal i.e.,  $\alpha_1=\alpha_2=2\pi/3$ . Determine (i) The RMS output voltage (ii) Input power factor (iii) Average current of thyristor (iv) The RMS current of thyristor. **CO5 L3 8M**
- b Outline the applications of AC voltage controller. **CO5 L2 4M**

**\*\*\* END \*\*\***