

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR**  
(AUTONOMOUS)  
**B.Tech III Year II Semester Regular Examinations August-2023**

**POWER SEMICONDUCTOR DRIVES**

(Electrical & Electronics Engineering)

**Time: 3 Hours**

**Max. Marks: 60**

(Answer all Five Units 5 x 12 = 60 Marks)

**UNIT-I**

- 1 With neat diagram, explain 1- $\phi$  fully controlled converter fed by separately excited DC motor in continuous conduction mode. CO1 L4 12M

OR

- 2 Using RLE load, analyze the operation of three phase fully controlled converter with neat sketch. CO1 L4 12M

**UNIT-II**

- 3 A non-circulating current dual converter is connected to a dc motor. Explain its control strategies for selecting its multi-quadrant operation converter with the help of power circuit diagrams. CO2 L5 12M

OR

- 4 a Explain the operation of closed loop speed control of dc drive. CO2 L2 6M  
b A 230V, 870rpm, 100A separately excited DC motor has an armature resistance of 0.02 $\Omega$ . It is coupled to an over hauling with a torque of 400N-m. Determine the speed at which motor can hold the Load by regenerative braking. CO2 L3 6M

**UNIT-III**

- 5 Describe how the operation of second quadrant can be obtained from chopper fed by separately excited DC motor. CO3 L2 12M

OR

- 6 A separately excited dc motor is running at 1100rpm, 210V, with an armature resistance of 0.08. The initial speed of the motor is 1200rpm when broken by plugging, Take  $I_a=140A$ . CO3 L3 12M  
(i) To limit the braking current to twice the full load value, calculate the resistance to be placed in armature circuit.  
(ii) Calculate the braking torque, and when speed is reduced to zero, calculate the torque.

**UNIT-IV**

- 7 Explain briefly Voltage source inverter control of induction motor? CO4 L2 12M

OR

- 8 Explain the speed control method for 3- $\phi$  induction motor bu using Cycloconverter. CO4 L3 12M

**UNIT-V**

- 9 Discuss the operation of a voltage source inverter fed synchronous motor Drive. CO5 L2 12M

OR

- 10 Explain the closed loop control scheme of adjustable speed synchronous motor drive. Mention its need and advantages. CO5 L2 12M

\*\*\* END \*\*\*

