



**SIDDHARTH GROUP OF INSTITUTIONS :: PUTTUR**  
Siddharth Nagar, Narayanavanam Road – 517583

**QUESTION BANK (DESCRIPTIVE)**

**Subject with Code :** EC-II(15A02301)

**Course & Branch:** B.Tech - EEE

**Year & Sem:** II-B.Tech & I-Sem

**Regulation:** R15


**UNIT -I**

**NETWORK TOPOLOGY**

1. Find the cutset matrix for the followings?


a)

[5M]

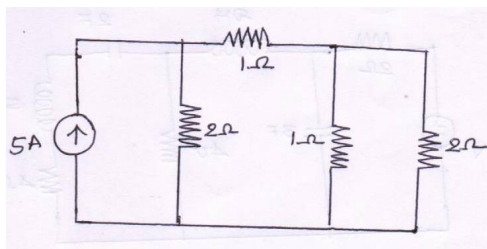

b)


[5M]

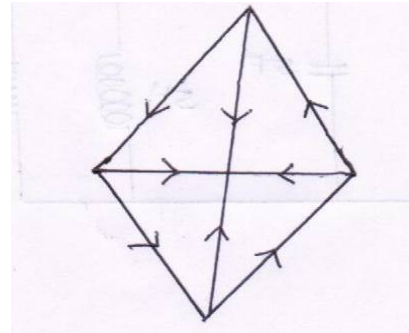

2. Find the tieset matrix for the followings?


a)

[5M]

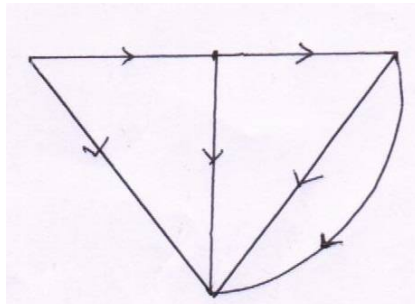


b)


[5M]

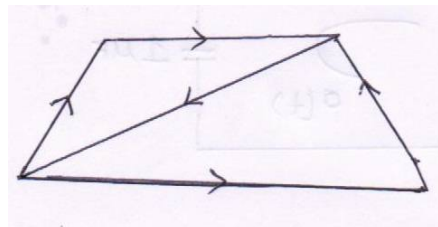

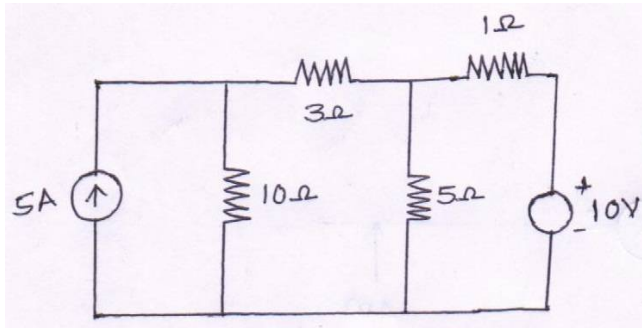
3. Determine current in  $10\Omega$  resistor for the following network by using nodal analysis. [10M]



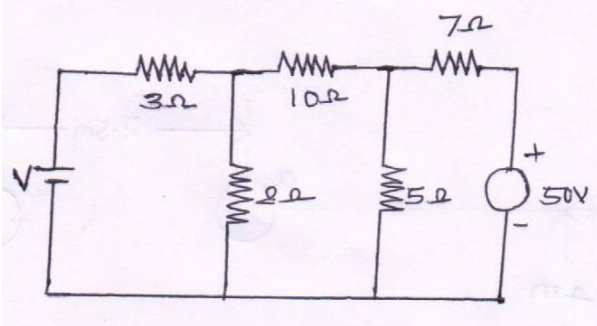
4. Find voltage  $V$  for the circuit shown in fig which makes the current in the  $10\Omega$  resistor is zero by using nodal analysis? [10M]



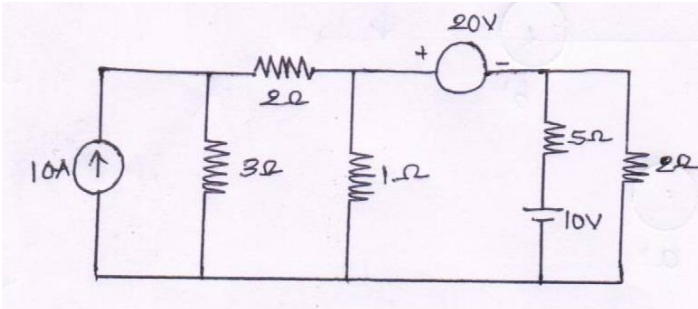
5. Determine current in  $5\Omega$  resistor for the circuit shown in figure. [10M]



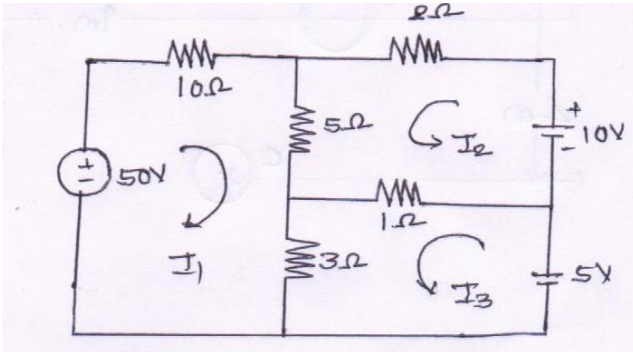
6. Determine mesh currents for the following network. [10M]



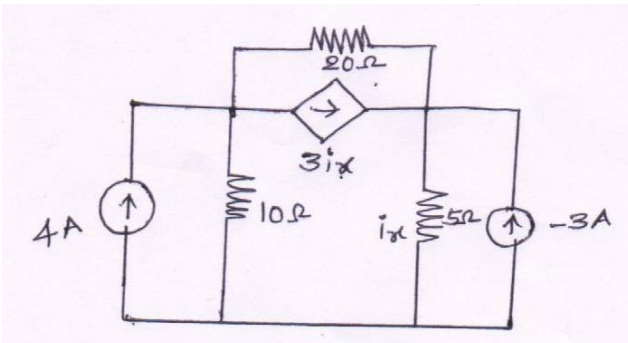7. Determine  $i_x$  for the following network. [10M]




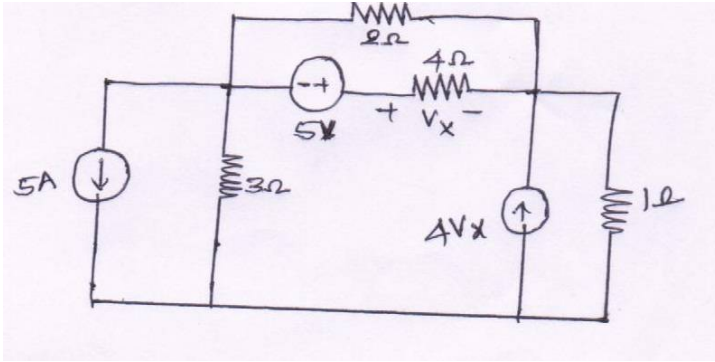8. For the circuit shown in figure. Find the voltage across  $4\Omega$  resistor using nodal analysis. [10M]




9. Write the procedure to draw the dual network and find dual network for the followings. [10M]

a) [5M]

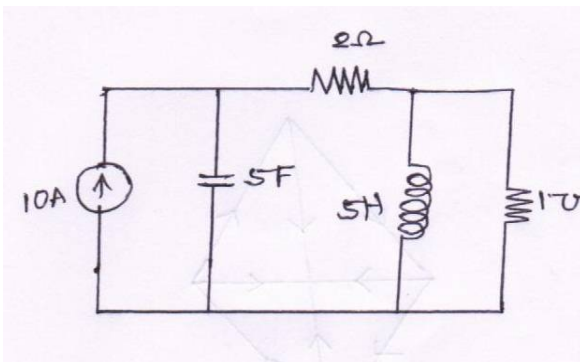

b) [5M]

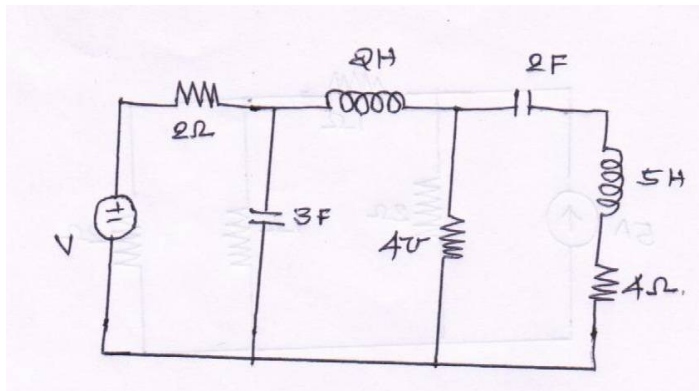

- |  |      |
|--|------|
| 10. a) Define graph.                   | [2M] |
| b) Define planar and non-planar graph. | [2M] |
| c) Define duality.                     | [2M] |
| d) Define cutset.                      | [2M] |
| e) Define tieset.                      | [2M] |



**SIDDHARTH GROUP OF INSTITUTIONS :: PUTTUR**  
Siddharth Nagar, Narayanavanam Road – 517583

**QUESTION BANK (DESCRIPTIVE)**

**Subject with Code :** EC-II(15A02301)

**Course & Branch:** B.Tech - EEE

**Year & Sem:** II-B.Tech & I-Sem

**Regulation:** R15

**UNIT-2**

**THREE PHASE AC CIRCUITS**

1. Derive the relationship of voltage and current in star connected load. [10M]
2. Derive the relationship of voltage and current in delta connected load. [10M]
3. A three phase balance delta connected load of  $(4+j8) \Omega$  is connected across a 400V, 3 $\phi$  balanced supply. Determine the phase currents and line currents. And also power drawn by the load. Assume RYB phase sequence. [10M]
4. A balanced star connected load having an impedance  $(15+j20) \Omega$  per phase is connected to a three phase 440 V, 50Hz supply. Find line currents and phase voltages. Assume RYB phase sequence and also calculate power drawn by the load. [10M]
5. A balanced star connected load of  $(4+j3) \Omega$  per phase is connected to a balanced 3 $\phi$  400v supply. The phase current is 12 A. Find a) active power b) reactive power c) Apparent power. [10M]
6. A balanced delta connected load of  $(4+j3) \Omega$  per phase is connected to a balanced 3 $\phi$  440v supply. The phase current is 12 A. Find a) active power b) reactive power c) Apparent power. [10M]
7. Three impedances  $Z_1=20\angle^{30^\circ}$ ,  $Z_2=40\angle^{60^\circ}$ ,  $Z_3=10\angle^{-90^\circ}$  are delta connected to a 400V, 3 $\phi$  System. Determine i) phase currents ii) line currents iii) total power consumed by the load. [10M]
8. An unbalanced 4 wire star connected load has a balanced voltage of 400V. The load are  $Z_1=(4+j8) \Omega$ ,  $Z_2=(5+j4)\Omega$ ,  $Z_3=(15+j20)\Omega$ . Calculate line currents, current in neutral wire, total power. [10M]
9. A 400V, 3 $\phi$  supply feeds an unbalanced 3 wire star connected 3 wire, star connected load. The branch impedances of the load are  $Z_R=(4+j8)\Omega$ ,  $Z_Y=(3+j4)\Omega$ ,  $Z_B=(5+j20)\Omega$ . Find the line currents and voltages across phase impedance. Assume RYB phase sequence. [10M]
10. a) Write the voltage and current relationship in star connected system? [2M]  
b) Write the voltage and current relationship in star connected system? [2M]  
c) What are the different methods are used to solve the unbalanced systems? [2M]  
d) Draw the star connected load. [2M]  
e) Draw the delta connected load. [2M]



**SIDDHARTH GROUP OF INSTITUTIONS :: PUTTUR**  
Siddharth Nagar, Narayanavanam Road – 517583

**QUESTION BANK (DESCRIPTIVE)**

**Subject with Code :** EC-II(15A02301)


**Course & Branch:** B.Tech - EEE

**Year & Sem:** II-B.Tech & I-Sem

**Regulation:** R15

**UNIT-III**  
**TRANSIENT RESPONSE**

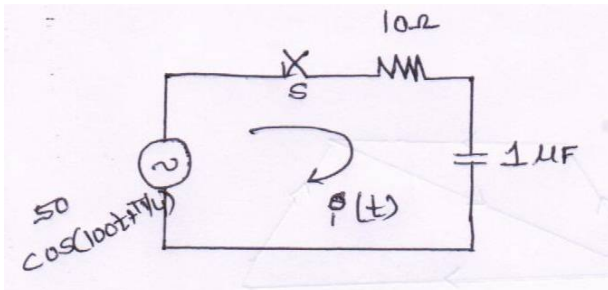1. Derive the transient response of an RL circuit with dc excitation. [10M]
2. Derive the transient response of an RC circuit with dc excitation. [10M]
3. Derive the transient response of an RLC circuit with dc excitation. [10M]
4. Derive the transient response of an RL circuit with Ac excitation. [10M]
5. Derive the transient response of an RLC circuit with AC excitation. [10M]
6. Derive the transient response of an RC circuit with AC excitation. [10M]
7. A series RL circuit with  $R=30\Omega$  and  $L=15H$  has a constant voltage  $V=60V$  applied at  $t=0$ . Determine the current  $I$ , the voltage across the resistor and across the inductor. [10M]
8. A series RC circuit consists of resistor of  $10\Omega$  and capacitor of  $0.1F$  has a constant voltage of  $20v$  is applied to the circuit at  $t=0$ . obtain the current equation. Determine the voltage across the resistor and the capacitor. [10M]
9. In the circuit shown in fig. Determine the complete solution for the current when switch is closed at  $t=0$ , applied voltage is  $V(t)=50\cos(10^2t+\pi/4)$ , resistance  $R=10\Omega$  and capacitance  $c=1\mu F$ . [10M]



- 10.a) Define steady state. [2M]
- b) Define transient state. [2M]
- c) Find the Laplace transform of the function  $f(t) = 4t^3 + t^2 - 6t + 7$ ? [2M]
- d) Find  $L\{\cos^2 t\}$ ? [2M]
- e) What is the transient response of RL series circuit with dc excitation? [2M]



**SIDDHARTH GROUP OF INSTITUTIONS :: PUTTUR**  
Siddharth Nagar, Narayanavanam Road – 517583

**QUESTION BANK (DESCRIPTIVE)**

**Subject with Code :** EC-II(15A02301)


**Course & Branch:** B.Tech - EEE

**Year & Sem:** II-B.Tech & I-Sem


**Regulation:** R15

**UNIT-IV**  
**FOURIER TRANSFORMS**

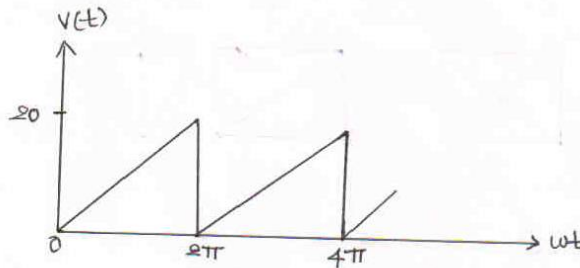
1. Derive the trigonometric form of Fourier series. [10M]
2. Derive the exponential form of Fourier series. [10M]
3. Find Fourier series for the following waveform shown in fig. [10M]



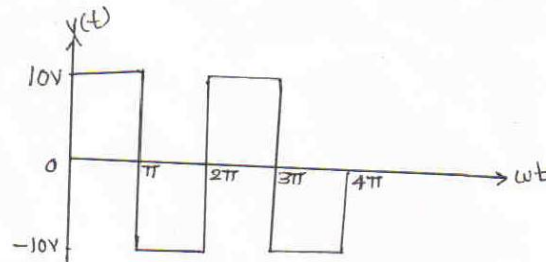
4. Find Fourier series for the following waveform shown in fig. [10M]



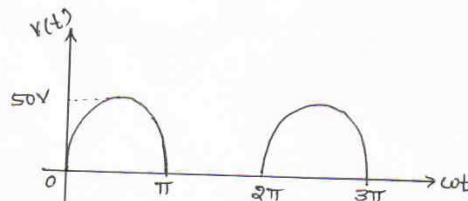5. Find Fourier series for the following waveform shown in fig. and plot the spectrum. [10M]




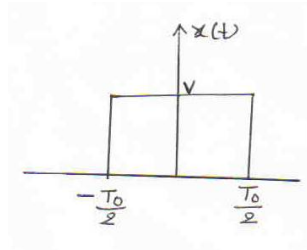6. Write and prove the properties of Fourier transforms? [10M]
7. Determine Fourier transform of the following waveform shown in fig. [10M]




8. Determine Fourier transform of the following waveforms shown in fig.

(a) [5M]

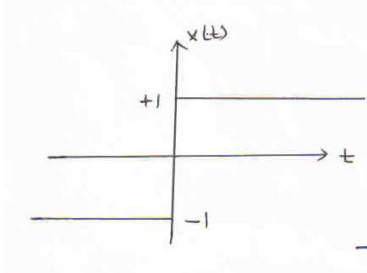


(b) [5M]

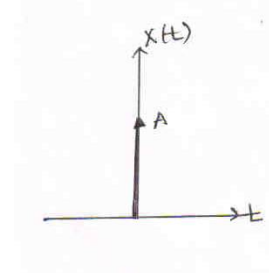


9. Determine Fourier transform of the following waveforms shown in fig.

a) [5M]

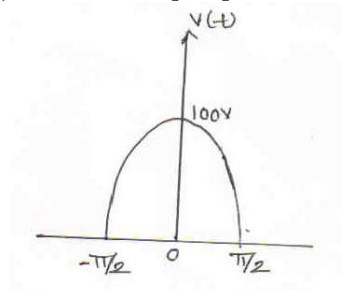

b) [5M]

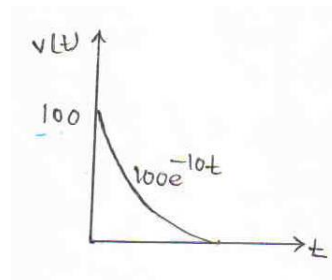

- |   |      |
|---|------|
| 10. a) Write exponential form of Fourier series?  | [2M] |
| b) Define Fourier series.                         | [2M] |
| c) Define Fourier transform.                      | [2M] |
| d) Write trigonometric form of Fourier series?    | [2M] |
| e) Write any two properties of Fourier transform? | [2M] |



**SIDDHARTH GROUP OF INSTITUTIONS :: PUTTUR**  
Siddharth Nagar, Narayanavanam Road – 517583

**QUESTION BANK (DESCRIPTIVE)**

**Subject with Code :** EC-II(15A02301)


**Course & Branch:** B.Tech - EEE

**Year & Sem:** II-B.Tech & I-Sem


**Regulation:** R15

**UNIT-V**  
**FILTERS AND CIRCUIT SIMULATION**

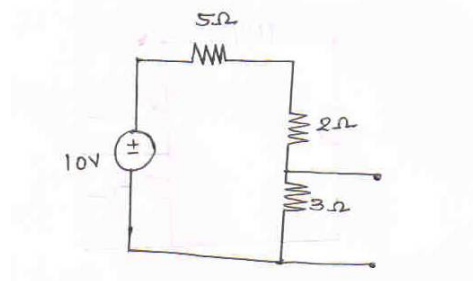1. Explain about different types of filters. [10M]
2. Explain about constant K low pass filter. [10M]
3. Explain about constant K high pass filter. [10M]
4. Design a high pass filter having cut of frequency of 1KHz with load resistance of 600ohms. [10M]
5. Design a low pass filter having cut of frequency of 2KHz with load resistance of 500ohms. [10M]
6. Design a low pass filter having cut of frequency of 5KHz with load resistance of 800ohms. [10M]
7. Design K-type band pass filter having cut of frequency of 2KHz & 10KHz and with load resistance of 500ohms. [10M]
8. Write the PS-PICE program for the circuit shown in fig. to determine voltage across the 3Ω resistor? [10M]



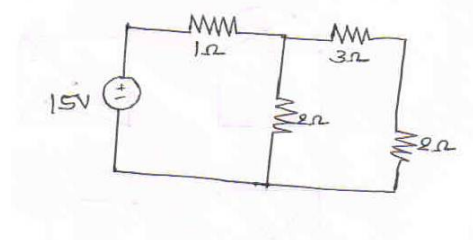9. Write the PS-PICE program for the circuit shown in fig. to determine voltage across the all nodes? [10M]



10. a) Define filter. [2M]
- b) Draw the RC filter. [2M]
- c) Draw the RL filter. [2M]
- d) What is the purpose of using .TRAN statement using in PSPICE program? [2M]
- e) Define PSPICE. [2M]





**SIDDHARTH GROUP OF INSTITUTIONS :: PUTTUR**  
Siddharth Nagar, Narayanavanam Road – 517583

**QUESTION BANK (OBJECTIVE)**

**Subject with Code :** EC-II(15A02301)

**Course & Branch:** B.Tech - EEE

**Year & Sem:** II-B.Tech & I-Sem


**Regulation:** R15

**UNIT – I**


**NETWORK TOPOLOGY**

1. A tree has [     ]  
 A) A closed path B) no closed path  
 C) Path D) none
2. The no. of branches in tree is \_\_\_\_\_ than the no. of branches in a graph. [     ]  
 A) More B) Less than  
 C) Equal D) None
3. The no. of nodes in tree is \_\_\_\_\_ than the no. of nodes in a graph. [     ]  
 A) More B) Less than  
 C) Equal D) None
4. In a plane surface, if there is no two branches cross each other in graph, then the graph is called \_\_\_\_\_. [     ]  
 A) Planar B) Non-planar  
 C) Both A&B D) None
5. Which of the following is a non-planar graph? [     ]

A)

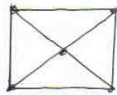

B)

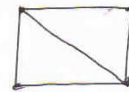

C)



D)



6. Which of the following is a planar graph? [     ]


A)




B)



C)

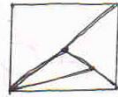

D)

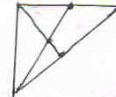

7. In a plane surface, if two branches are cross each other in graph, then the graph is called \_\_\_\_\_ [ ]

- A) Planar  
 B) Non-planar  
 C) Both A&B  
 D) None

8. Planar graph has \_\_\_\_\_ [ ]

- A) Cross over branches  
 B) no cross over branches  
 C) Both A&B  
 D) none

9. Non-Planar graph has \_\_\_\_\_ [ ]

- A) Cross over branches  
 B) no cross over branches  
 C) Both A&B  
 D) none

10. Which of the following statement is correct \_\_\_\_\_ [ ]

- A)  $b=e-1$   
 B)  $b=n-1$   
 C)  $b=n+2$   
 D)  $b=l+2$

11. Which of the following statement is correct \_\_\_\_\_ [ ]

- A)  $l=e-1$   
 B)  $l=b-1$   
 C)  $l=n+2$   
 D)  $l=e-b$

12. The incidence of elements to nodes in a connected graph is shown by \_\_\_\_\_ matrix. [ ]

- A) Cutset  
 B) Tieset  
 C) Incidence matrix  
 D) None

13. Incidence matrix contains \_\_\_\_\_ [ ]

- A) nodes, branches  
 B) nodes, links  
 C) links, nodes  
 D) None

14. The value in the matrix A is positive 1 if \_\_\_\_\_ [ ]

- A) The element is incident to the node  
 B) The element is far away to the node  
 C) The element is not connected to the node  
 D) none

15. The value in the matrix A is negative 1 if \_\_\_\_\_ [ ]

- A) The element is incident to the node  
 B) The element is far away to the node  
 C) The element is not connected to the node  
 D) none

16. The value in the matrix A is 0 if \_\_\_\_\_ [ ]

- A) The element is incident to the node  
 B) The element is far away to the node  
 C) The element is not connected to the node  
 D) none

17. The dimension of incidence matrix is \_\_\_\_\_ [ ]

- A)  $n \times e$   
 B)  $n \times b$   
 C)  $n \times l$   
 D)  $n \times (b-1)$

18. The dimension of incidence matrix is \_\_\_\_\_ [ ]

- A)  $n \times e$   
 B)  $(n-1) \times e$   
 C)  $n \times (e-1)$   
 D)  $(n-1) \times (e-1)$

19. The branches of a tree is called [    ]  
 A) Cord    B) twing  
 C) Both A& B    D)none
20. The links of a tree is called [    ]  
 A) Cord    B) twing  
 C) Both A& B    D)none
21. Which of the following is the property of incidence matrix\_\_\_\_\_ [    ]  
 A) The sum of values in column matrix is zero B) The sum of the values in row matrix is zero  
 C) Both A&B    D) None
22. The tieset schedule gives relation between [    ]  
 A) Branch currents and link currents    B) branch voltages and link currents  
 C) Branch currents and link voltages    D) None
23. The cutset schedule gives relation between [    ]  
 A) Branch currents and link currents    B) branch voltages and link voltages  
 C) Branch voltages and link currents    D) None
24. The no. of possible combinations of trees can be calculated using the formulae. [    ]  
 A)  $\det[BA]$     B)  $\det[AA^T]$   
 C)  $\det[A^T A]$     D)  $\det[BA^T]$
25. The fundamental loop of a tree is called \_\_\_\_\_ [    ]  
 A) Cutset    B) Tieset  
 C) Both A&B    D) None
26. No. of cutsets are equal to the no. of \_\_\_\_\_ of the tree [    ]  
 A) Branch    B) loop  
 C) link    D) None
27. No. of tiesets of a tree is equal to the no. of \_\_\_\_\_ of the tree. [    ]  
 A) Branch    B) loop  
 C) link    D) None
28. The direction of cutset is in the direction of \_\_\_\_\_ of the tree. [    ]  
 A) Branch    B) loop  
 C) link    D) None
29. The direction of tieset is in the direction of \_\_\_\_\_ of the tree. [    ]  
 A) Branch    B) loop  
 C) link    D) None
30. The dimension of tieset matrix is \_\_\_\_\_ [    ]  
 A)  $1 \times e$     B)  $b \times e$   
 C)  $1 \times n$     D)  $n \times 1$
31. The dimension of cutset matrix is \_\_\_\_\_ [    ]  
 A)  $1 \times e$     B)  $b \times e$   
 C)  $1 \times n$     D)  $n \times 1$
32. The no. of cutsets of the below graph is \_\_\_\_\_ [    ]  
 A) 1    B) 2  
 C) 3    D) 4



33. The no. of tiesets of the above graph is \_\_\_\_\_ [     ]  
 A) 1                                      B) 2  
 C) 3                                      D) 4
34. The no. of links of above graph is \_\_\_\_\_ [     ]  
 A) 1                                      B) 2  
 C) 3                                      D) 4
35. The no. of twings of above Graph is \_\_\_\_\_ [     ]  
 A) 1                                      B) 2  
 C) 3                                      D) 4
36. The no. of branches of tree of above graph is \_\_\_\_\_ [     ]  
 A) 1                                      B) 2  
 C) 3                                      D) 4
37. The no. of branches of tree of above graph is \_\_\_\_\_ [     ]  
 A) 1                                      B) 2  
 C) 3                                      D) 4
38. The no. of cords of tree of above graph is \_\_\_\_\_ [     ]  
 A) 1                                      B) 2  
 C) 3                                      D) 4
39. Mesh analysis based on \_\_\_\_\_ [     ]  
 A) KCL                                    B) KVL  
 C) Both                                    D) none
40. Mesh analysis based on \_\_\_\_\_ [     ]  
 A) KCL                                    B) KVL  
 C) Both                                    D) none



**SIDDHARTH GROUP OF INSTITUTIONS :: PUTTUR**  
Siddharth Nagar, Narayanavanam Road – 517583

**QUESTION BANK (OBJECTIVE)**

**Subject with Code :** EC-II(15A02301)

**Course & Branch:** B.Tech - EEE

**Year & Sem:** II-B.Tech & I-Sem

**Regulation:** R15

**UNIT – II**

**THREE PHASE AC CIRCUITS**

1. The voltage between any line and the Neutral point is called \_\_\_\_\_  
[     ] phase  
A) voltage                      B) line voltage  
C) Both A&B  
D) None
2. Phase voltage is \_\_\_\_\_  
[     ]  
A) The voltage between any line and the neutral point  
B) The voltage between R line and the neutral point  
C) The voltage between Y line and the neutral point  
D) The voltage between B line and the neutral point
3. The voltage between any two lines is called \_\_\_\_\_  
[     ]  
A)Phase voltage                      B) line voltage  
C) Both A&B                      D) None
4. The line voltage is \_\_\_\_\_  
[     ]  
A) The voltage between any two lines                      B)The voltage between R and Y lines  
C) The voltage between Y and B lines                      D) The voltage between B and R lines
5. The voltages generated by the 3 phase alternator are \_\_\_\_\_  
[     ]  
A) Same  
    magnitude and different frequency                      B)different magnitude and same frequency  
C) different  
    magnitude and different frequency                      D) same magnitude and same frequency
6. In a three-phase system, the voltages are separated by \_\_\_\_\_  
[     ]  
A) 45<sup>0</sup>  
    B) 90<sup>0</sup>

- C)  $120^\circ$   
D)  $180^\circ$
7. In a three-phase system, when the loads are perfectly balanced, the neutral current is [ ]  
A) Zero  
B) one-third of maximum  
C) two-thirds  
D) at maximum
8. In a certain three-wire Y-connected generator, the phase voltages are 2 kV. The magnitudes of the line voltages are [ ]  
A) 2,000 V  
B) 6,000 V  
C) 666 V  
D) 3,464 V
9. In a  $\Delta$ -connected source driving a  $\Delta$ -connected load, the [ ]  
A) load voltage and line voltage are one-third the source voltage for a given phase  
B) load voltage and line voltage are two-thirds the source voltage for a given phase  
C) load voltage and line voltage cancel for a given phase  
D) load voltage, line voltage, and source phase voltage are all equal for a given phase
10. In a  $\Delta$ -connected source feeding a Y-connected load, [ ]  
A) each phase voltage equals the difference of the corresponding load voltages  
B) each phase voltage equals the corresponding load voltage  
C) each phase voltage is one-third the corresponding load voltage  
D) each phase voltage is  $60^\circ$  out of phase with the corresponding load voltage
11. In a Y-Y source/load configuration, the [ ]  
A) phase current, the line current, and the load current are all equal in each phase  
B) phase current, the line current, and the load current are  $120^\circ$  out of phase  
C) phase current and the line current are in phase, and both are  $120^\circ$  out of phase with the load current  
D) line current and the load current are in phase, and both are out of phase with the phase current
12. In a Y-connected circuit, the magnitude of each line current is [ ]  
A) one-third the phase current  
B) three times the corresponding phase current  
C) equal to the corresponding phase current  
D) zero
13. Polyphase generators produce simultaneous multiple sinusoidal voltages that are separated [ ]  
A) certain constant phase angles  
B) certain constant frequencies  
C) certain constant voltages  
D) certain constant currents
14. Which of the following is unit of current [ ]  
A) ampere  
B) volts  
C) watts  
D) All
15. Which of the following is unit of voltage [ ]

- A) Ampere  
C) watts
- B) volts  
D) All
16. Which of the following is unit of power [     ]  
A) Ampere  
C) watts  
B) volts  
D) all
17. Which of the following is unit of energy [     ]  
A) Ampere  
C) watts  
B) volts  
D) joules
18. What is the units for Active power \_\_\_\_\_ [     ]  
A) KVA  
C) KVAR  
B) KW  
D)none
19. What is the units for Reactive power \_\_\_\_\_ [     ]  
A) KVA  
C) KVAR  
B) KW  
D)none
20. What is the units for Apparent power \_\_\_\_\_ [     ]  
A) KVA  
C) KVAR  
B) KW  
D)none
21. Units of frequency is [     ]  
A) KVA  
C) Hz  
B) KW  
D) none
22. The power in the Delta connected system is [     ]  
A)  $3 V_{ph} I_{ph} \cos \theta$   
C) Both A&B  
B)  $\sqrt{3} V_{ph} I_{ph} \cos \theta$   
D) None
23. The power in the Star connected system is [     ]  
A)  $3 V_{ph} I_{ph} \cos \theta$   
C) Both A&B  
B)  $\sqrt{3} V_{ph} I_{ph} \cos \theta$   
D) None
24. Which of the following statement is correct for star connected load system [     ]  
A)  $V_{ph} = V_L$   
C)  $V_{ph} = \sqrt{3} V_L$   
B)  $I_{ph} = I_L$   
D)  $I_L = \sqrt{3} I_{ph}$
25. Which of the following statement is correct for delta connected load system [     ]  
A)  $V_{ph} = V_L$   
C)  $V_{ph} = \sqrt{3} V_L$   
B)  $I_{ph} = I_L$   
D)  $I_L = \sqrt{3} I_{ph}$
26. In which of the following system, the phase is equal to line voltage [     ]  
A) star  
C) star-delta  
B) delta  
D) delta-star
27. In which of the following system, the line voltage is equal to the phase voltage [     ]  
A) Star  
C) star-delta  
B) delta  
D) delta-star
28. In which of the following system, the line voltage is equal to the  $\sqrt{3}$  times of the phase voltage [     ]  
A) Star  
C) star-delta  
B) delta  
D) delta-star

29. In which of the following system, the line current is equal to the  $\sqrt{3}$  times of the phase current [ ]
- A) Star  
B) Star  
C) star-delta  
D) delta-star
30. A balanced star connected load of  $(4+j3)\Omega$  per phase is connected to a balanced 3 phase 400V supply. The phase current is 12A. What is P.F. of the system [ ]
- A) 0.8 Lag  
B) 0.6 Lag  
C) 0.7 Lag  
D) 0.4 Lag
31. A balanced star connected load of  $(4+j3)\Omega$  per phase is connected to a balanced 3 phase 400V supply. The phase current is 12A. What is total active power [ ]
- A) 6.6 kW  
B) 9.5 kW  
C) 10 kW  
D) 12 kW
32. If in a Y-connected ac generator, each phase voltage has a magnitude of 90 VRMS, what is the magnitude of each line voltage? [ ]
- A) 0V  
B) 90V  
C) 156 V  
D) 180V
33. In a balanced three-phase load, each phase has [ ]
- A) an equal amount of power  
B) one-third of total power  
C) two-thirds of total power  
D) a power consumption equal to  $I_L$
34. In a Y-connected circuit, between each line voltage and the nearest phase voltage, there is a phase angle of [ ]
- A)  $0^\circ$   
B)  $30^\circ$   
C)  $60^\circ$   
D)  $90^\circ$
35. In a certain Y-Y system, the source phase currents each have a magnitude of 9 A. The magnitude of each load current for a balanced load condition is [ ]
- A) 3A  
B) 6A  
C) 9A  
D) 27A
36. In a Y-connected circuit, each line voltage is shifted with \_\_\_ angle of that of phase voltages [ ]
- A)  $30^\circ$  lead  
B)  $30^\circ$  lag  
C)  $60^\circ$  lead  
D)  $60^\circ$  lag
37. In a  $\Delta$ -connected circuit, each line current is shifted with \_\_\_ angle of that of phase currents [ ]
- A)  $30^\circ$  lead  
B)  $30^\circ$  lag  
C)  $60^\circ$  lead  
D)  $60^\circ$  lag
38. Two wattmeter method of power measurement can be used to measure power in [ ]
- A) Balanced circuits  
B) Un-balanced circuits  
C) Both A & B  
D) none
39. Three wattmeter method of power measurement can be used to measure power in [ ]
- A) Balanced circuits  
B) Un-balanced circuits  
C) Both A & B  
D) none
40. Which of the following methods are used to solve the unbalanced 3 wire star connected load [ ]



- A) Star to delta transformation  
 C) Loop method
- B) millimen's theorem  
 D) ALL



**SIDDHARTH GROUP OF INSTITUTIONS :: PUTTUR**  
 Siddharth Nagar, Narayanavanam Road – 517583

**QUESTION BANK (OBJECTIVE)**

**Subject with Code :** EC-II(15A02301)

**Course & Branch:** B.Tech - EEE

**Year & Sem:** II-B.Tech & I-Sem

**Regulation:** R15

**UNIT – III**

**TRANSIENT ANALYSIS**

1. Transient behaviour occurs in any circuit when [ ]  
 A) There are sudden changes of applied voltages B)the voltage source is shorted  
 C) The circuit is connected or disconnected from the supply D) ALL
2. The transient response occurs [ ]

- A) resistance circuit      B) only I inductive circuits      Only in
- C) capacitive circuits      D) both A& B      Only in
3. state current and voltages \_\_\_\_      In steady  
[      ]  
Changes
- A) w.r.t to time      B) doesn't changes w.r.t time
- C)      both A& B
- D) none
4. state current and voltages \_\_\_\_      In transient  
[      ]  
Changes
- A) w.r.t to time      B) doesn't changes w.r.t time
- C)      both A& B
- D) none
5. doesn't allows sudden changes in      Inductor  
[      ]  
Currents
- A)      B) voltages
- C)      Both A &
- B      D) none
6. doesn't allows sudden changes in      Capacitor  
[      ]  
Currents
- A)      B) voltages
- C)      Both A &
- B      D) none
7. allows sudden changes in      Inductor  
[      ]  
Currents
- A)      B) voltages
- C)      Both A &
- B      D) none
8. allows sudden changes      Capacitor  
[      ]  
Currents
- A)      B) voltages
- C)      Both A &
- B      D) none
9. constant of series RL circuit is      The time  
[      ]  
LR
- A)      B) L/R

- C) R/L  
D) ALL
10. The time constant of series RC circuit is [ ]  
A)  $1/RC$   
B)  $R/C$   
C) RC  
D) ALL
11. L/R is time constant of which of the following circuit [ ]  
A) Parallel RC circuit  
B) series RC circuit  
C) Series RL circuit  
D) parallel RL circuit
12. RC is time constant of which of the following circuit [ ]  
A) Parallel RC circuit  
B) series RC circuit  
C) Series RL circuit  
D) parallel RL circuit
13. When series RL circuit is connected to a voltage source V at  $t=0$ , the current passing through the inductor L at  $t=0^+$  is [ ]  
A)  $V/R$   
B) infinity  
C) Zero  
D)  $V/L$
14. When series RL circuit is connected to a voltage source V at  $t=0$ , the current passing through the inductor L at  $t=\infty$  is [ ]  
A)  $V/R$   
B) Infinity  
C) Zero  
D)  $V/L$
15. When series RC circuit is connected to a voltage source V at  $t=0$ , the current passing through the inductor L at  $t=0^+$  is [ ]  
A) Infinity  
B) zero  
C)  $V/R$   
D)  $V/WC$
16. When series RC circuit is connected to a voltage source V at  $t=0$ , the current passing through the inductor L at  $t=\infty$  is [ ]

- A) Infinity  
 B) zero  
 C) V/R  
 D) V/WC
17. When series RC ( $R=10\Omega, C=2\mu\text{F}$ ) circuit is connected to a voltage source V at  $t=0$ , what is the time constant of the network [     ]  
 A) 2 ms  
 B)  $2\ \mu\text{s}$   
 C) 0.2 ms  
 D)  $0.2\ \mu\text{s}$
18. When series RL ( $R=10\Omega, L=5\text{mH}$ ) circuit is connected to a voltage source V at  $t=0$ , what is the time constant of the network [     ]  
 A) 50 ms  
 B)  $50\ \mu\text{s}$   
 C) 5 ms  
 D)  $5\ \mu\text{s}$
19. When series RC ( $R=10\Omega, C=10\mu\text{F}$ ) circuit is connected to a voltage source V at  $t=0$ , the current passing through the inductor L at  $t=0.1\text{ms}$  is [     ]  
 A) Infinity  
 B) zero  
 C) V/R  
 D) V/WC
20. When series RL ( $R=10\Omega, L=10\text{mH}$ ) circuit is connected to a voltage source V at  $t=0$ , the current passing through the inductor L at  $t=0.1\text{s}$  is [     ]  
 A) Infinity  
 B) zero  
 C) V/R  
 D) V/WC
21. The transient current in an RLC circuit is over damped when [     ]  
 A)  $\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$   
 B)  $\left(\frac{R}{2L}\right)^2 = \frac{1}{LC}$   
 C)  $\left(\frac{R}{2L}\right)^2 < \frac{1}{LC}$   
 D) None
22. The transient current in an RLC circuit is under damped when [     ]

- A)  $\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$
- B)  $\left(\frac{R}{2L}\right)^2 = \frac{1}{LC}$
- C)  $\left(\frac{R}{2L}\right)^2 < \frac{1}{LC}$
- D) None
23. The transient current in an RLC circuit is critically damped when
- A)  $\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$
- B)  $\left(\frac{R}{2L}\right)^2 = \frac{1}{LC}$
- C)  $\left(\frac{R}{2L}\right)^2 < \frac{1}{LC}$
- D) None
24. If  $\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$  condition gives \_\_\_\_\_ response in RLC series circuit
- A) damped over
- B) under damped critically
- C) damped critically
- D) none
25. If  $\left(\frac{R}{2L}\right)^2 = \frac{1}{LC}$  condition gives \_\_\_\_\_ response in RLC series circuit
- A) damped over
- B) under damped critically
- C) damped critically
- D) none
26. If  $\left(\frac{R}{2L}\right)^2 < \frac{1}{LC}$  condition gives \_\_\_\_\_ response in RLC series circuit
- A) damped over
- B) under damped critically
- C) damped critically
- D) none
27. The Laplace transform analysis gives \_\_\_\_\_ time
- A) domain response only
- B) frequency response only
- C) Both A & B
- D) NONE
28. The laplace transform o a unit step function is
- A)  $1/S$
- B) 1

- B)  $1/S^2$
- D)  $\frac{1}{S+A}$
29. The laplace transform of a unit ramp function is [     ]
- A)  $1/S$
- B) 1
- C)  $1/S^2$
- D)  $\frac{1}{S+A}$
30. The laplace transform of the first derivative of a function f(t) is [     ]
- A)  $F(S)/S$
- B)  $SF(S)-F(0)$
- C)  $SF(S)-F(0)$
- D)  $F(0)$
31. The laplace transform of the integral of a function f(t) is [     ]
- A)  $F(S)/S$
- B)  $SF(S)-F(0)$
- C)  $SF(S)-F(0)$
- D)  $F'(0)$
32. Laplace transform of the function  $e^{-20t}$  is [     ]
- A)  $\frac{1}{s-20}$
- B)  $s+20$
- C)  $s-20$
- D)  $\frac{1}{s+20}$
33. Laplace transform of  $\cos 2t$  is [     ]
- A)  $\frac{1}{s^2+4}$
- B)  $\frac{1}{s^2-4}$
- C)  $\frac{s}{s^2+4}$
- D)  $\frac{s}{s^2-4}$
34. Laplace transform of  $\sin 4t$  is [     ]
- A)  $\frac{1}{s^2+16}$
- B)  $\frac{1}{s^2-16}$

- C)  $\frac{4}{s^2+16}$
- D)  $\frac{4}{s^2+16}$
35. transform of  $e^{5t}f(t)$  is  
 A)  $F(s)$   
 B)  $F(s-1)$   
 C)  $F(s-5)$   
 D)  $F(s-5)$
36. transform of  $\frac{6}{s^4}$  is  
 A) 3  
 B)  $t^3$   
 C)  $t^2$   
 D)  $3t$
37. laplace of  $\frac{2}{s+3}$  is  
 A)  $2(t+3)$   
 B)  $2e^{-3t}$   
 C)  $e^{-3t}$   
 D)  $2e^{-t}$
38. transform of damped sinewave  $e^{-3t} \sin 50t$  is  
 A)  $\frac{s}{(s+3)^2+50^2}$   
 B)  $\frac{50}{(s+3)^2+50^2}$   
 C)  $\frac{50}{(s+3)^2+50^2}$   
 D)  $\frac{50^2}{(s+3)^2+50^2}$
39. value of  $\frac{2s+1}{s^2+8s^2+16s^2+s}$  is  
 A) 2  
 B) infinity  
 C) zero  
 D) 1
40. value of  $20-10t-e^{-25t}$  is  
 A) 20  
 B) 19  
 C) 10  
 D) 25

$$\frac{4}{s^2+16}$$

The laplace  
[ ]  
 $F(s)$

$F(s/5)$

The inverse  
[ ]

3

$t^2$

The inverse  
[ ]

$2(t+3)$

$e^{-3t}$

Laplace  
[ ]

$$\frac{s}{(s+3)^2+50^2}$$

$$\frac{50}{(s+3)^2+50^2}$$

The initial  
[ ]

2

zero

The initial  
[ ]

20

10



**SIDDHARTH GROUP OF INSTITUTIONS :: PUTTUR**

Siddharth Nagar, Narayanavanam Road – 517583

**QUESTION BANK (OBJECTIVE)**

**Subject with Code :** EC-II(15A02301)

**Course & Branch:** B.Tech - EEE

**Year & Sem:** II-B.Tech & I-Sem

**Regulation:** R15

**UNIT – IV**

**FOURIER TRANSFORMS**

1. Fourier series for the signal  $e^{-at}$  does not exist if [     ]  
A)  $a \geq 0$                       B)  $a = 0$   
C)  $a = 1$                         D)  $a < 0$
2. The Fourier transform [     ]  
A) satisfies linearity        B) does not satisfies linearity  
C) both A & B                D) none
3. Fourier transform of the unit impulse  $\delta(t)$  is [     ]



- A) 0                      B)  $\pi$   
C) 1                      D)  $\delta(w)$
4. What is the spectrum of a dc signal [    ]  
A) 0                      B)  $\pi$   
C)  $2\pi$                       D)  $2\pi\delta(w)$
5. The Fourier transform exist ,if the following condition is satisfied [    ]  
A)  $\int_{-\infty}^{\infty} |f(t)| dt > K$       B)  $\int_{-\infty}^{\infty} |f(t)| dt < \infty$   
C)  $\int_{-\infty}^{\infty} |f(t)| dt = 0$       D) none
6. Inverse Fourier transform of  $\delta(w-w_0)$  [    ]  
A)  $\frac{1}{2\pi} e^{-jw_0 t}$               B)  $\frac{1}{2\pi}$   
C)  $e^{-jw_0 t}$                       D)  $e^{jw_0 t}$
7. The Fourier transform of signal x(t) is [    ]  
A)  $-x(w)$                       B)  $x(-w)$   
C)  $-x(-w)$                       D)  $x(w)$
8. The Fourier transform of  $\sin(t)$  function is [    ]  
A)  $\frac{2}{jw}$                       B)  $\frac{2}{jw}$   
C)  $jw$                       D)  $2jw$
9. Time convolution property states that [    ]  
A)  $F_1(t)*F_2(t)$               B)  $F_1(t)F_2(t)$   
C)  $F_1(w)*F_2(w)$               D)  $F_1(w)/F_2(w)$
10. The frequency convolution property states that [    ]  
A)  $F_1(t)*F_2(t)$               B)  $F_1(t)F_2(t)$   
C)  $F_1(w)*F_2^*(w)$               D)  $F_1(w)/F_2(w)$
11. In a periodic signal, The period  $T_0$  is doubled, the fundamental frequency  $w_0$  in the spectrum becomes [    ]  
A) Doubled                      B) halved  
C) Increased 4 times              D) no change
12. Any periodic function can be expressed by a Fourier series when the function having[    ]  
A) Infinite number of finite discontinuities in a period  
B) finite number of finite discontinuities in a period  
C) finite number of infinite discontinuities in a period  
D) Infinite number of infinite discontinuities in a period
13. A function is said to be even, if x(t) is [    ]

- A)  $x(-t)$                       B)  $-x(t)$   
 C)  $x(2t)$                       D)  $x(t)$
14. A function is said to be even, if  $x(t)$  is [      ]  
 A)  $x(-t)$                       B)  $-x(t)$   
 C)  $x(2t)$                       D)  $x(t)$
15. If  $x(-t)=x(t)$  then the function is called [      ]  
 A) Odd function              B) even function  
 C) Both A & B              D) none
16. If  $x(-t)=-x(t)$  then the function is called [      ]  
 A) Odd function              B) even function  
 C) Both A & B              D) none
17. Identify the even function [      ]  
 A) Cosine                      B) sine  
 C) Both A&B              D) none
18. Identify the odd function [      ]  
 A) Cosine                      B) sine  
 C) Both A&B              D) none
19. A periodic function  $x(t)$  is said to have half wave symmetry if  $x(t)$  is [      ]  
 A)  $-x(t+\frac{T}{2})$                       B)  $x(t+\frac{T}{2})$   
 C)  $-x(t-\frac{T}{2})$                       D)  $-x(t-\frac{T}{2})$
20. The Fourier transform of a conjugate symmetric function is always [      ]  
 A) imaginary                      B) conjugate anti-symmetric  
 C) real                              D) conjugate symmetric
21. The Fourier transform may be applied to [      ]  
 A) Non-periodic                      B) Periodic  
 C) Both periodic & non-periodic      D) Neither periodic or non-periodic
22. The Fourier transform of  $u(t)$  is [      ]  
 A)  $\frac{1}{j\omega}$                               B)  $j\omega$   
 C)  $\frac{1}{1+j\omega}$                               D)  $\pi\delta(\omega) + \frac{1}{j\omega}$
23. The Fourier transform of  $e^{-\alpha t}u(t)$  is [      ]  
 A)  $\frac{1}{\alpha-j\omega}$                               B)  $\frac{1}{\alpha+j\omega}$   
 C)  $\frac{1}{\alpha^2+\omega^2}$                               D)  $\frac{1}{\alpha^2-\omega^2}$

24. The Fourier transform of  $tx(t)$  is [     ]

- A)  $\frac{dX(j\omega)}{d\omega}$                       B)  $j \frac{dX(j\omega)}{d\omega}$   
 C)  $\frac{X(j\omega)}{\omega}$                       D)  $\frac{j dX(j\omega)}{d\omega}$

25. The Fourier transform of  $e^{-j\omega_0 t} x(t)$  is [     ]

- A)  $X(\omega + \omega_0)$                       B)  $X(\omega_0)$   
 C)  $X(\omega - \omega_0)$                       D)  $X(\frac{\omega}{\omega_0})$

26. The Fourier transform of  $x^*(t)$  is [     ]

- A)  $X^*(\omega)$                       B)  $X^*(-\omega)$   
 C)  $-X^*(\omega)$                       D)  $-X^*(-\omega)$

27. The Fourier transform of  $\frac{dx(t)}{dt}$  is [     ]

- A)  $\frac{d\omega}{\omega} X(\omega)$                       B)  $\frac{1}{\omega} X(\omega)$   
 C)  $j\omega X(\omega)$                       D)  $\frac{j\omega}{X(\omega)}$

28. The Fourier transform of  $x(at)$  is [     ]

- A)  $\frac{1}{|a|} X\left(\frac{\omega}{a}\right)$                       B)  $\frac{1}{|a|} X(a\omega)$   
 C)  $\frac{1}{|a|} X\left(\frac{\omega}{a}\right)$                       D)  $\frac{1}{|a|} X\left(\frac{\omega}{a}\right)$

29. The Fourier series may be applied to [     ]

- A) Non-periodic                      B) Periodic  
 C) Both periodic & non-periodic    D) Neither periodic or non-period

30. Periodic signal are analyzed by using [     ]

- A) Fourier series                      B) Fourier transforms  
 C) Both A&B                      D) none

31. Non-Periodic signal are analyzed by using [     ]

- A) Fourier series                      B) Fourier transforms  
 C) Both A&B                      D) none

32. If the signals can be represented by sum of the sinusoids whose frequencies are integral multiple of fundamental frequency is called [     ]

- A) Non-periodic                      B) Periodic  
 C) Both periodic & non-periodic    D) Neither periodic or non-period

33. If the signals can be represented by sum of the sinusoids whose frequencies are not integral multiple of fundamental frequency is called [     ]

- A) Non-periodic                      B) Periodic

- C) Both periodic & non-periodic    D) Neither periodic or non-period
34. Fourier series can be represented as [    ]  
 A) Trigonometric form                      B) exponential form  
 C) Both A & B                                  D) none
35. Series coefficient  $a_0$  in Fourier series can be calculated using [    ]  
 A)  $\frac{1}{2\pi} \int_0^{2\pi} x(t) d(\omega t)$                       B)  $\frac{1}{2\pi} \int_0^{2\pi} x(t) d(\omega t)$   
 C)  $\frac{1}{2\pi} \int_{-\pi}^{\pi} x(t) d(\omega t)$                       D)  $\frac{1}{2\pi} \int_{-\pi}^{\pi} x(t) d(\omega t)$
36. Series coefficient  $a_n$  in Fourier series can be calculated using [    ]  
 A)  $\frac{1}{\pi} \int_0^{\pi} x(t) d(\omega t)$                       B)  $\frac{1}{\pi} \int_0^{2\pi} x(t) \cos n\omega t d(\omega t)$   
 C)  $\frac{1}{\pi} \int_0^{2\pi} x(t) \sin n\omega t d(\omega t)$                       D)  $\frac{1}{\pi} \int_{-\pi}^{\pi} x(t) \cos n\omega t d(\omega t)$
37. Series coefficient  $b_n$  in Fourier series can be calculated using [    ]  
 A)  $\frac{1}{\pi} \int_0^{\pi} x(t) d(\omega t)$                       B)  $\frac{1}{\pi} \int_0^{2\pi} x(t) \cos n\omega t d(\omega t)$   
 C)  $\frac{1}{\pi} \int_0^{2\pi} x(t) \sin n\omega t d(\omega t)$                       D)  $\frac{1}{\pi} \int_{-\pi}^{\pi} x(t) \cos n\omega t d(\omega t)$
38. Which of the following is a periodic signal [    ]  
 A)  $x(t)$     B)  $x(t+T)$   
 C)  $x(2t)$     D)  $x(\omega)$
39. Parseval's identity states that  $\int_{-\infty}^{\infty} |f(t)|^2 dt =$  [    ]  
 A)  $\int_{-\infty}^{\infty} X_1(\omega) X_2^*(\omega) d\omega$                       B)  $\frac{1}{2\pi} \int_{-\infty}^{\infty} X_1(\omega) X_2^*(\omega) d\omega$   
 C)  $\frac{1}{2\pi} \int_{-\infty}^{\infty} X_1^*(\omega) X_2(\omega) d\omega$                       D)  $2\pi \int_{-\infty}^{\infty} X_1(\omega) X_2^*(\omega) d\omega$
40. The Fourier transform of  $x_1(n) * x_2(n)$  is [    ]  
 A)  $X_1(\omega) X(\omega)$                               B)  $X_1(\omega) X_2(\omega)$   
 C)  $X_1(\omega) * X_2(\omega)$                               D) Does not exist



**SIDDHARTH GROUP OF INSTITUTIONS :: PUTTUR**  
Siddharth Nagar, Narayanavanam Road – 517583

**QUESTION BANK (OBJECTIVE)**

**Subject with Code :** EC-II(15A02301)

**Course & Branch:** B.Tech - EEE

**Year & Sem:** II-B.Tech & I-Sem

**Regulation:** R15

**UNIT – V**

**FILTERS AND CIRCUITS SIMULATION**

1. filter is one which A low  
[    ]  
 A) Passes all  
 low frequencies B) attenuates all high frequencies  
 C) passes all  
 frequencies up to cut-off frequency and attenuates all other frequencies D) none
2. filter is on which A high pass  
[    ]  
 A) Passes all  
 high frequencies

- B) attenuates  
all low frequencies
- C) Attenuates  
all frequencies below a designated cut-off frequency, and passes all frequencies above cut off
- D) none  
A band
3. stop filter is one which [     ]
- A) Attenuates  
frequencies between two designed cut off frequencies and passes all other freq
- B) Passes  
frequencies between two designated cut off frequencies and attenuates all other frequencies
- C) Passes all  
frequencies
- D) None
4. An ideal filter should have [     ]
- A) Zero  
attenuation in pass band                      B)infinite attenuation in pass band
- C) Zero  
attenuation in attenuation band            D)infinite attenuation in attenuation band
5. The propagation constant of a symmetrical T-section and  $\pi$ -section are [     ]
- A) Same  
B) not same
- C) Equal to 1  
D) equal to zero
6. A line work as [     ]
- A) attenuator  
B) LPF
- C) HPF  
D) neither of the above
7. Attenuation is expressed in [     ]
- A) Decibels  
B) nepers
- C) Both  
D)none
8. Attenuation distortion occurs due to [     ]
- A) Non  
uniform attenuation against frequency    B)uniform attenuation against frequency
- C) Non  
uniform attenuation against time            D)uniform attenuation against time

9. Decibel is unit of which of the following [    ]  
 A) Attenuation  
 B) transient  
 C) Power  
 D) energy
10. Neper is unit of which of the following [    ]  
 A) Attenuation  
 B) transient  
 C) Power  
 D) energy
11. The natural logarithm of ration of input voltage( or current) to output voltage(or current) is called [    ]  
 A) Decibel  
 B) neper  
 C) Power  
 D) voltage ratio
12. \_\_\_\_\_ Is defined as 10 times of the ratio of input voltage(( or current) to output voltage(or current) is called [    ]  
 A) Decibel  
 B) neper  
 C) Power  
 D) voltage ratio
13. \_\_\_\_\_ Is defined as 10 times of the ratio of input power to output power [    ]  
 A) Decibel  
 B) neper  
 C) Power  
 D) voltage ratio
14. One decibel is equal to \_\_\_\_\_ neper [    ]  
 A) 1.115  
 B) 0.115  
 C) 2.113  
 D) 5.115
15. One neper is equal to \_\_\_\_\_ decibels [    ]  
 A) 8.009  
 B) 8.69  
 C) 9.69  
 D) 10.69
16. The critical frequency is defined as the point at which the response drops\_\_\_\_ from the pass band [    ]  
 A) -20 dB  
 B) -3 dB  
 C) -6 dB  
 D) -40 dB
17. \_\_\_\_\_ filter passes all frequencies within a band between a lower and an upper critical frequency and rejects all others outside this band. [    ]  
 A) low-pass  
 B) high pass  
 C) band pass  
 D) band stop
18. A third-order filter will have a roll-off rate of [    ]  
 A) -20 dB/decade  
 B) -40 dB/decade  
 C) -60 dB/decade  
 D) -80 dB/decade
19. A network designed to pass signals with all frequencies except those between two specified cut-off frequencies is called a [    ]  
 A) low-pass  
 B) high pass  
 C) band pass  
 D) band stop
20. A network designed to pass signals at frequencies above a specified cut-off frequency is called a [    ]  
 A) low-pass  
 B) high pass

C) band pass

D)band stop

21. A network designed to pass signals at frequencies below a specified cut-off frequency is called a [    ]

A) low-pass

B)high pass

C) band pass

D)band stop

22. A network designed to pass signals with frequencies between two specified cut-off frequencies is called a [    ]


A) low-pass

B)high pass


C) band pass

D)band stop

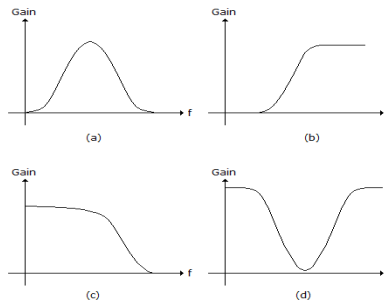
23. Identify the frequency response curve for a band-pass filter. [    ]



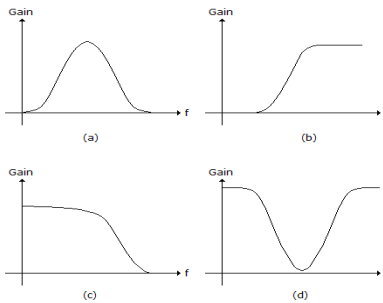24. Identify the frequency response curve for a low-pass filter [    ]




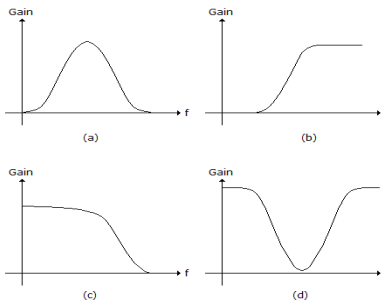25. Identify the frequency response curve for a high-pass filter [    ]



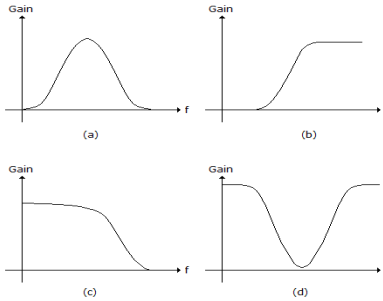26. Identify the frequency response curve for a band-stop filter [    ]





27. A point in network or diagram at which paths or line intersects is called\_\_\_\_\_ [  ]
- A) Branch
  - B) node
  - C) element
  - D) ALL
28. The interconnection of nodes is called [  ]
- A) Branch
  - B) node
  - C) element
  - D)ALL
29. The element which delivers power is called [  ]
- A) Load
  - B) source
  - C) Both
  - D) none
30. The element which consumes power is called [  ]
- A) Load
  - B)source
  - C) Both
  - D)none
31. Which of the following is passive element [  ]
- A) Current source
  - B) voltage source
  - C) Power
  - D) resistor
32. Which of the following is active element [  ]
- A) Power
  - B) resistor
  - C) Voltage source
  - D) diode
33. The maximum output voltage of a certain low-pass filter is 15 V. The output voltage at the critical frequency is [  ]
- A) 0 V
  - B) 15 V
  - C) 10.60 V
  - D) 21.21 V
34. A practical voltage source consists of [  ]
- A) an ideal voltage source in series with an internal resistance
  - B) an ideal voltage source in parallel with an internal resistance
  - C) both (A) and (B) are correct
  - D) none of the above
35. A practical current source consists of [  ]
- A) an ideal current source in series with an internal resistance
  - B) an ideal current source in parallel with an internal resistance
  - C) both (A) and (B) are correct
  - D) none of the above
36. Which of the following is dependent is not a dependent source [  ]
- A) CCVS
  - B) VCCS
  - C) VCCS
  - D) VCDS

37. Which of the following statement is used to calculate all node voltages and reference node voltage [      ]
- A) .TRAN    B) .OP  
C) .END    D) .PRINT
38. Which of the following statement is used to provide graphical capacity of PSpice [      ]
- A) .TRAN    B) .OP  
C) .PROB    D) .PRINT
39. Which of the following statement is used for outputs of PSpice [      ]
- A).TRAN    B) .OP  
C) .END    D) .PRINT
40. Which of the following statement is used to specifies the time interval over which transient analysis takes place of PSpice [      ]
- A) .TRAN    B) .OP  
C) .END    D) .PRINT

Prepared by **B.JAYANTHI**