



**SIDDHARTH GROUP OF INSTITUTIONS :: PUTTUR
(AUTONOMOUS)**

Siddharth Nagar, Narayanavanam Road – 517583

QUESTION BANK (DESCRIPTIVE)

Subject with Code : NETWORK THEORY(19EE0242) Course & Branch: B.Tech - ECE

Year & Sem: II-B.Tech & I-Sem

Regulation: R19


UNIT –I

CIRCUIT ANALYSIS TECHNIQUES

1. a) Explain about Nodal analysis and write the steps for applying nodal analysis.
b) Determine the mesh currents for the following network.

[L2][CO1][5M]


[L4][CO1][5M]

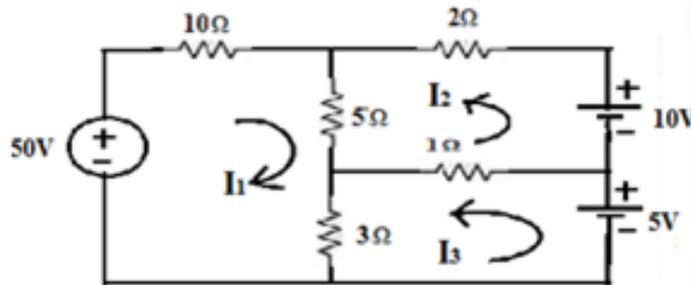

2. a) Explain about Mesh analysis and write the steps for writing mesh analysis.
b) Determine the current in 10Ω resistor for the following network by using nodal analysis.


[L2][CO1][5M]

[L4][CO1][5M]

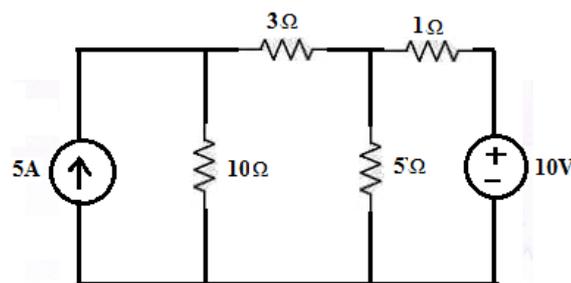

3. a) Determine i_x for the following network.

[L4][CO1][5M]

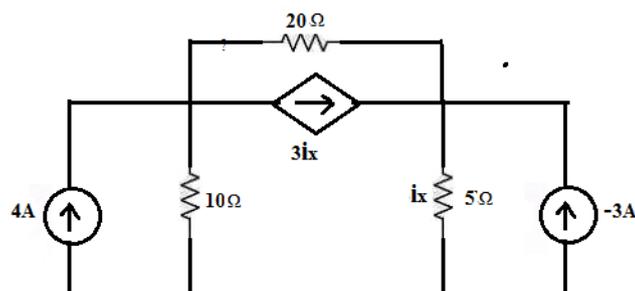

- b) Explain about source transformation briefly.


[L2][CO1][5M]

4. a) State and prove Tellegen's theorem.

[L2][CO2][5M]

b) Determine the equivalent current source between the terminals A and B.

[L4][CO1][5M]

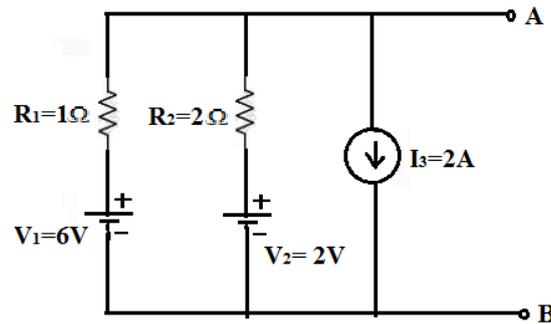


5. a) State and prove Reciprocity theorem.

[L2][CO2][5M]

b) Determine the mesh currents for the circuit shown in below figure.


[L4][CO1][5M]

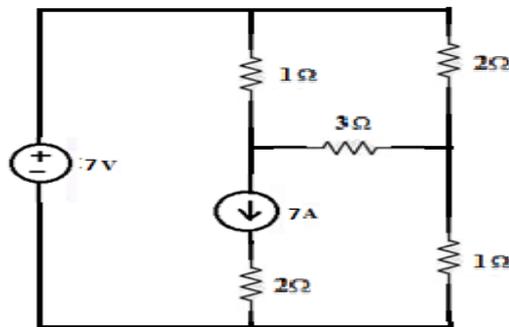

6. a) Explain about Super Nodal analysis and write the steps for applying nodal analysis. [L2][CO1][5M]

b) Calculate the current 'I' shown in below figure by using Milliman's theorem. [L4][CO2][5M]

[L4][CO2][5M]

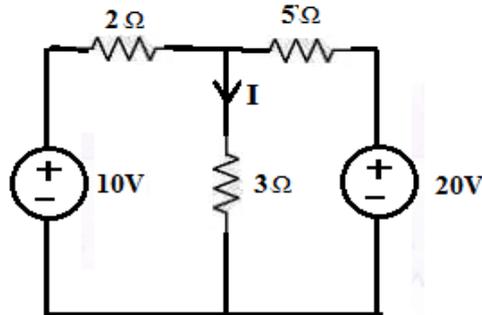


7. a) State and prove Compensation theorem.

[L2][CO2][5M]

b) Verify Tellegen's theorem for the circuit shown in below figure.

[L4][CO2][5M]

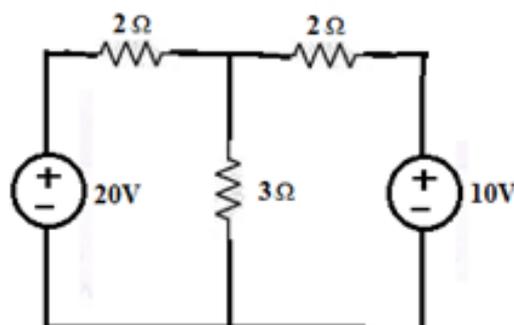


8. a) State and prove Milliman's theorem.

[L2][CO2][5M]


b) Verify reciprocity theorem for the network shown in below figure.

[L4][CO2][5M]

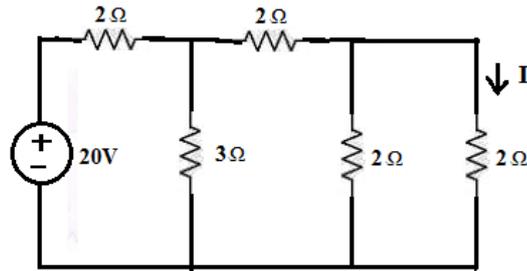


9. a)) Find the current I_L , use millman's theorem as shown in figure below.

[L4][CO2][5M]

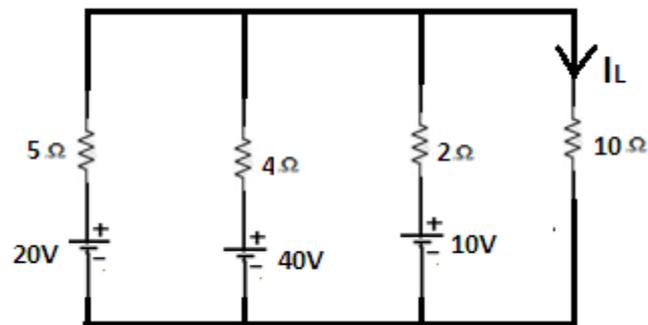

b) Determine the ammeter reading where it is connected to 6Ω resistor as shown in below figure. The internal resistance of the ammeter is 2Ω ., by using compensation theorem.

[L4][CO2][5M]

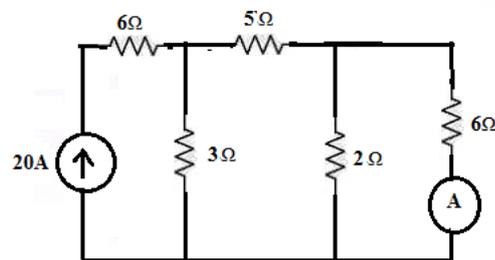

10. a) Write statement of millman's theorem .

[L1][CO2][2M]

b) Define Super node and Super mesh.

[L1][CO1][2M]

c) Write statement of Reciprocity theorem.

[L1][CO2][2M]

d) Write statement of Tellegen's theorem.

[L1][CO2][2M]


e) Draw a circuit diagram of voltage source to current source by using source transformation.

[L1][CO1][2M]


UNIT-II

RESONANCE AND FILTERS

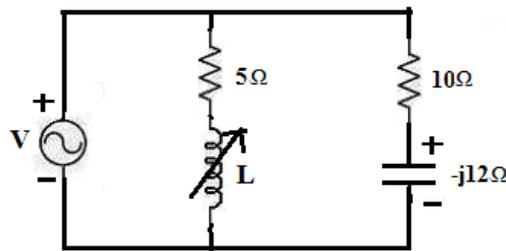
1. a) A series RLC circuit has $R=10\Omega$, $L=0.1\text{H}$ and $C=50\mu\text{F}$. The applied voltage is 100V. Find Resonant frequency & Quality factor of a coil. [L4][CO1][5M]
- b) Explain about Series resonance with phasor diagrams. [L2][CO1][5M]
2. a) Explain about Parallel resonance with phasor diagrams. [L2][CO1][5M]
- b) Find the value of 'L' at which the circuit resonates at a frequency of 1000 rad/sec in the circuit shown in figure. [L4][CO1][5M]



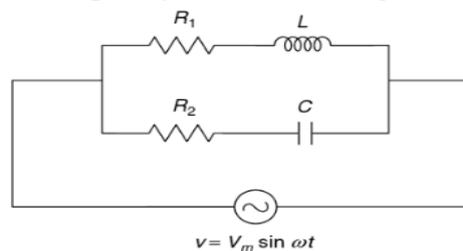3. a) Explain about Quality factor and Band-width of Series resonance. [L2][CO1][6M]
- b) Design constant-K band pass filter having a design impedance of 500Ω and cut-off frequencies $f_1=1\text{kHz}$ and $f_2=10\text{kHz}$. [L4][CO6][4M]
- 4.a) Derive the expression of resonant Frequency of the following circuit. [L4][CO1][5M]



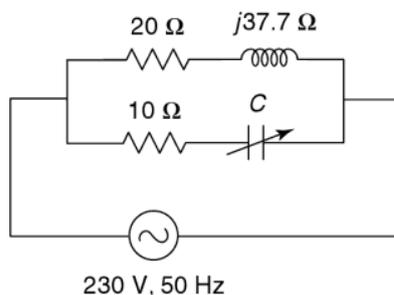- b) Find the value of C in the circuit shown to get resonance. [L4][CO1][5M]




5. a) Explain about classification of filters. [L2][CO6][4M]
- b) Explain about Propagation constant and Characteristic impedance in T-network filters. [L2][CO6][6M]
6. a) Explain about Propagation constant and Characteristic impedance in Π -network filters. [L2][CO6][6M]
- b) Design Low Pass Filter in both T & Π section having a cut off frequency of 2KHz to operate with a terminated load resistance of 500Ω . [L2][CO6][4M]
7. Explain about Constant-K low-pass filter in detail. [L3][CO6][10M]
8. a) Design a High-pass filter having a cut-off frequency of 1kHz with a load resistance of 600Ω . [L4][CO6][5M]

- b) Design a Band-elimination filter having design impedance of 600Ω and cut-off frequencies $f_1 = 2\text{kHz}$ and $f_2 = 6\text{kHz}$. [L4][CO6][5M]
9. Explain about Constant-K band-pass filter in detail. [L3][CO6][10M]
10. a) Define Quality-factor and Selectivity. [L1][CO3][2M]
- b) Define Neper and Decibel. [L1][CO6][2M]
- c) Draw the block diagram of band-pass and band-elimination filters. [L1][CO6][2M]
- d) Draw the characteristics of Low-pass and High-pass filters. [L1][CO6][2M]
- e) Define Resonance and Resonant frequency. [L1][CO3][2M]


UNIT-III

TRANSIENT ANALYSIS

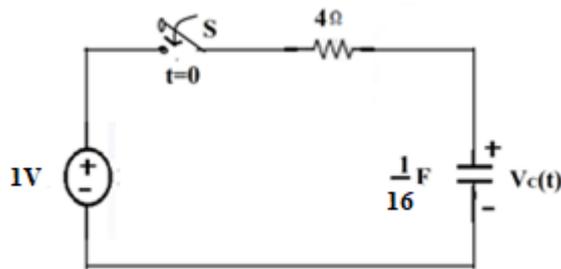1. a) Derive the Transient Response of series RL-circuit with D.C excitation. [L2][CO3][6M]
- b) Determine The Current I for $T > 0$ If $V_c(0) = 9\text{V}$ For The Circuit Shown In Fig. [L2][CO3][4M]



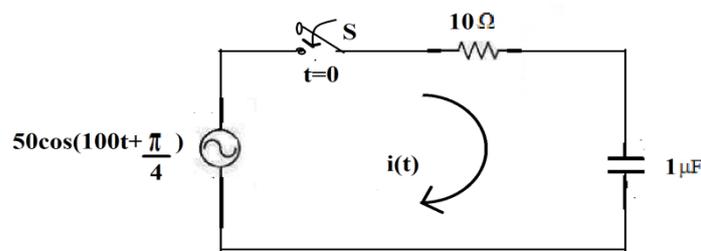2. a) Derive the Transient Response of series RC-circuit with D.C excitation. [L2][CO3][5M]
- b) The Circuit Consists Of Resistance=20 Ohm, Inductance = 0.05H, Capacitance = 20μF in Series With a 100V Constant at $t=0$. Find The Current Transient. [L4][CO3][5M]
3. Derive the Transient Response of series RLC-circuit with D.C excitation. [L2][CO3][10M]
4. a) Derive the Laplace Transform of Series RL Circuit . [L2][CO3][5M]
- b) A series RC circuit consists of a resistor of 10Ω and capacitor of 0.1 F with a constant voltage of 20v, is applied to the circuit at $t=0$. Obtain the current equation. Determine the voltage across the resistor and the capacitor. [L4][CO3][5M]
5. Derive the Transient Response of Series RL circuit with Sinusoidal excitation. [L2][CO3][10M]
6. a) In the circuit shown in figure, determine the complete solution for the current when switch is closed at $t=0$, applied voltage is $V(t) = 50 \cos(10^2 t + \pi/4)$, resistance $R = 10\Omega$ and capacitance $C = 1\mu\text{F}$. [L4][CO3][5M]




- b) A voltage $V = 300\sin(314t)$ is applied at $t = 2.14\text{msec}$ to a series RC circuit having resistance of 10Ω and a capacitance of $200\mu\text{F}$. Find an expression for current. Also, find the value of current 1msec after Switching-On. [L4][CO3][5M]

7. Derive the Transient Response of Series RLC circuit with Sinusoidal excitation. [L2][CO3][10M]
8. a) Derive the Laplace Transform of Series RC Circuit. [L2][CO3][5M]
 b) A series RL circuit with $R=30\Omega$ and $L=15H$ has a constant voltage $V=60v$ applied at $t=0$.
 Determine the current "I", voltage across resistor and voltage across inductor. [L4][CO3][5M]
9. Derive the Transient Response of Series RC circuit with A.C excitation. [L2][CO3][10M]
10. a) Define steady state and transient state [L1][CO3][2M]
 b) What are the initial conditions? Explain briefly. [L1][CO3][2M]
 c) What is the transient response of series RL and RC circuits with D.C excitation? [L1][CO3][2M]
 d) What is the behavior of Inductor in Initial and Steady state conditions? [L1][CO3][2M]
 e) What is the behavior of Capacitor in Initial and Steady state conditions? [L1][CO3][2M]


UNIT-IV

TWO PORT NETWORKS

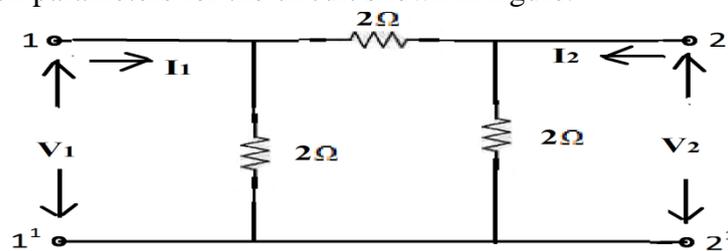
1. a) Explain about Impedance parameters. [L2][CO5][5M]
 b) Find the transmission parameters for the circuit shown in figure. [L4][CO5][5M]



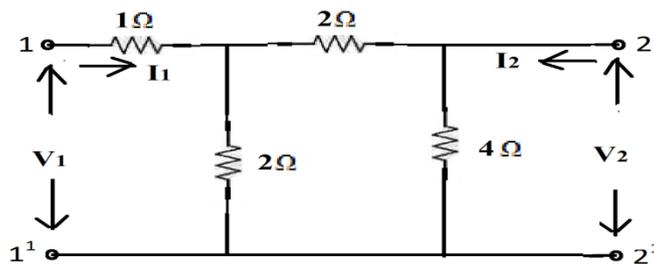
2. a) Explain about short-circuit parameters. [L2][CO5][5M]
 b) Find the h-parameters of the network shown in figure. [L4][CO5][5M]



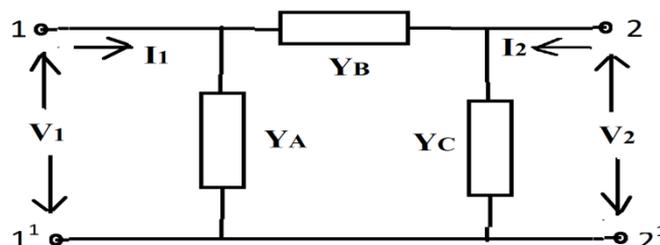
3. a) Explain about h-parameters in terms of y-parameters. [L2][CO5][5M]
 b) Find the Short-circuit parameters for the circuit shown in figure. [L4][CO5][5M]



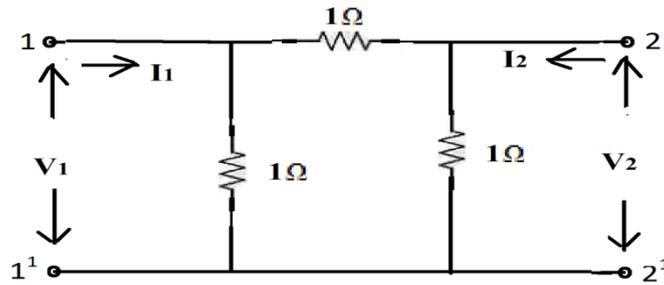
4. a) Explain about ABCD-parameters. [L2][CO5][5M]
 b) Find the Z-parameters of the network shown in below figure. [L4][CO5][5M]



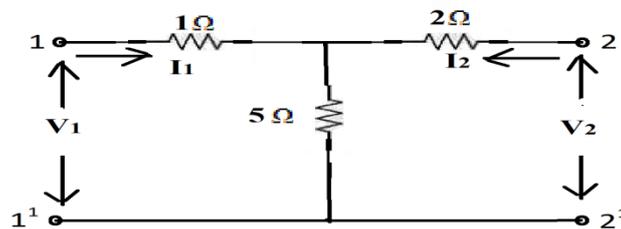
5. a) Derive the expressions for Chain parameters in terms of Z-parameters. [L2][CO5][4M]
 b) The Z-parameters of a two-port network are $Z_{11}=10\Omega$, $Z_{22}=15\Omega$, $Z_{12}=5\Omega$ and $Z_{21}=5\Omega$. Find the equivalent T-network and ABCD parameters. [L2][CO5][6M]
 6. a) Find the transmission parameters for the circuit shown in figure. [L4][CO5][5M]



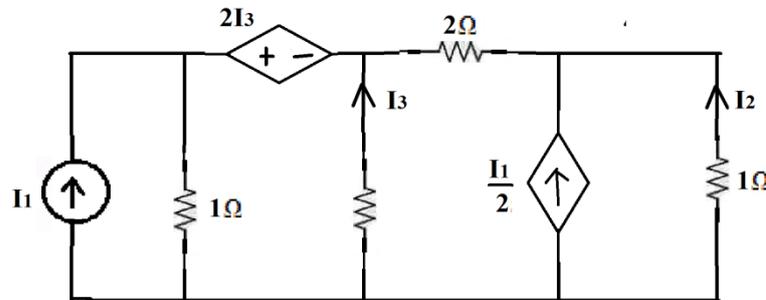- b) The hybrid parameters of a two-port network is shown in figure are, $h_{11}=1K$, $h_{12}=0.003$, $h_{21}=100$ and $h_{22}=50\mu\Omega$. Find V_2 and Z-parameters of the network. [L4][CO5][5M]
 7. a) Derive the expressions for Z-parameters in terms of ABCD-parameters. [L2][CO5][5M]
 b) Find the current transfer ratio I_2/I_1 for the network shown on figure. [L2][CO5][5M]



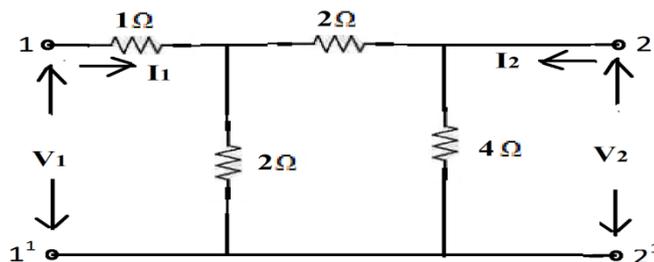8. a) Derive the expressions for Y-parameters in terms of ABCD parameters. [L2][CO5][5M]
 b) Determine the y-parameters of the following network. [L4][CO5][5M]



9. a) The given ABCD parameters are, $A=2$, $B=0.9$, $C=1.2$, $D=0.5$. Find Y-parameters. [L4][CO5][5M]
 b) The given Y-parameters are, $Y_{11}=0.5$, $Y_{12}=Y_{21}=0.6$, $Y_{22}=0.9$. Find Z-parameters. [L4][CO5][5M]
 10. a) Define Two-port network. [L1][CO5][2M]
 b) Draw the equivalent circuit of Z-parameters. [L1][CO5][2M]
 c) What is the condition for Symmetry in Z and Y parameters? [L1][CO5][2M]

- d) What is the condition for Reciprocity in Z and Y parameters?
 e) Write the equations for Z-parameters in terms of Y-parameters.

[L1][CO5][2M]


[L1][CO5][2M]

UNIT-V
FOURIER TRANSFORMS

1. a) Derive the Trigonometric form of Fourier series.
 b) Find the Fourier series for the following waveform.

[L2][CO4][5M]


[L4][CO4][5M]

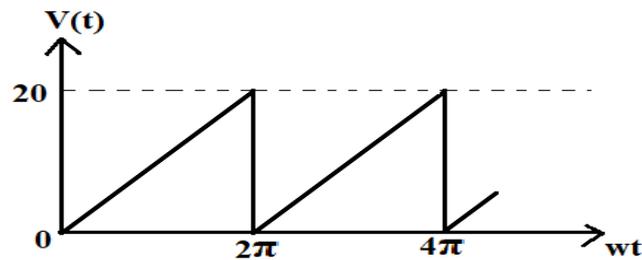


2. a) Derive the Exponential form of Fourier series.
 b) Obtain the Fourier series for the following waveform shown in figure.

[L2][CO4][5M]

[L4][CO4][5M]

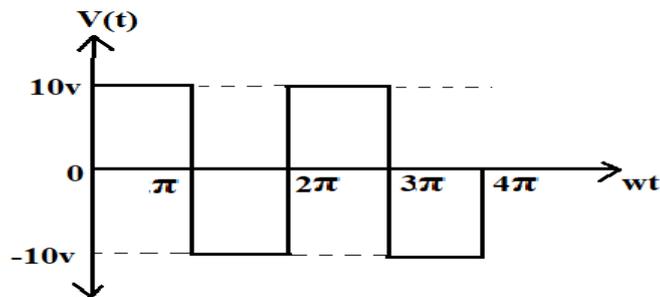


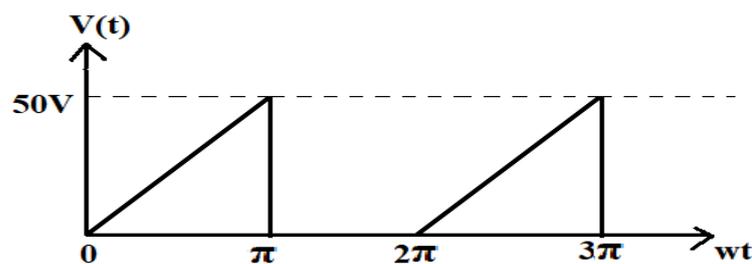3. a) Find the Trigonometric Fourier series for the following waveform shown in figure. [L4][CO4][5M]



- b) Find the Exponential Fourier series for the following waveform shown in figure. [L4][CO4][5M]

[L4][CO4][5M]

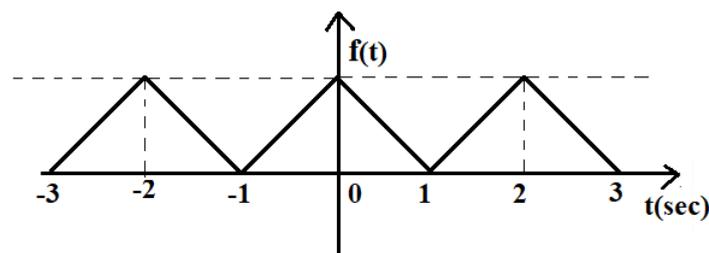

4. Write and prove the properties of Fourier transforms.


[L2][CO4][10M]

5. a) Explain about Line spectrum and Phase spectrum.

[L2][CO4][6M]


b) Obtain the magnitude and phase spectrum of the waveform shown in figure.

[L2][CO4][4M]

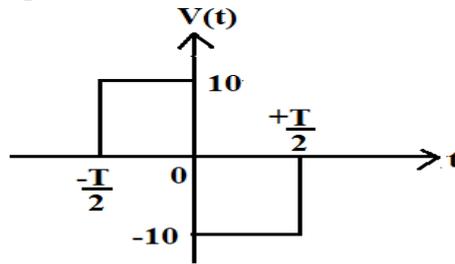


6. a) Find the Trigonometric Fourier series for the waveform shown in figure and sketch the spectrum.

[L4][CO4][6M]

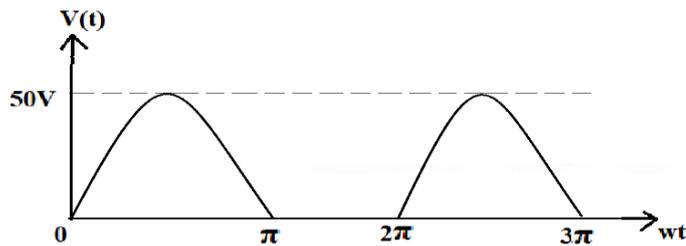



b) Find the Fourier transform of a periodic pulse train shown in figure.

[L4][CO4][5M]

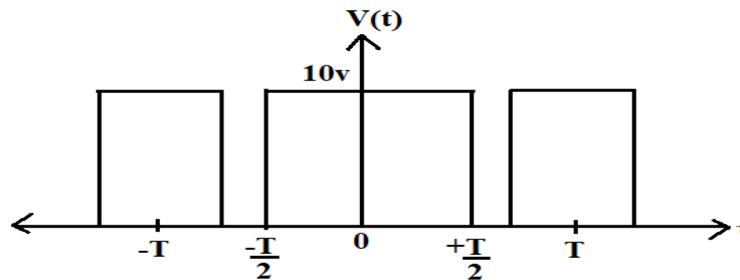



7. Determine the Fourier transforms of the following waveforms shown in figure(a) and figure(b).

[L4][CO4][10M]

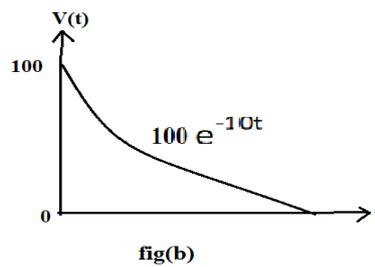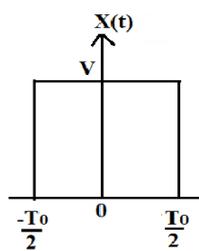


8. Determine the Fourier transforms of the following waveforms shown in figure (a) and figure (b).

[L4][CO4][10M]

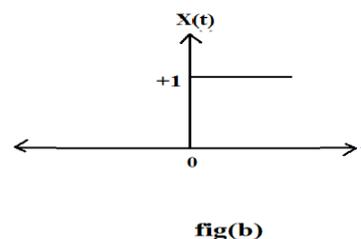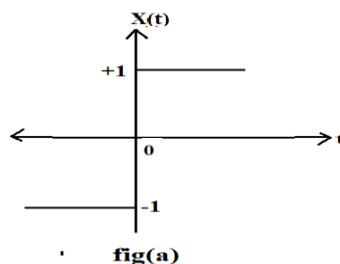

9. a) Find the Fourier Transform of a periodic unit impulse train shown in figure

[L4][CO4][5M]

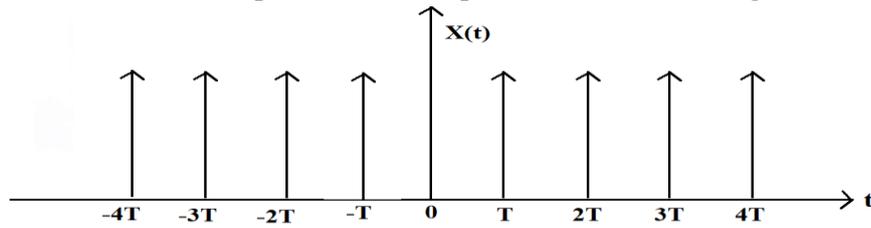

b) Explain about waveform symmetry for even and odd functions.

[L2][CO4][5M]

10. a) Define Fourier series.

[L1][CO4][2M]

b) Define Fourier transform.

[L1][CO4][2M]

c) Write the expression for trigonometric form of Fourier series.

[L1][CO4][2M]

d) Write the expression for exponential form of Fourier series.

[L1][CO4][2M]

e) Write any two properties of Fourier transforms.

[L1][CO4][2M]

Prepared By
V.MANASA REDDY