



**SIDDHARTH GROUP OF INSTITUTIONS :: PUTTUR**  
Siddharth Nagar, Narayanavanam Road – 517583

**QUESTION BANK (DESCRIPTIVE)**

**Subject with Code :** EMI(16EC416)

**Course & Branch:** B.Tech – ECE

**Year & Sem:** III B.Tech & I Sem

**Regulation:** R16

**UNIT –I**

1. a) Explain about static characteristics of measuring instrument. [CO1][L2][5M]  
b) Define any two statistical analysis of measuring instrument. [CO1][L1][5M]
2. a) Explain the construction of multi-range voltmeter & Range extension DC voltmeter. [CO1][L2][5M]  
b) A D'Arsonval movement with a full scale deflection current of  $50 \mu\text{A}$  and internal resistance of  $500\Omega$  is to be converted into a multirange voltmeter. Define the value of multiplier required for 0-20v, 0-50v, 0-100v, [CO1][L5][5M]
3. a) Explain different types of errors that occur in measurements. [CO1][L2][5M]  
b) Explain about Differential type voltmeter. [CO1][L2][5M]
4. a) How do we determine the performance characteristics (static & dynamic) of an instrument. [CO1][L1][8M]  
  
b) Explain the process of calibration. [CO1][L1][2M]
5. a) Define sensitivity. Calculate the sensitivity of a  $200 \mu\text{A}$  meter movement which is to be used as a dc voltmeter. [CO1][L1][2M]  
b) Draw and explain solid state DC Voltmeter. [CO1][L2][8M]
6. a) Explain the dynamic response of Zero order, first order, second order instrument. [CO1][L2][7M]  
b) Explain multirange AC voltmeter. [CO1][L2][3M]
7. a) With neat sketch explain thermocouple type RF ammeter. [CO1][L2][7M]  
b) Discuss about basic DC Ammeters. [CO1][L2][3M]
8. a) Describe with the help of circuit diagram the construction and working of a shunt-type ohm meter [CO1][L2][7M]  
  
b) Explain the fundamental principle on which DC meter is constructed. [CO1][L2][3M]
9. a) Explain how a multi-meter can be used as i) DC voltmeter & AC voltmeter [CO1][L2][7M]  
b) Explain how a multi-meter can be used as Ohmmeter [CO1][L2][3M]
10. a) Explain with the help of circuit diagram the construction & working of a series type ohm meter. [CO1][L2][7M]  
  
b) Explain about basic DC Ammeter. [CO1][L2][3M]

**UNIT –II**

1. a) Draw the neat diagrams of vertical deflection systems and explain briefly about their working. [CO2][L2][7M]  
 b) Discuss briefly about Horizontal amplifier [CO2][L2][3M]
2. a) Discuss about important CRT features. [CO2][L1][3M]  
 b) Draw the block diagram of a dual beam oscilloscope & explain its working. [CO2][L2][7M]
3. a) Draw the block diagram of a general purpose oscilloscope(CRO) and explain function of each block in detail . [CO2][L2][8M]  
 b) List the applications of CRO [CO2][L1][2M]
4. a) Explain the major parts of CRT with a block diagram. [CO2][L2][7M]  
 b) Compare dual trace oscilloscopes and dual beam CRO. [CO2][L4][3M]
5. a) Draw the block diagram of Delay line circuit and explain its working. [CO2][L2][7M]  
 b) State the standard specifications of a sample CRO. [CO2][L4][3M]
6. a) Discuss in detail, the construction and working of a digital sampling oscilloscope. [CO2][L2][5M]  
 b) Explain in details the construction and working of Time base generator [CO2][L2][5M]
7. a) Describe in details the construction and working of an analog type storage oscilloscope. [CO2][L2][5M]  
 b) Explain with the block diagram how the digital frequency can be measured using counter/meter instrument. [CO2][L2][5M]
8. a) Describe in details the construction and working of an digital storage oscilloscope [CO2][L2][5M]  
 b) Explain the function of trigger circuit. [CO2][L2][5M]
9. a) Explain with a diagram how frequency & phase can be measured using a Lissajous method. [CO2][L1][5M]  
 b) Briefly discuss about digital storage oscilloscope. [CO2][L1][5M]
10. a) Explain with the block diagram how the digital frequency and time period can be measured using Counter/meter instrument. [CO2][L1][6M]  
 b) List and explain any two different types of CRO probes? [CO2][L1][4M]

**UNIT –III**

1. a) With the help of block diagram explain the functioning of a conventional standard signal generator. [CO3][L2][7M]  
 b) Describe about fixed AF oscillator and variable AF oscillator. [CO3][L2][3M]
2. a) Draw the block diagram of a function generator and explain its operation. [CO3][L2][7M]  
 b) List the applications of random noise generator. [CO3][L2][3M]
3. a) With a neat diagram discuss the operation of a pulse generator. [CO3][L2][6M]  
 b) Explain the working of arbitrary waveform generator [CO3][L2][4M]
4. a) Discuss in detail about RF signal generator operation. [CO3][L2][5M]  
 b) Explain the method of generating of random noise with neat sketch [CO3][L2][5M]
5. a) Explain the working of a standard sweep generator with diagram. [CO3][L2][7M]  
 b) Define sweep generator [CO3][L1][3M]
6. a) With help of a neat sketch, explain the working of a frequency selective wave analyser. [CO3][L2][7M]  
 b) Define the function of wave analyser? [CO3][L1][3M]
7. a) Describe with diagram the operation of a Logic analyser. [CO3][L2][7M]  
 b) List the application of wave analysers. [CO3][L1][3M]
8. a) Draw the circuit diagram and explain the working of a heterodyne type wave analyser. [CO3][L2][7M]  
 b) What is distortion? What does a distortion analyser measure [CO3][L1][3M]
9. a) Define the function of harmonic distortion analyser. [CO3][L1][3M]  
 b) Describe the diagram with operation of a harmonic distortion analyser using Wein bridge and frequency selective type. [CO3][L2][7M]
10. a) With a neat sketch explain the operation of Spectrum analyser. [CO3][L2][5M]  
 b) Explain how wave analyser can be tuned to a particular frequency within the audible frequency range. [CO3][L2][5M]

**UNIT –IV**

1. a) Discuss the working principle of Q-meter & its applications. [CO4][L2][6M]  
 b) Write short note on interference & explain noise reduction techniques. [CO4][L2][4M]
2. a) Explain any Two ac bridges to measure unknown inductance. [CO4][L2][8M]  
 b) Distinguish between AC Bridges and DC bridges [CO4][L2][2M]
3. a) Describe in detail about EMI & EMC with suitable examples. [CO4][L2][4M]  
 b) Explain the working principle & operation of Capacitance & Inductance bridge circuit [CO4][L2][6M]
4. a) Explain the operation of Kelvin Bridge. [CO4][L2][4M]  
 b) Derive the expression for unknown resistance of kelvin bridge [CO4][L2][6M]
5. a) Discuss briefly about bridges? [CO4][L2][3M]  
 b) Draw the Anderson's bridge circuit and derive necessary equations & explain it. [CO4][L2][7M]
6. a) Explain the Schering bridge circuit [CO4][L2][8M]  
 b) List the applications of schering bridge circuit [CO4][L1][2M]
7. a) Explain how a Maxwell bridge can be used for measuring an unknown inductance. [CO4][L2][6M]  
 b) What is interference & explain noise reduction techniques. [CO4][L2][4M]
8. a) Describe the operation of the Wheatstone bridge [CO4][L2][5M]  
 b) Derive the expression for current when the bridge is balanced. [CO4][L2][10M]
9. a) Explain how a Maxwell bridge can be used for measuring an unknown inductance. [CO4][L2][5M]  
 b) A Maxwell bridge is used to measure an inductive impedance the bridge constants at balance are  $C1=0.01 \mu\text{F}$ ,  $R1=470\text{K}\Omega$ ,  $R2=5.1 \text{K}\Omega$  and  $R3=100 \text{K}\Omega$ . Find the series equivalent of the unknown impedance. [CO4][L5][5M]
10. a) What are the applications of Wheatstone bridge. And list out its limitations. [CO4][L2][4M]  
 b) Describe the operation of the Wheatstone bridge and derive the expression for DC resistance. [CO4][L2][6M]

**UNIT –V**

- |   |               |
|---|---------------|
| 1. a) With a neat sketch explain the operation of LVDT.                                       | [CO5][L2][8M] |
| b) What are the advantages & disadvantages of LVDT  | [CO5][L2][2M] |
| 2. a) Explain strain gauge for resistance measurement   | [CO5][L2][8M] |
| b) List the applications of LVDT  | [CO5][L2][2M] |
| 3. a) Describe the operation of i) resistive transducers                                      | [CO5][L2][5M] |
| b) Describe the operation of capacitive transducers.  | [CO5][L2][5M] |
| 4. a) Distinguish between the active & passive transducers.                                   | [CO5][L2][3M] |
| b) Explain the operation of potentiometric transducer.  | [CO5][L2][7M] |
| 5. a) Define a transducer. List the applications.   | [CO5][L1][3M] |
| b) Explain about Inductive transducers.   | [CO5][L2][7M] |
| 6. a) Draw the diagram of Resistance Thermometer & explain briefly.                           | [CO5][L2][7M] |
| b) What are the functions of transducers?   | [CO5][L1][3M] |
| 7. a) Write short notes on i) LVDT ii) thermocouple   | [CO5][L2][6M] |
| b) Discuss about signal conditioning circuits.  | [CO5][L2][4M] |
| 8. a) With a neat sketch, explain the operation of piezo-electric transducers in detail.      | [CO5][L2][7M] |
| b) Explain how an electrical transducer can be used to find the unknown pressure of a liquid. | [CO5][L2][3M] |
| 9. a) List the three types of temperature transducers & describe the application of each.     | [CO5][L2][5M] |
| b) Explain about pH measurement.  | [CO5][L2][5M] |
| 10. a) Define piezoelectric effect. Write the applications of piezoelectric transducer.       | [CO5][L2][5M] |
| b) Write about IC sensors & smart sensors.  | [CO5][L2][5M] |

Prepared by: **A.RAJASEKHAR YADAV & CH.SILPA**

