

Time: 3 Hours

Max. Marks: 70

PART-A

(Answer all the Questions 10 x 2 = 20 Marks)

- | | | | | | |
|---|---|--|-----|----|----|
| 1 | a | What is the need for multistage amplifiers? | CO1 | L1 | 2M |
| | b | Draw the h-parameter model of a transistor. | CO1 | L1 | 2M |
| | c | List the internal capacitances of MOS differential amplifier. | CO1 | L4 | 2M |
| | d | Define gain of an amplifier and express it in dB. | CO1 | L1 | 2M |
| | e | List the four basic feedback topologies. | CO1 | L2 | 2M |
| | f | Define oscillator and list the types of oscillators. | CO1 | L1 | 2M |
| | g | Define Power amplifier. List the different types of power amplifiers. | CO3 | L1 | 2M |
| | h | Give the expression for total harmonic distortion (THD) in an amplifier. | CO3 | L1 | 2M |
| | i | Define tuned amplifier and list the applications of tuned amplifiers. | CO2 | L1 | 2M |
| | j | Differentiate between astable and Monostable multivibrators. | CO3 | L2 | 2M |

PART-B

(Answer all Five Units 5 x 10 = 50 Marks)

UNIT-I

- | | | | | | |
|---|---|--|-----|----|----|
| 2 | a | Define distortion. Explain the cause and effects of amplitude, frequency and phase distortion in an amplifier. | CO1 | L2 | 5M |
| | b | Classify the amplifiers. | CO1 | L4 | 5M |

OR

- | | | | | | |
|---|--|---|-----|----|-----|
| 3 | | With suitable circuit diagrams, derive the expression for differential voltage gain of a MOS differential amplifier using small signal operation. | CO2 | L3 | 10M |
|---|--|---|-----|----|-----|

UNIT-II

- | | | | | | |
|---|---|--|-----|----|----|
| 4 | a | Draw the high frequency model of MOSFET. | CO2 | L2 | 5M |
| | b | With relevant circuit diagrams, explain the internal capacitive effects of MOSFET. | CO2 | L2 | 5M |

OR

- | | | | | | |
|---|---|---|-----|----|----|
| 5 | a | Derive the relation between f_T and f_β for a BJT CE amplifier operating at high frequency. | CO2 | L4 | 5M |
| | b | Short circuit CE current gain of a transistor is 20 at a frequency of 1MHz. If $f_\beta = 200\text{KHz}$, Calculate (i) f_T (ii) h_{fe} (iii) Find $ A_v $ at frequency of 10MHz | CO2 | L4 | 5M |

UNIT-III

- | | | | | | |
|---|---|--|-----|----|----|
| 6 | a | Explain the four feedback amplifier topologies in detail with neat block diagrams. | CO3 | L5 | 6M |
| | b | Explain types of samplers and mixers used in negative feedback amplifiers. | CO3 | L2 | 4M |

OR

- | | | | | | |
|---|---|--|-----|----|----|
| 7 | a | Determine the frequency of oscillations when a RC phase shift oscillator has $R=10\text{k}\Omega$, $C=0.01\mu\text{F}$ and $RC = 2.2 \text{ K}\Omega$. Also find the minimum current gain needed for this purpose. | CO4 | L3 | 5M |
| | b | In a Wein-bridge oscillator, if the value of R is 100 K Ω , and frequency of oscillation is 10 KHz, Calculate the value of capacitor C. | CO4 | L4 | 5M |

UNIT-IV

- | | | | | | |
|---|---|---|-----|----|----|
| 8 | a | With neat diagrams, explain Series fed directly coupled Class A Power amplifier. | CO3 | L2 | 5M |
| | b | Derive the maximum efficiency expression for Series fed directly coupled Class A Power Amplifier. | CO3 | L3 | 5M |

OR

- | | | | | | |
|---|---|--|-----|----|----|
| 9 | a | Compare class A, class B, Class AB and Class C power amplifiers. | CO3 | L4 | 5M |
| | b | Describe the structure of Power MOSFET. | CO3 | L2 | 5M |

UNIT-V

- | | | | | | |
|----|---|--|-----|----|----|
| 10 | a | Explain the operation of Schmitt trigger. | CO3 | L5 | 5M |
| | b | Determine the value of capacitors to be used in an Astable multivibrator to provide a train pulse $2\mu\text{s}$ wide at a repetition rate of 100 KHz, if $R_1 = R_2 = 20\text{k}\Omega$. | CO5 | L2 | 5M |

OR

- | | | | | | |
|----|---|---|-----|----|----|
| 11 | a | Explain the operation of a single tuned capacitive coupled amplifier with a neat circuit diagram. | CO2 | L2 | 5M |
| | b | Compare different types of tuned amplifiers. | CO1 | L4 | 5M |

*** END ***