

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR**  
(AUTONOMOUS)

B.Tech. II Year II Semester Supplementary Examinations December-2025

**ELECTRONIC CIRCUITS ANALYSIS**

(Electronics & Communications Engineering)

Time: 3 Hours

Max. Marks: 70

**PART-A**

(Answer all the Questions 10 x 2 = 20 Marks)

- |     |  |     |    |    |
|-----|--|-----|----|----|
| 1 a | A three-stage amplifier has gain of 10 dB, 20 dB and 30 dB respectively. Calculate overall gain of the amplifier | CO2 | L3 | 2M |
| b   | Define bandwidth of an amplifier and give its unit.  | CO1 | L1 | 2M |
| c   | List the internal capacitances of MOS differential amplifier.  | CO1 | L1 | 2M |
| d   | What is gain bandwidth product?  | CO1 | L1 | 2M |
| e   | What is meant by feedback? Classify the types of feedback.   | CO1 | L1 | 2M |
| f   | Define oscillator and list the types of oscillators.   | CO1 | L1 | 2M |
| g   | State total harmonic distortion (THD) in an amplifier mathematically.  | CO3 | L1 | 2M |
| h   | List the key characteristics of power BJTs.  | CO3 | L1 | 2M |
| i   | Define tuned amplifier and list the applications of tuned amplifiers.  | CO2 | L1 | 2M |
| j   | Differentiate between Astable and Monostable multivibrators.   | CO2 | L2 | 2M |

**PART-B**

(Answer all Five Units 5 x 10 = 50 Marks)

**UNIT-I**

- |     |   |     |    |    |
|-----|---|-----|----|----|
| 2 a | Define distortion. Explain the cause and effects of amplitude, frequency and phase distortion in an amplifier.            | CO1 | L2 | 5M |
| b   | Construct the circuit diagram of BJT cascode amplifier and derive the expressions for $A_v$ , $A_i$ , $R_i$ , and $R_o$ . | CO2 | L3 | 5M |

**OR**

- |     |   |     |    |    |
|-----|---|-----|----|----|
| 3 a | List the non-ideal characteristics of a differential amplifier.                                   | CO1 | L1 | 4M |
| b   | Explain in detail about input offset voltage and input offset current of a BJT differential pair. | CO1 | L2 | 6M |

**UNIT-II**

- |     |  |     |    |    |
|-----|--|-----|----|----|
| 4 a | Derive the break frequencies of CE (Common Emitter) amplifier at low frequencies. Obtain the expression for overall gain or transfer function and draw the frequency response. | CO2 | L3 | 5M |
| b   | Draw the high frequency model of BJT.  | CO1 | L1 | 5M |

**OR**

- |   |  |     |    |     |
|---|--|-----|----|-----|
| 5 | Derive the expressions for gain and upper 3dB frequency of a MOSFET CS amplifier operating at high frequency and draw the high frequency response. | CO2 | L3 | 10M |
|---|--|-----|----|-----|

**UNIT-III**

- |     |   |     |    |    |
|-----|---|-----|----|----|
| 6 a | Explain in detail about the types of basic amplifiers used in feedback amplifier topologies.                                      | CO3 | L2 | 5M |
| b   | Draw the structure and equivalent circuit of series-shunt topology and derive the equations for $A_f$ , $R_{if}$ , and $R_{of}$ . | CO3 | L3 | 5M |

**OR**

- |     |   |     |    |
|-----|---|-----|----|
| 7 a | Determine the frequency of oscillations for Hartley and Colpitts oscillator with suitable equation and circuit diagram                      | CO4 | L4 |
| b   | In Colpitts oscillator, $C_1 = 0.2\mu F$ and $C_2 = 0.02\mu F$ . If the frequency of oscillation is 10kHz, Calculate the value of inductor. | CO4 | L4 |

**UNIT-IV**

- |     |  |     |    |
|-----|--|-----|----|
| 8 a | Derive the maximum efficiency expression for Series fed directly coupled Class A Power Amplifier.            | CO3 | L3 |
| b   | Discuss about Transformer coupled Class A Power Amplifier with diagram and determine its Maximum efficiency. | CO3 | L2 |

**OR**

- |     |  |     |    |
|-----|--|-----|----|
| 9 a | Compare class A, class B, Class AB and Class C power amplifiers. | CO3 | L2 |
| b   | Explain the V-I Characteristics of Power MOSFETs.                | CO3 | L2 |

**UNIT-V**

- |      |   |     |    |
|------|---|-----|----|
| 10 a | Explain the operation of a single tuned capacitive coupled amplifier with a neat circuit diagram.   | CO2 | L2 |
| b    | Deduce the expressions for Quality factor, voltage gain and bandwidth of a single tuned capacitive coupled amplifier with necessary circuit diagrams. | CO2 | L4 |

**OR**

- |    |   |     |    |
|----|---|-----|----|
| 11 | With a neat circuit diagram, explain the working of a collector coupled Astable multivibrator and draw the i/p-o/p waveforms. | CO3 | L2 |
|----|---|-----|----|

